

Homework #7

	V_S	V_G	V_D	$ V_{GS} $	$ V_{ov} $	$ V_{DS} $	Region of operation	
1.	+1	+1	+2	0V	-1V	1V	Cutoff	$V_t = 1V$
	+1	+2.5	+1.5	1.5V	.5V	.5V	triode	
	0	+2.5	+1	2.5V	1.5V	1V	triode	
	-1	0	+1	-1V	0V	2V	Saturation	


	V_S	V_G	V_D	$ V_{GS} $	$ V_{ov} $	$ V_{DS} $	Region of operation	
2.	2	2	0	0V	1V	2V	Cutoff	$V_t = -1V$
	2	0	0	2V	1V	2V	Cutoff	
	2	0	1.5	2V	1V	.5V	Cutoff	

3.

- Assume saturation
- Put $I_G = 0$ and $I_D = I_S$
- Use $I_D = \frac{1}{2} k_n (\frac{W}{L}) (V_{GS} - V_t)^2$
- calculate Voltages and current
- Check saturation conditions $\Rightarrow |V_{DS}| > |V_{GS}| - |V_t|$

4. NMOS is built with n-type source and drain and a p-type substrate, while PMOS is built with p-type source and drain and n-type substrate. NMOS carriers are electrons, PMOS carriers are holes. When high voltage is applied to gate, NMOS conducts while PMOS will not. When low, PMOS conducts and NMOS does not.

$$5. \quad |V_T| = 2V \quad k'n\left(\frac{W}{L}\right) = 1mA/V^2, \quad \lambda = 0$$

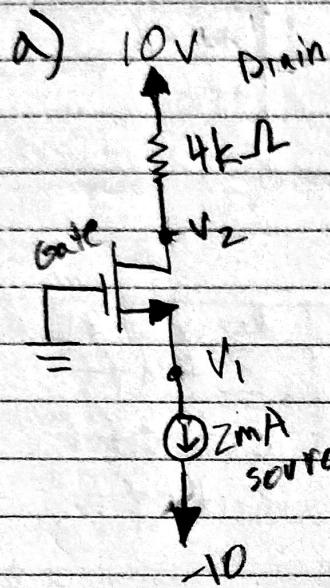

$$V_2 = 10V \cdot (2mA) (4k\Omega)$$

$$\boxed{= 2V}$$


$$2mA = \frac{1}{2} (1mA) (V_{GS} - 2)^2$$

$$V_{GS} = 4$$

$$V_G = 0$$

$$4 = 0 - V_S$$

b)

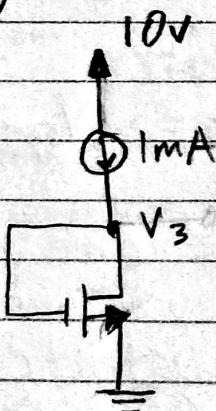


$$\boxed{V_1 = V_S = -4V}$$

$$1mA = \frac{1}{2} (1mA) (V_{GS} - 2)^2$$


$$V_{GS} = 3.4V$$

$$V_S = 0$$

$$\boxed{V_G = V_3 = 3.4V}$$

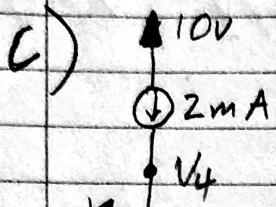

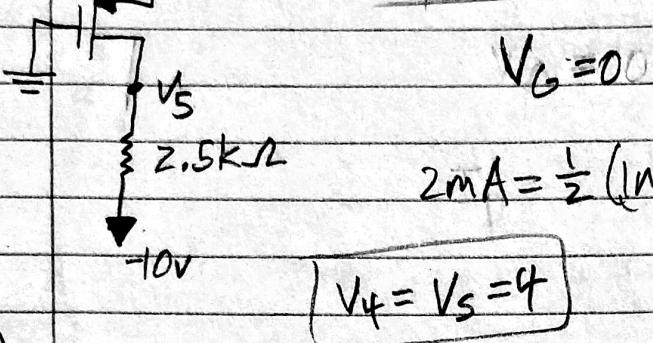
$$V_5 = -2 \text{ mA} (2.5 \text{ k}\Omega) = -5 \text{ V}$$



$$2 \text{ mA} = \frac{1}{2} (1 \text{ mA}) (V_s - 2)^2$$


$$| V_4 = V_s = 4 \text{ V}$$

d)

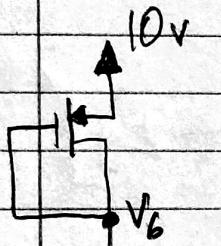

$$2 \text{ mA} = \frac{1}{2} (1 \text{ mA}) (-V_G + 10 - 2)^2$$


$$| V_G = V_6 = 6 \text{ V}$$

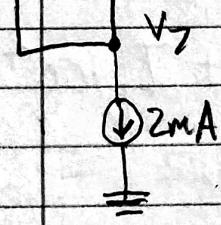

$$2 \text{ mA} = \frac{1}{2} (1 \text{ mA}) (-V_G + 6 - 2)^2$$

$$| V_G = V_7 = 2 \text{ V}$$
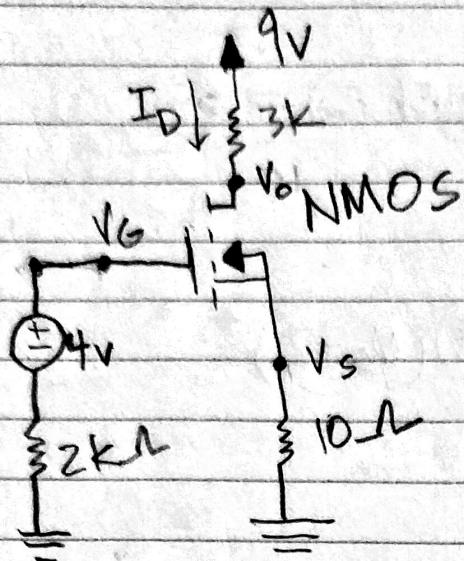
$$6. \quad V_t = 2V \quad k_n(\frac{W}{L}) = 4mA/V^2 \quad \lambda = 0$$



a)

$$I_D = \frac{1}{2} (4mA) \left[(4 - I_D(10\Omega)) - 2 \right]^2$$

$$500 \cdot I_D = [2 - I_D(10)]^2$$

$$I_1 = 0$$

$$500I_D = 4 - 20I_D - 20I_D + I_D 100^2$$

$$0 = 4 - 540I_D + I_D 100^2$$

$$I_D = \frac{538.51648071}{2(100)}$$

$$I_S = I_D = \frac{-540 \pm \sqrt{540^2 - 4(100)(4)}}{2(100)}$$


For 7.4mA:

$$-7.4mA, -5.39A$$

$$V_S = (7.4mA)(10) = .074V$$

$$V_{GS} = 4V - .074 = 3.26V > V_t \quad \text{Saturation!}$$

$$V_{DS} = 9V - 0.74V = 8.26V > 3.26 - 2 = 1.26$$

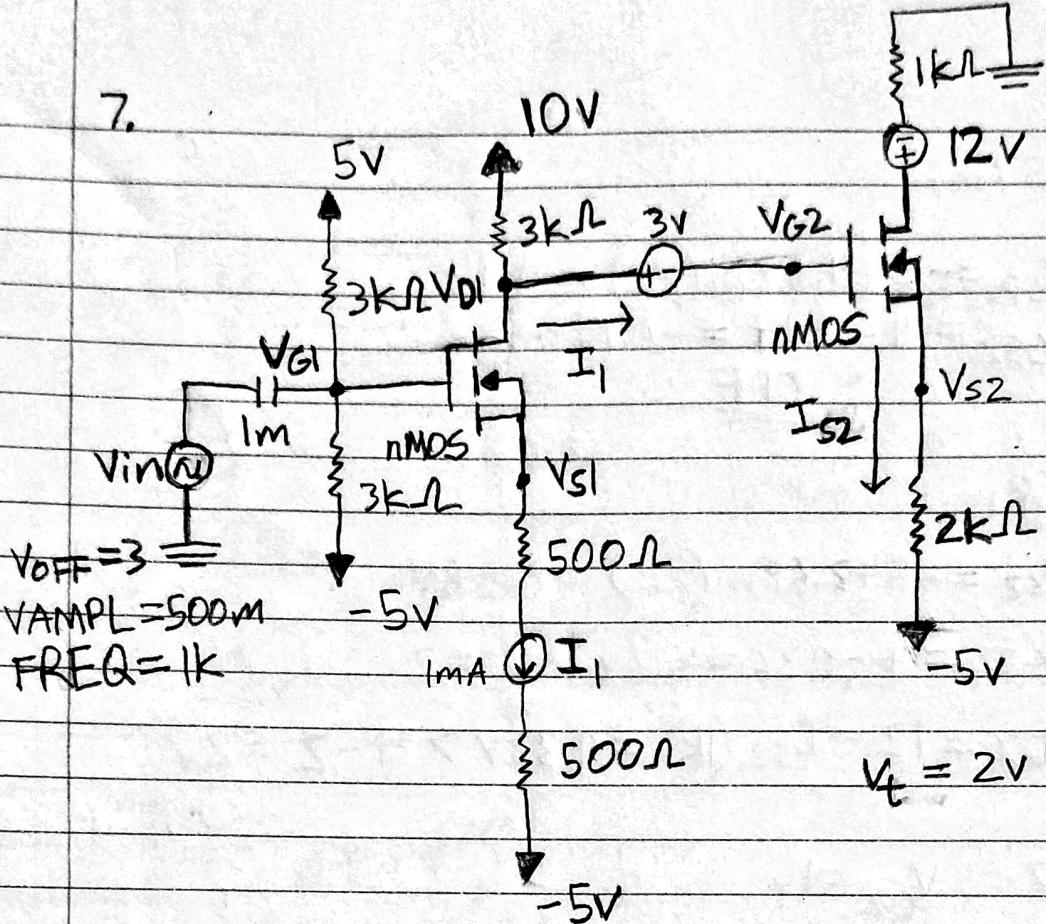

For 4.57m:

$$V_{S2} = -5 + 4.57m(2k) = 4.14$$
$$V_{GS2} = 4 - 4.14 = -0.14 < V_t = 2$$

OFF

For 2.68m:

$$V_{S2} = -5 + 2.68m(2k) = 0.36V$$

$$V_{GS2} = 4 - 0.36 = 3.64 > V_t = 2$$

$$V_{D2} = 12 - I_{S2}(1k) = 9.32V > 4 - 2 = 2V$$


SAT

$$I_s = 0 \quad V_{G2} = 4V$$

$$I_{S2} = 2.68m \quad V_{G2} = 4V$$

$$V_{S2} = 0.36V$$

8.

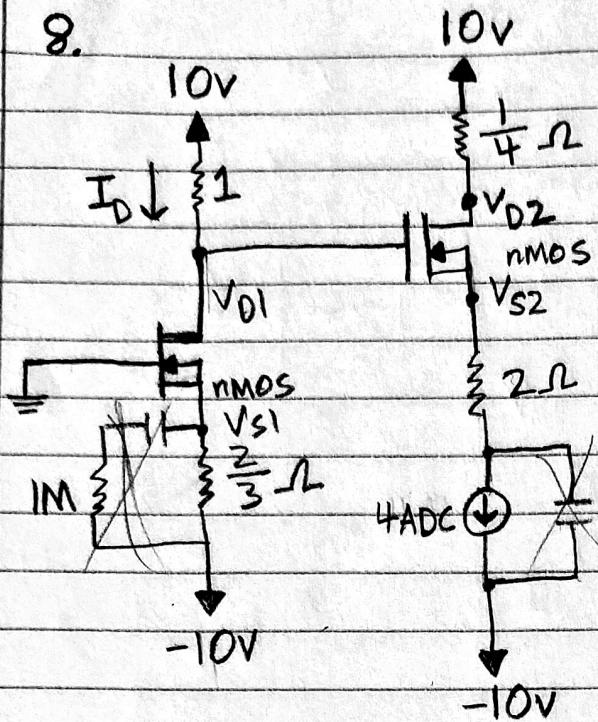

$$V_t = 1V$$

$$k'n\left(\frac{W}{L}\right) = 2A/V^2$$

$$\lambda = 0$$

$$V_{DS2} = 9 - 4 = 5$$

$$V_{GS2} = 1 - 4 = -3$$

$$4 = \frac{1}{2}(2)(1 - V_s - 1)^2$$

$$4 = V_s^2 / 5 > 3 - 1 \quad \text{SAT}$$

$$V_{D2} = 10 - 1 = 9V$$

$$V_{G1} = 0$$

$$V_{S1} = -10 + I_D (2/3)$$

$$I_{D1} = \frac{1}{2}(2A)(10 + I_D (2/3) - 1)^2$$

$$I_{D1} = 81 - I_D 6 - I_D 6 + I_D \frac{4}{9}$$

$$0 = 81 - I_D 13 + I_D^2 \frac{4}{9}$$

$$143 \pm \sqrt{13^2 - 4(\frac{4}{9})(81)}$$

$$2(4)$$

$$9, 20.25$$

$$V_{D1} = 10 - 9 = 1V$$

$$V_{D1} = 10 - 20.25 = 10.25V$$

$$V_{S1} = -10 + 6 = -4$$


$$V_{S1} = -10 + 13.5 = 3.5$$

$$V_{DS1} = 5V$$

$$V_{GS1} = 4V$$

$$V_{DS1} = 6.75$$

$$V_{GS1} = -3.5$$

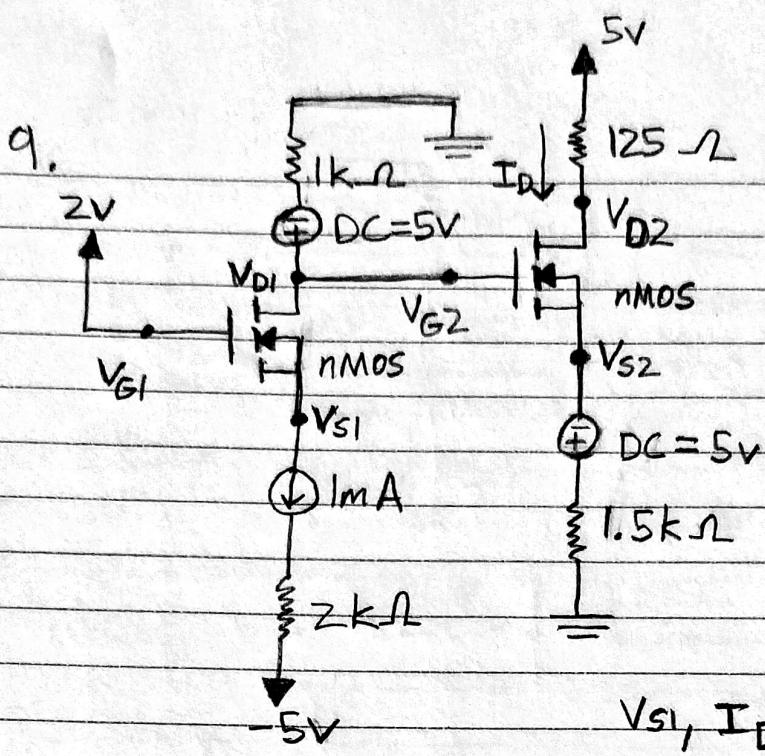

$$V_t = 1V$$

$$K_n \left(\frac{W}{L} \right) = 2mA$$

$$\lambda = 0$$

V_{S1}, I_D, V_{D2} ?

$$1mA = \frac{1}{2} (2mA) (2 - V_{S1} - 1)^2$$

$V_{S1} = 0$

$$V_{D1} = 5V$$

$$I_D = \frac{1}{2} (2mA) (5 - I_D (1.5k) + 5 - 1)^2$$

$$1kI_D = (9 - I_D 1.5k)^2$$

$$81 - 13.5kI_D - 13.5kI_D + I_D^2 2.25M$$

$$0 = I_D^2 2.25M - 28kI_D + 81$$

$$28k \pm \sqrt{-28k^2 - 4(2.25M)(81)} \\ 2(2.25M)$$

.0045, .0078


$V_{D2} = 5 - 4mA(125) = 4.5V$

$$V_{S2} = 1.5k(4mA) - 5 = 1V$$

$$V_{GS} = 5 - 1 = 4V$$


$$V_{DS} = 4.5 - 1 = 3.5$$
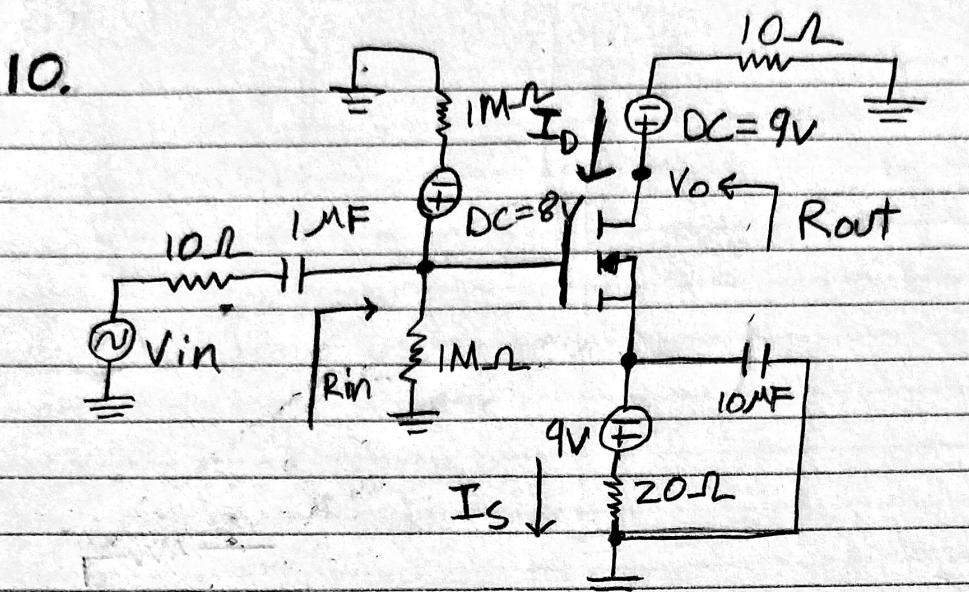
$$3.5 > 4 - 1 \quad \underline{\underline{SAT}}$$



$$V_t = 2V$$
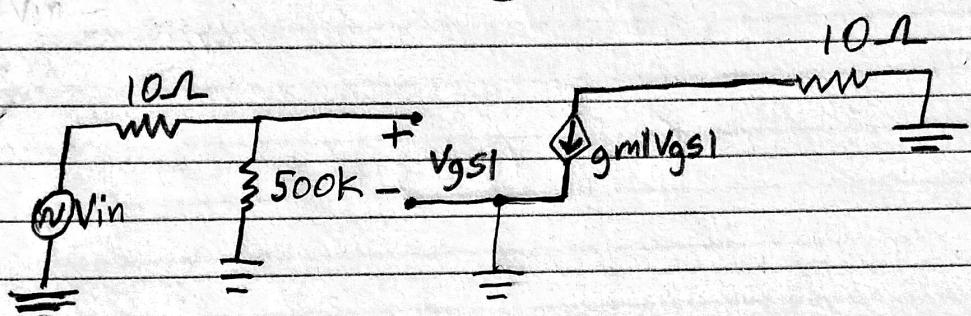
$$k'n(\frac{W}{L}) = 180 \text{ mA/V}^2$$



$$gm = \sqrt{(180 \text{ mA})(2)(10 \text{ mA})} = 1.9 \text{ mA}$$

$$V_c = 8$$

~~$$I_D = \frac{1}{2}(180)(8 - (9 - 2) - 2)$$~~

~~$$11.111kI_D = (-3 + 2(I_D))^2$$~~

~~$$11.111kI_D = 9 - 6I_D - 60I_D + 400I_D^2$$~~

~~$$I_D = 9 - 112.21I_D + 400I_D^2$$~~

~~$$112.21I_D^2 + 9 - 112.21I_D - 400(9)$$~~

~~$$2(I_D)$$~~