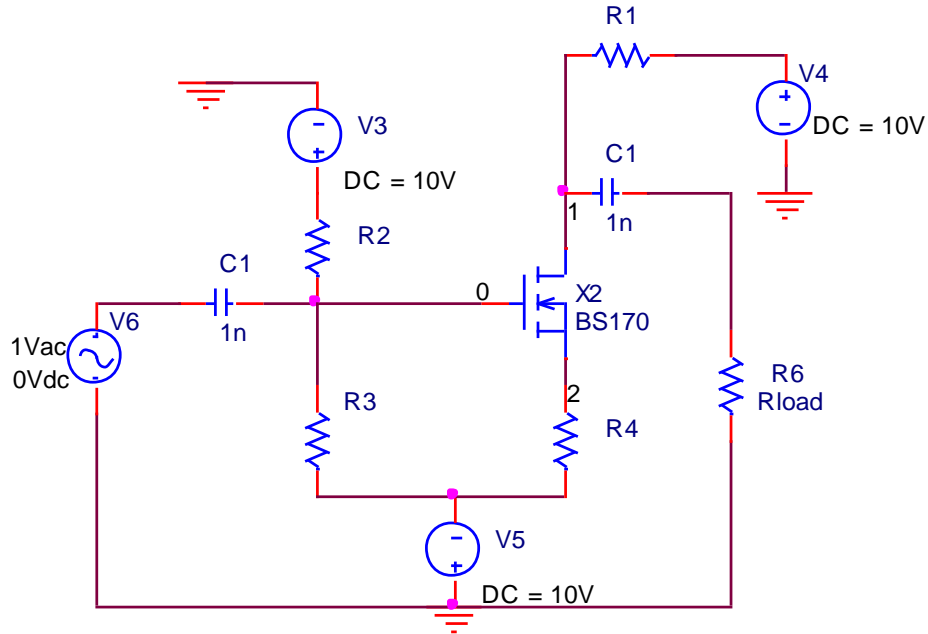



## Finding output impedance for a circuit


Assume with the circuit below that the output impedance is wanted from the marked voltage node.




Step 1: Remove the input V6 and set it to ground or the input values to zero.

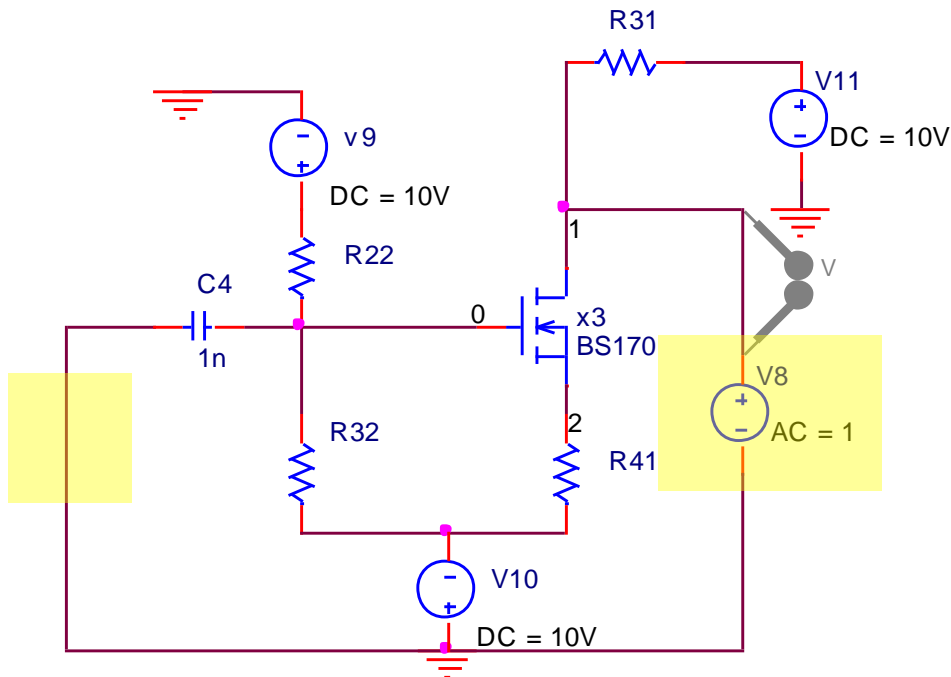Step 2: Replace the load resistor, R6 with a test source (Current or Voltage for out example) and place V marker and I marker at the node you want to find the resistance.




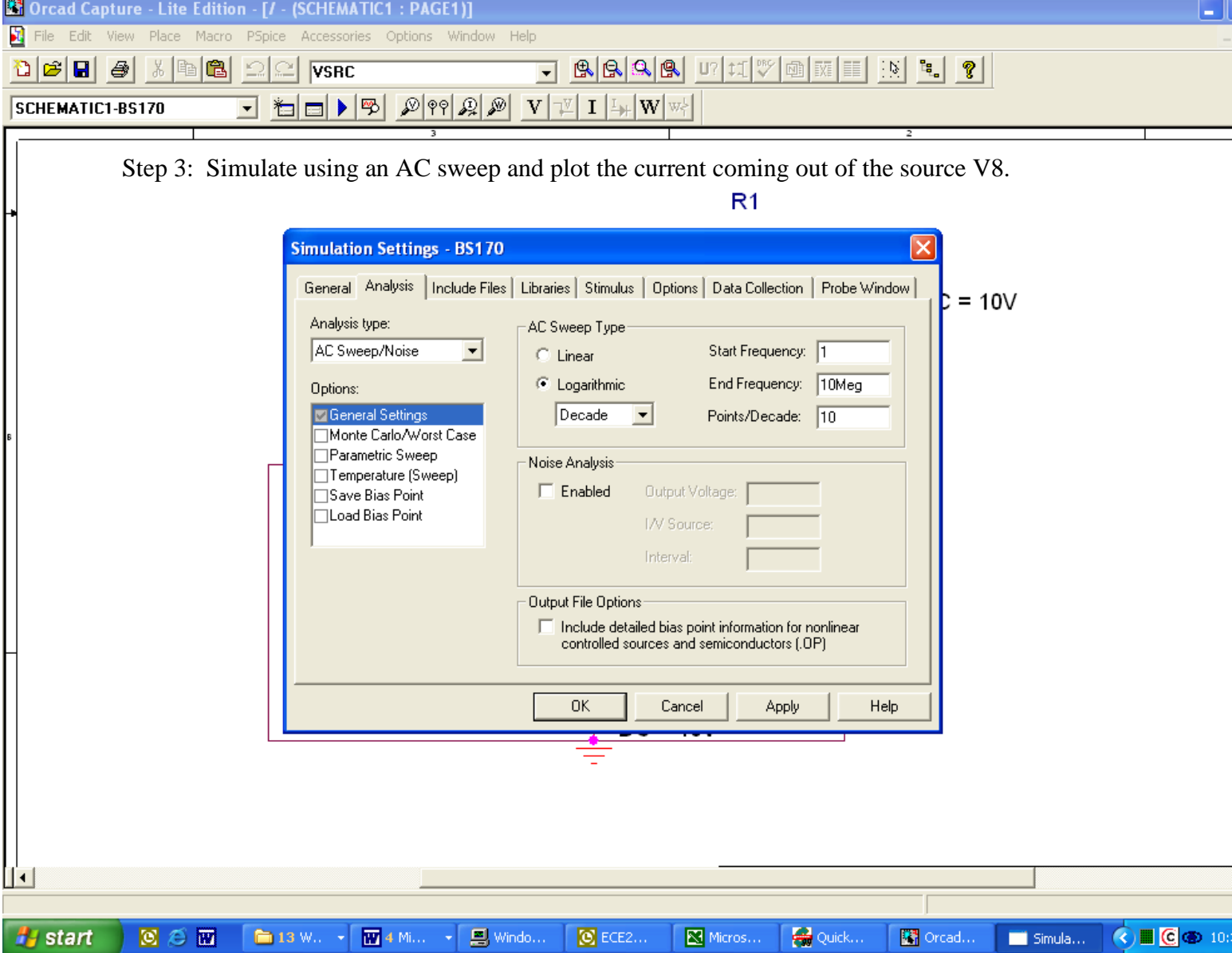

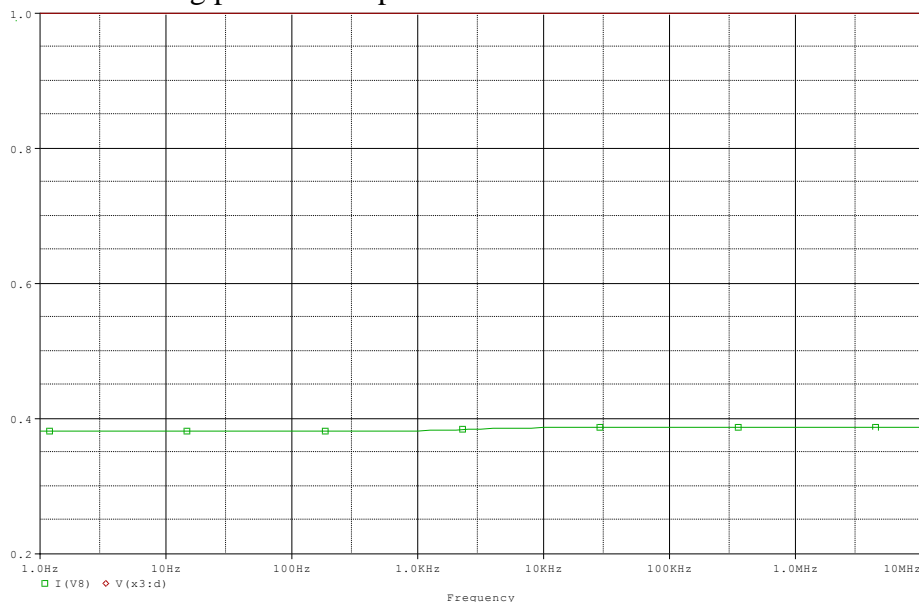
Step 4. Determine the output impedance vs frequency value =>  
a. The following plot comes up of I and V on it.



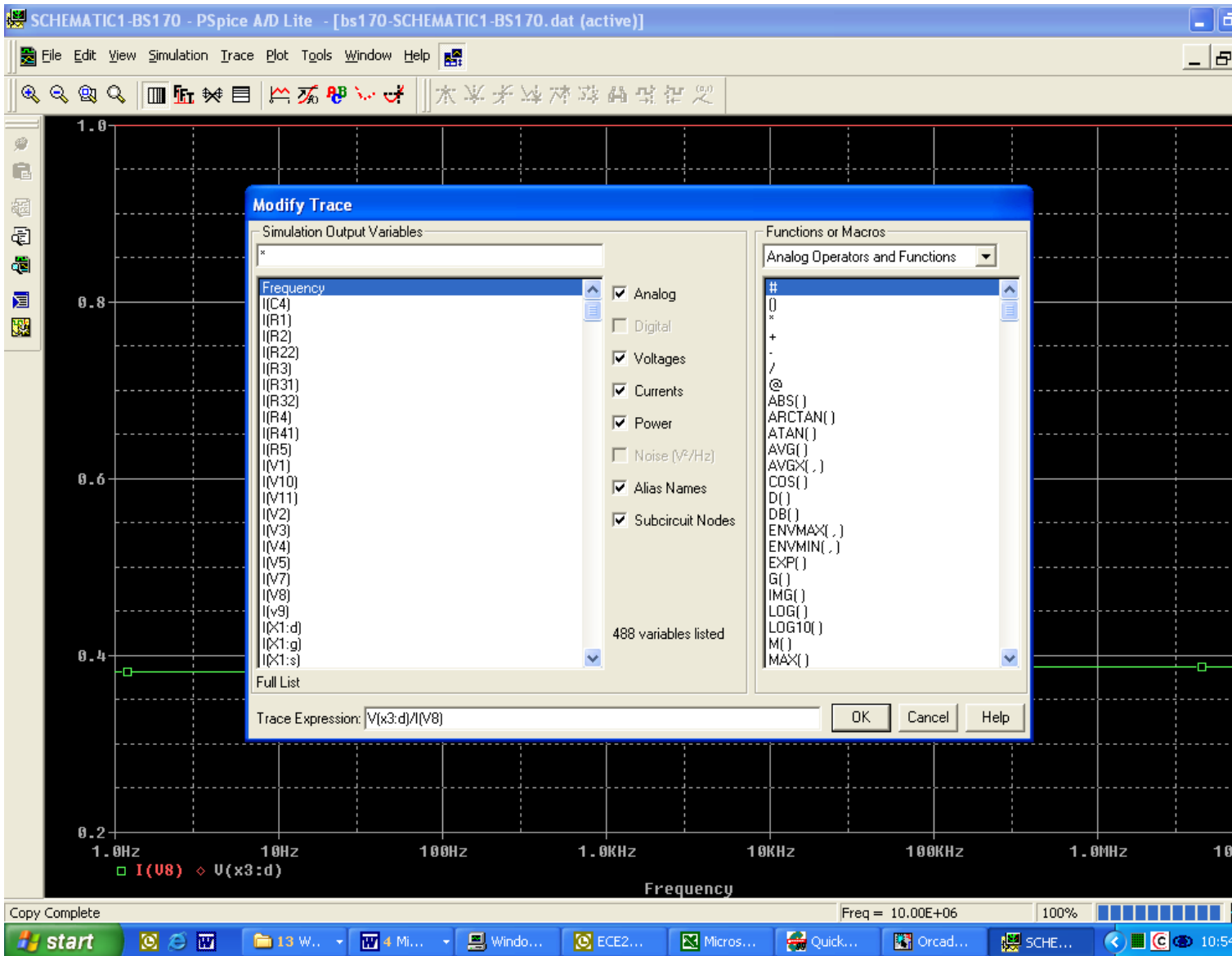Note that the current is I(V8) and the voltage is V(x3:d) =>



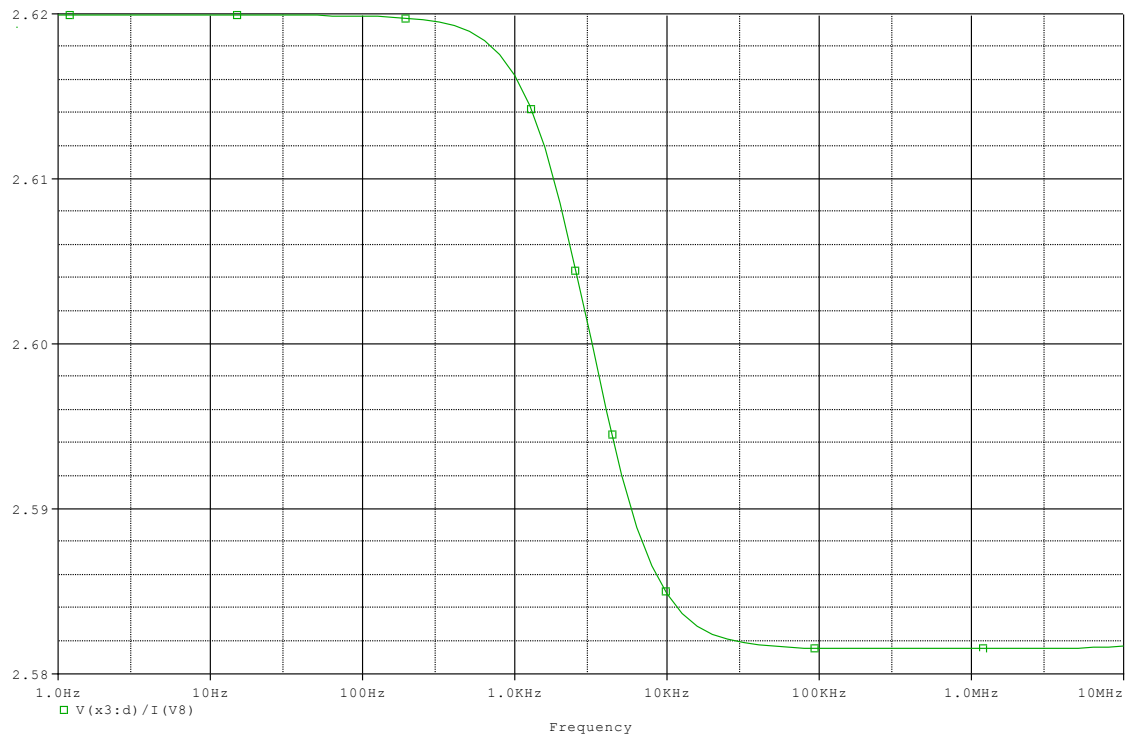
Get to the Modify Trace window (either by double clicking on the variable I(V8) or a different variable or through the menus. Replace the Trace Expression with V/I to give you the graph of resistance vs frequency. Trace Expression: V(x3:d)/I(V8) {your node voltages will be different than mine}. The resultant plot should look something like the form below:




where this shows  $R_{out} = 2.62$  when it is under 200 Hz.
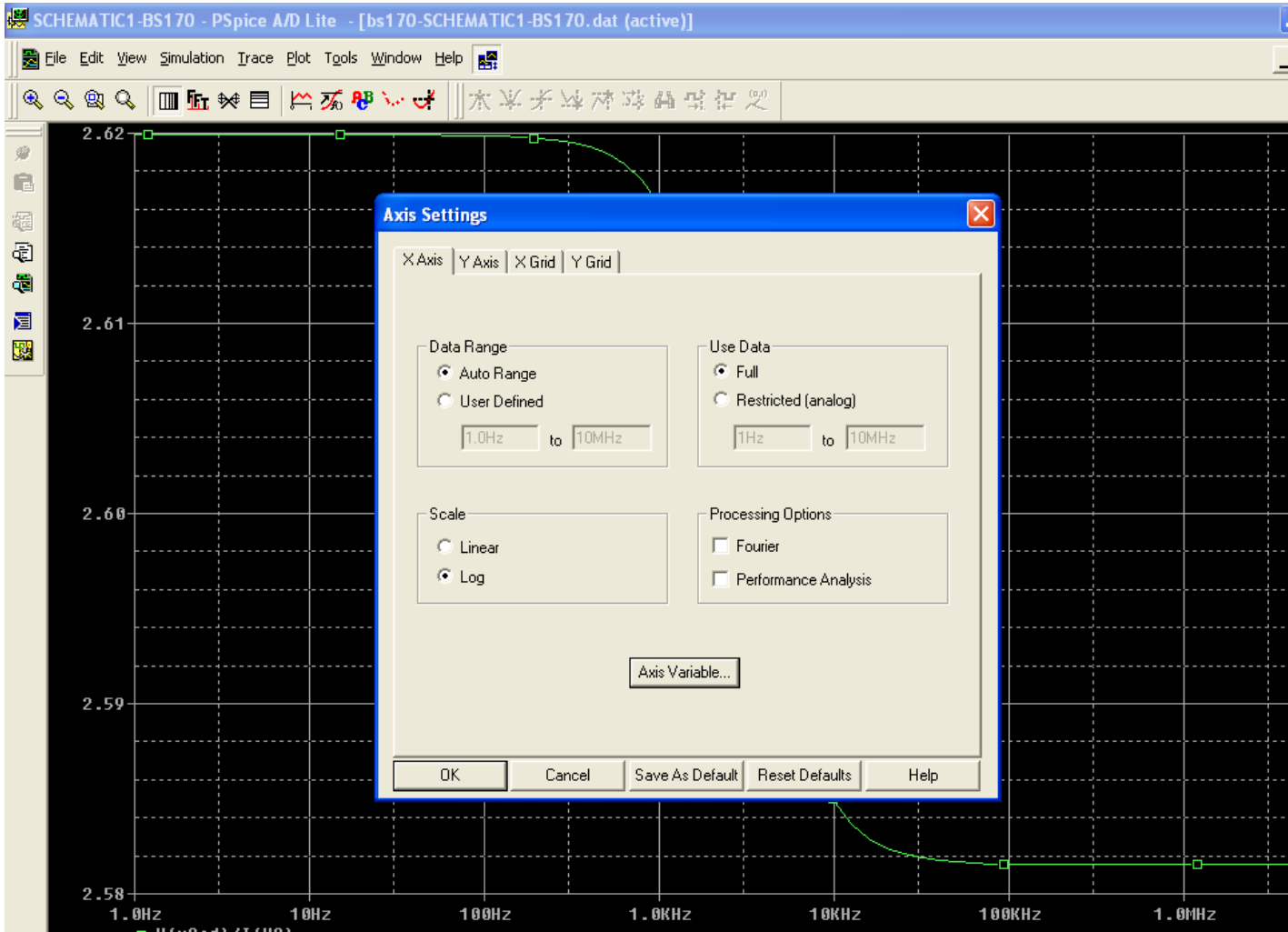
### Plotting to create a VGS x-axis:

Step 1. Create graph of  $V_{out}$  vs  $V_G$ . Double click on the x-axis to get the following:



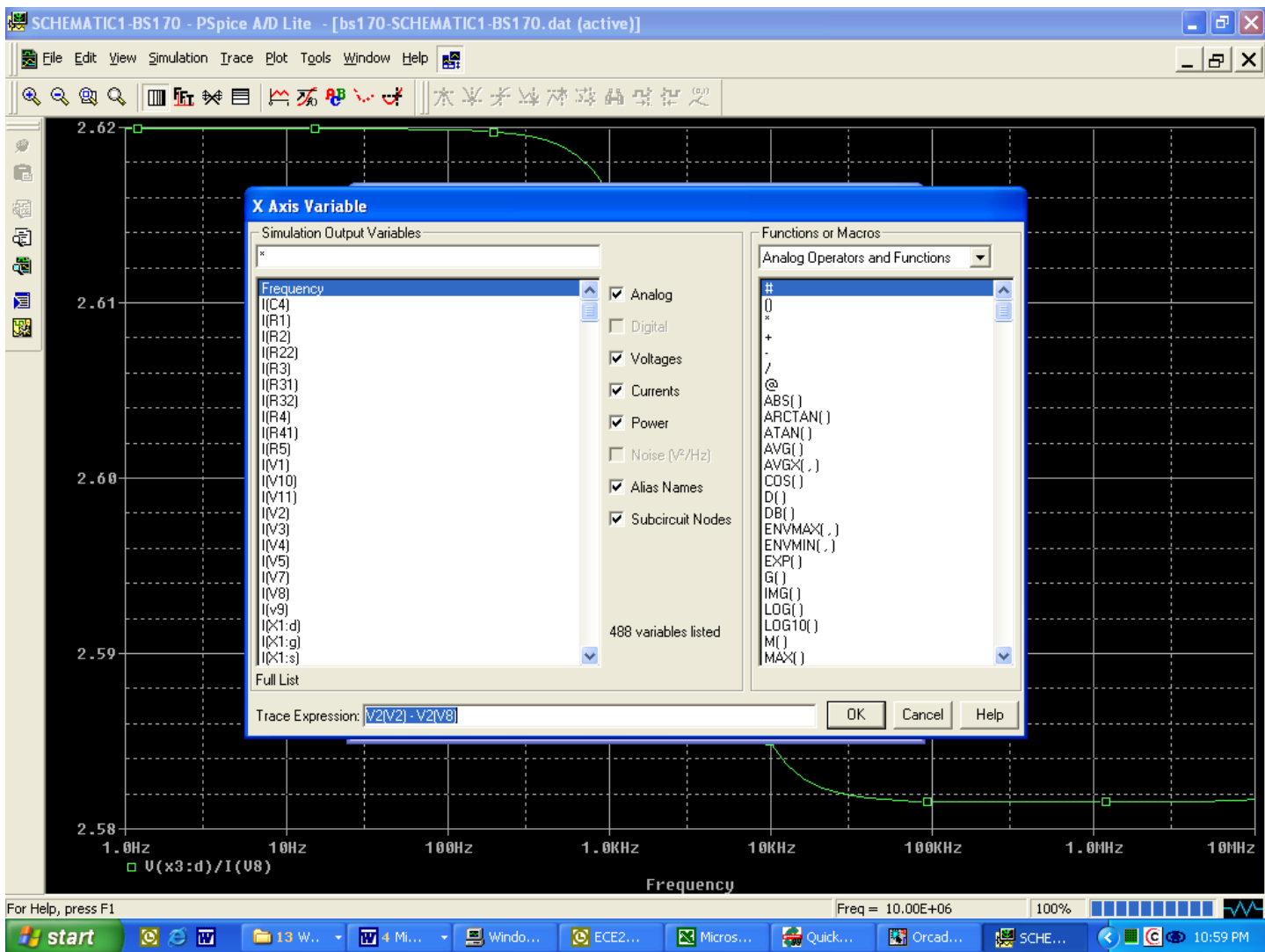Under the x-axis tab => click on axis variable.



Change the Trace Expression to be the VG node – VS node (depends on your circuit).  
Click OK and this changes the axis to be the above expression instead of just VG.