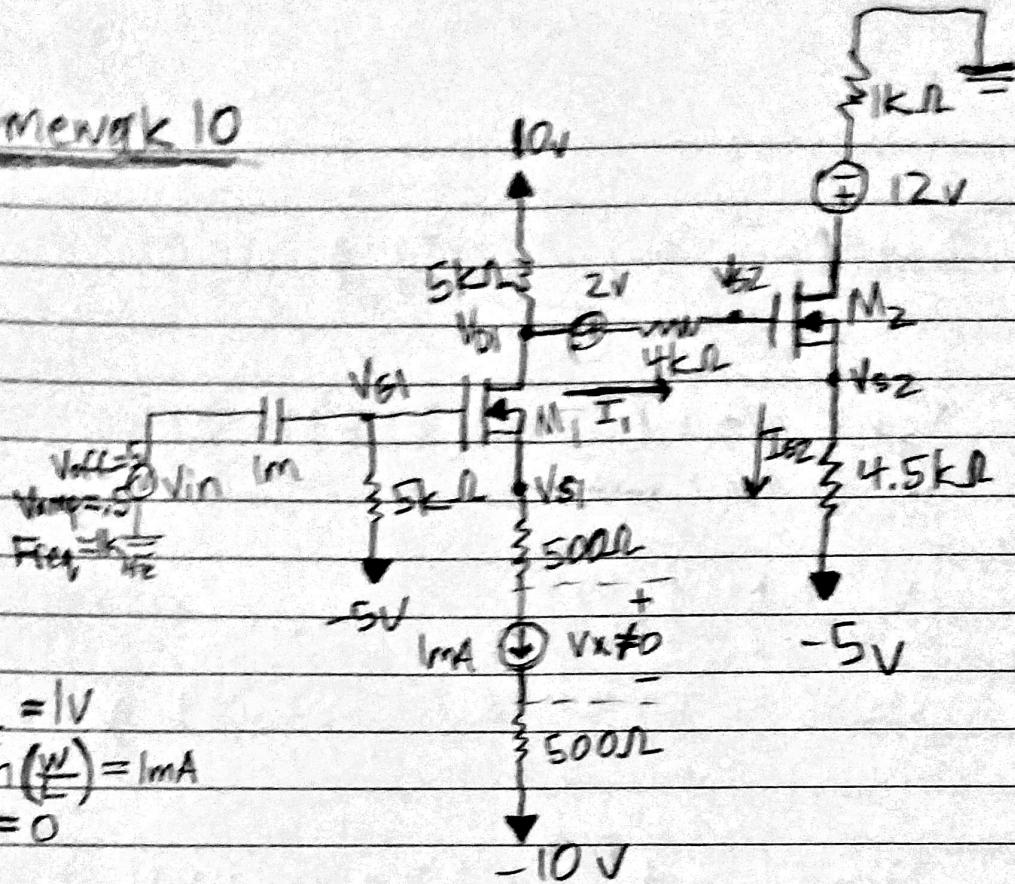


Homework 10

1.



$$V_L = 1V$$

$$k_i \left(\frac{w}{E} \right) = 1mA$$

$$\lambda = 0$$

$$V_{G1} = -5V$$

$$I_m = \frac{1}{2} (1m) (-5 - V_S = 1)^2$$

$$V_{S1} = -7.41$$

$$I_1 = 0$$

$$V_{D1} = 10 - (1m)(5k) = 5V$$

$$V_{G2} = 10 - 5 + 2 = 7V$$

$$I_{S2} = \frac{1}{2} (1m) (7 + 5 - I_{S2}(4.5k) - 1)^2$$

$$500I_{S2} = (11 - I_{S2}(4.5k))^2$$

$$500I_{S2} = 121 - 99000I_{S2} + 20.25M I_{S2}^2$$

$$0 = 121 - 99500I_{S2} + 20.25M I_{S2}^2$$

$$I_{S2} = \frac{99.5kI_{S2} \pm \sqrt{99.5k^2 - 4(20.25M)(121)}}{2(20.25M)}$$



$$I_{S2} = 2.7 \text{ mA}, |2 \text{ mA}|$$

$$V_{S2} = -5 + (2.7 \text{ mA})(4.5 \text{ k}) = 7.15 \text{ V}$$

$$V_{D2} = 1 \text{ k}(2.7 \text{ mA}) - 12 \text{ V} = -9.3$$

$$|V_{DS}| > |V_{GS}| - |V_T|$$

$$|6.45| > |7 - 7.15| - |1| \quad \checkmark \quad -1.15 > 1 \quad X$$

$$V_{S2} = -5 \text{ V} + (2 \text{ mA})(4.5 \text{ k}) = 4 \text{ V}$$

$$V_{D2} = 1 \text{ k}(-2 \text{ mA}) - 12 \text{ V} = -10 \text{ V}$$

$$-9.7 + 10 - 4 > (7 - 4) - 1 \quad +1$$

$$14 > 2 \quad \checkmark \quad 3 > 1 \quad \checkmark$$


Bias point: $V_{GS} = 2.4 \text{ V}$

$$I_D = 1 \text{ mA}$$


2.

$$\frac{V_{S2}}{V_{in}} = (-3)(0.5) = -1.5$$

$$V_{S2\text{ total}} = 4 \pm -1.5$$

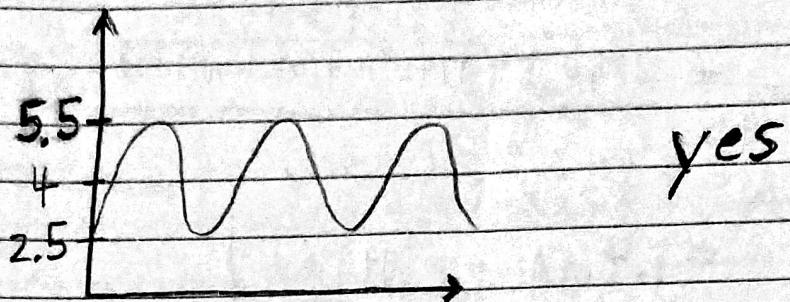

3.

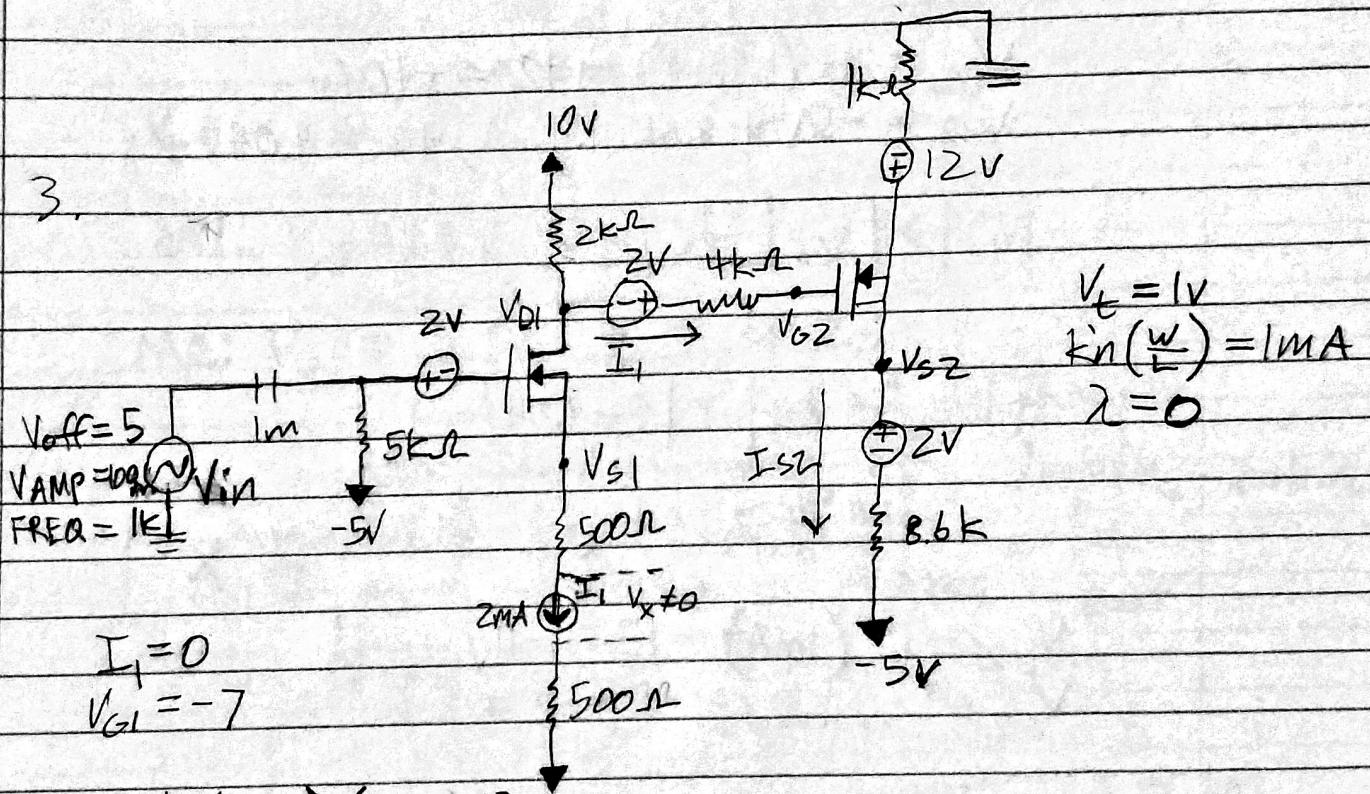

$$ZmA = \frac{1}{2}(1mA)(-7 - V_{S1})^2 - 15V$$

$$q = (-8 - V_{S1})^2$$

$$-10V = V_{S1}$$

$$V_{G2} = 10 - 2k(Zm) + 2 = 8V$$

$$I_{S2} = \frac{1}{2}(1mA)(8 + 5 - (I_{S2})(8.6k) - 2 - 1)$$

$$2kI_{S2} = (10 - I_{S2}(8.6k))^2$$

$$2kI_{S2} = 100 - 172kI_{S2} + 73.96M I_{S2}^2$$

$$0 = 100 - 174kI_{S2} + 73.9M I_{S2}^2$$

$$I_{S2} = \frac{26305.9}{-174k \pm \sqrt{-174k^2 - 4(73.9M)(100)}} \\ = 1.4 \text{ mA} = \boxed{999 \mu\text{A}}$$

$$V_{D2} = 1k(1.4 \text{ mA}) - 12 = -10.6 \text{ V}$$

$$V_{S2} = -5v + 8.6k(1.4 \text{ mA}) + 2 = 9.04 \text{ V}$$

$$|V_{DS}| > |V_{GS}| - |V_t|$$

$$|-10.6 - 9.04| > |8 - 9.04| - 1$$

$$19.64 > .04 \quad \checkmark \quad -1.04 < 1 \quad \times$$

$$V_{D2} = 1k(1 \text{ mA}) - 12 = -11 \text{ V}$$

$$V_{S2} = -5v + 8.6k(1 \text{ mA}) + 2 = 5.6 \text{ V}$$

$$|-11 - 5.6| > |8 - 5.6| - 1 \quad 2.4 > 1$$

$$16.6 > 1.4 \quad \checkmark \quad \checkmark$$

Bias Point:


$$V_{GS1} = 3 \text{ V}$$

$$I_{D1} = 2 \text{ mA}$$

4.

$$\frac{V_{GS}}{V_{IN}} = (-30)(1) = -3V$$

$$V_{S2\text{ total}} = 5.6 \pm -3V$$

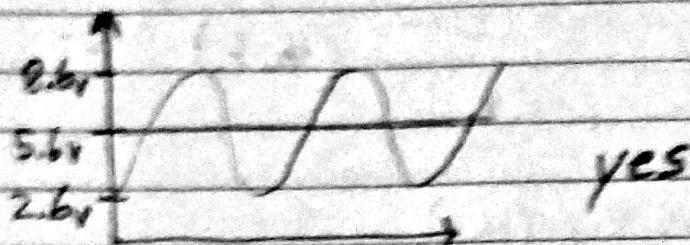


5.

$$V_t = 1V \quad k_n \left(\frac{W}{L} \right) = 2mA \quad \lambda = 0$$

$$M1: V_{GS} = 1.5V, I_D = 0.25mA$$

$$M2: V_{GS} = 13.5V, I_D = 156.25mA$$

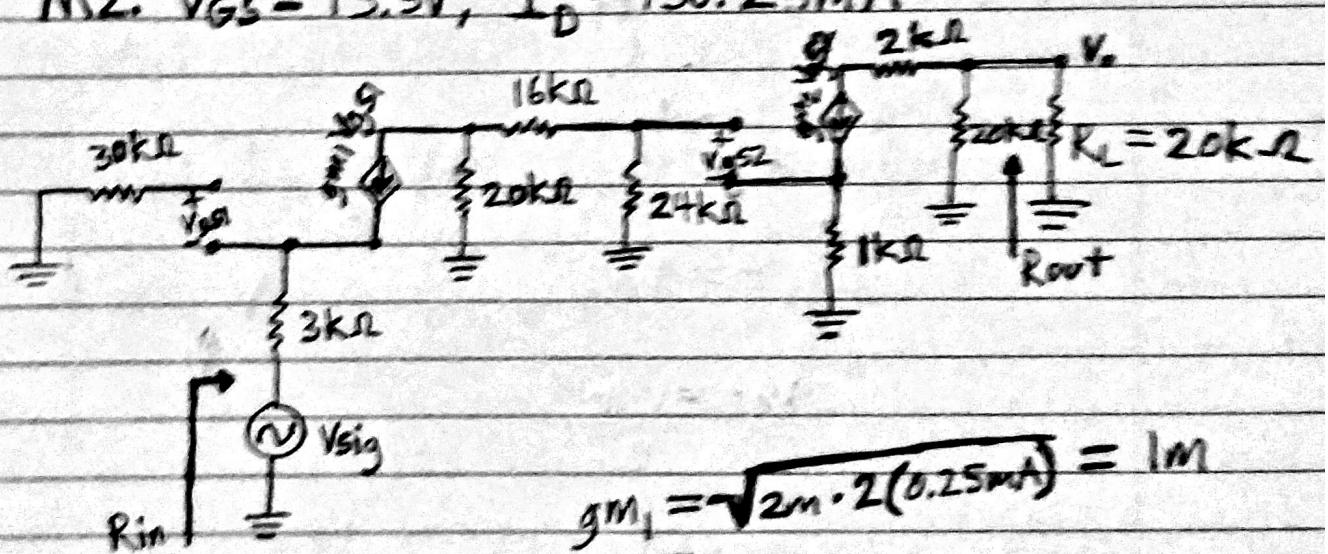

$$g_{m1} = \sqrt{2m \cdot 2(0.25mA)} = 1m$$

$$R_{in} = 3k + \frac{1}{g_{m1}} = 4k\Omega$$

$$R_{out} = 20k\Omega$$



$$V_o = \frac{-gm_2 V_{gs2} (20k\Omega)}{40k\Omega} (20k\Omega)$$

$$V_{gs2} = V_{g2} - V_{s2}$$

$$V_{g2} = \frac{-gm_1 V_{gs1} (20k\Omega)}{60k\Omega} (40k)$$

$$V_{s2} = gm_2 V_{gs2} (1k\Omega)$$

$$V_{gs1} = V_{g1} - V_{s1}$$

$$V_{s1} = gm_1 V_{gs1} (1k\Omega) - V_{sig}$$

$$V_{g1} = 0$$

$$gm_2 = \sqrt{2m \cdot 2(156.25m)} = 25m$$

$$V_{gs1} = -lm V_{gs1} (1k) + V_{sig}$$

$$2V_{gs1} = V_{sig}$$

$$V_{gs1} = \frac{V_{sig}}{2}$$

$$V_{g2} = -lm \left(\frac{V_{sig}}{2} \right) (20k) (40k)$$

$$V_{g2} = -V_{sig} 6.66$$

$$V_{GS2} = 25V_{GS2}$$

$$V_{GS2} = V_{sig} 6.66 - 25V_{GS2}$$

$$V_{GS2} = -2664V_{sig}$$

$$V_o = \frac{-25(-.2664V_{sig})(20k\Omega)}{40k\Omega} = 20k\Omega$$


$$\frac{V_o}{V_{sig}} = -19.2V/V$$

6.

$$V_t = IV, k_n \left(\frac{W}{L}\right) = 2mA, \lambda = 0$$

$$M_1: V_{GS} = 1.5V$$

$$M_2: I_D = 156.25mA$$

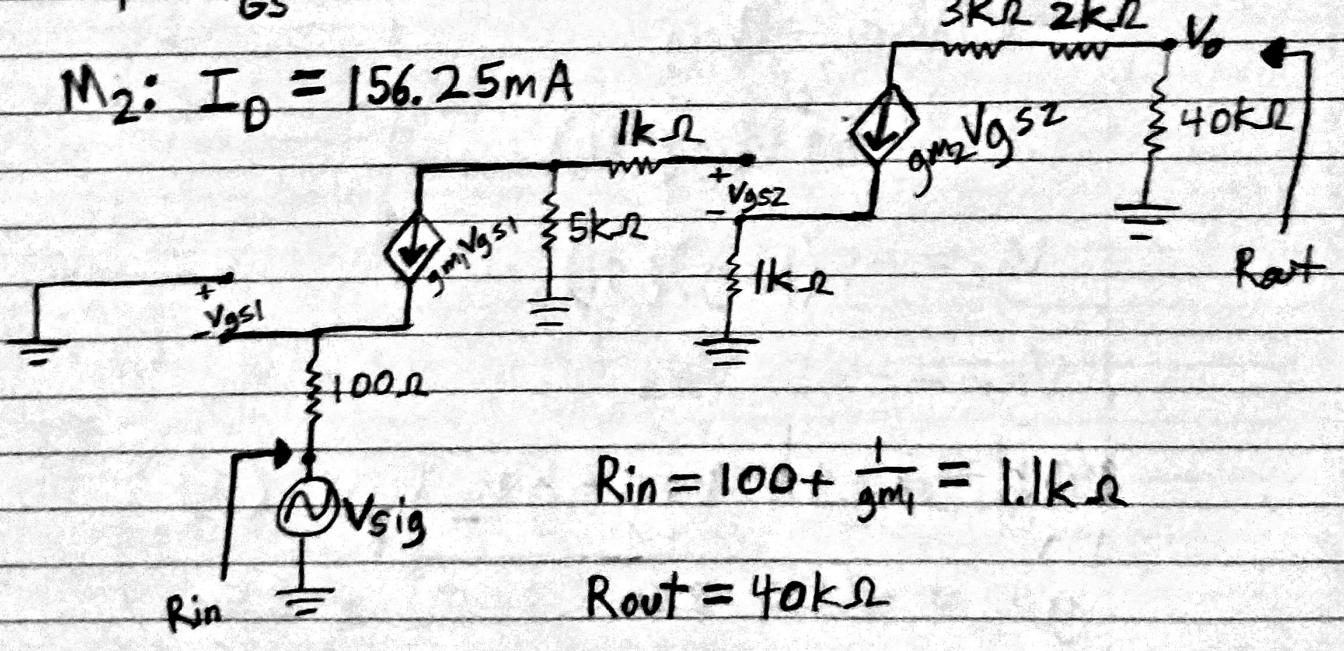

$$R_{in} = 100 + \frac{1}{gm_1} = 1.1k\Omega$$

$$R_{out} = 40k\Omega$$

$$gm_1 = 2mA (1.5 - 1) = 1m$$

$$V_o = -g_{m2} V_{gs2} (5k)$$



$$V_{gs2} = \pm 175 V_{sig}$$

$$V_{gs2} = V_{g2} - V_{o2}$$

$$V_{o2} = g_{m2} V_{gs2} (1k)$$

$$V_{g2} = -g_{m1} V_{gs1} (5k)$$

$$V_{gs1} = V_{g1} - V_{s1}$$

$$V_{s1} = g_{m1} V_{gs1} (100) - V_{sig}$$

$$V_{g1} = 0$$

$$V_{s1} = -100m V_{gs1} - V_{sig}$$

$$V_{gs1} = -100m V_{gs1} + V_{sig}$$

$$I_1 V_{gs1} = V_{sig}$$

$$V_{gs1} = V_{sig} (.91)$$




$$V_{g2} = -5 (V_{sig}) (.91)$$

$$V_{g2} = -4.55 V_{sig}$$

$$V_{gs2} = -4.55 V_{sig} - g_{m2} V_{gs2} (1k)$$

$$g_{m2} = \sqrt{2m \cdot 2 (156.25mA)} = 25m$$

$$V_{gs2} = -4.55 V_{sig} - 25 V_{gs2}$$

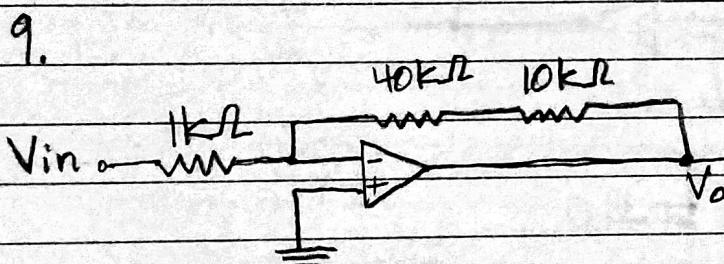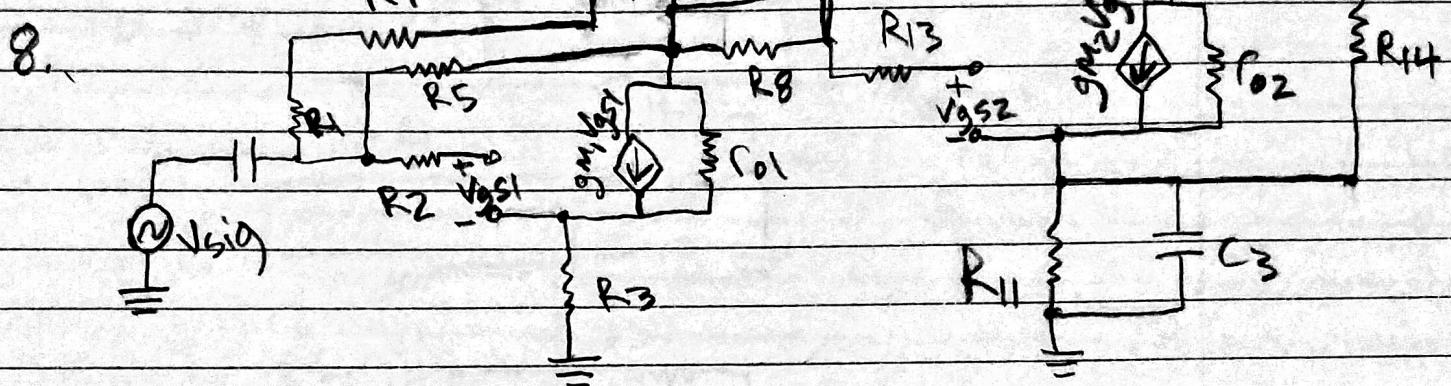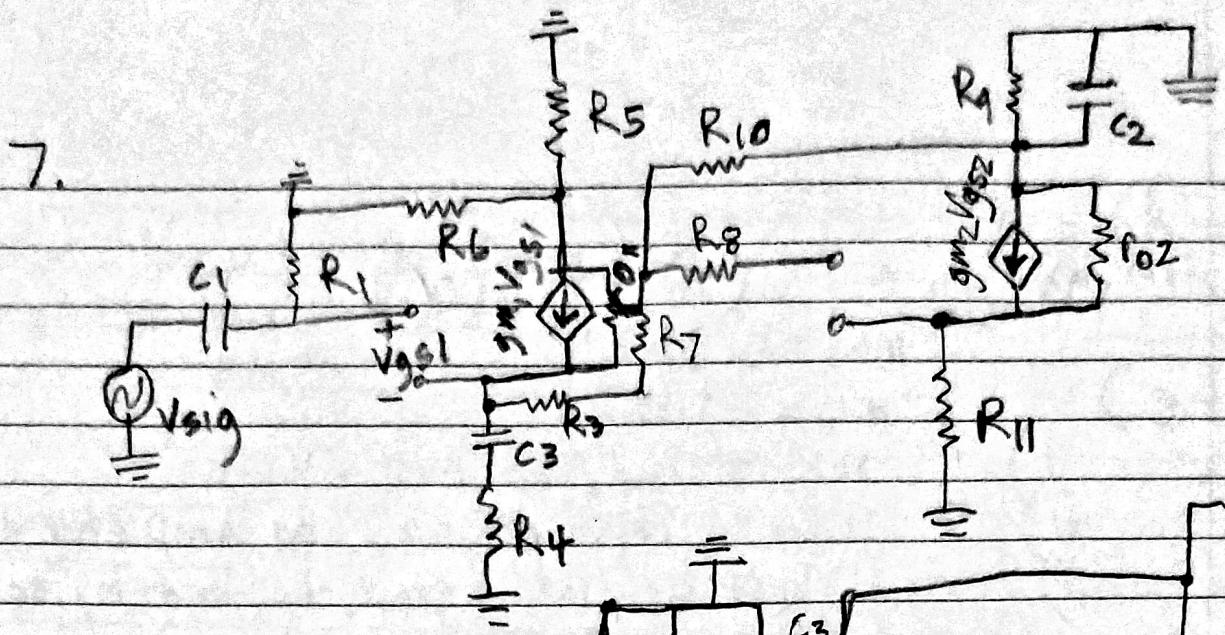

a)

$$\frac{V_o}{V_{in}} = \frac{50k\Omega}{1k\Omega} = -50 \text{ V/V}$$

b)

$$f_c = \frac{5T}{50+1} = \frac{1.5M}{51} = 29,411.76$$

$$f_{max} = \frac{1}{1A} \cdot \frac{1}{2\pi(5)} = 22,281.69$$

c)

$$f_c = \frac{75M}{51} = 1,470,588.235$$

Larger

$$f_{max} = \frac{15}{1A} \cdot \frac{1}{2\pi(5)} = 1477464.83$$

d)

$$V_{\text{total}} = 51(7m) \mp 50(.1)$$

$$\text{MAX} = 5.357$$

$$\text{min} = -4.643$$

e)


i)
ii)
iii)

Highest AV, so Amp 6484


Highest input offset, so Amp 6484

Highest slew rate \Rightarrow Gain-Bandwidth, so Amp 6154

f)

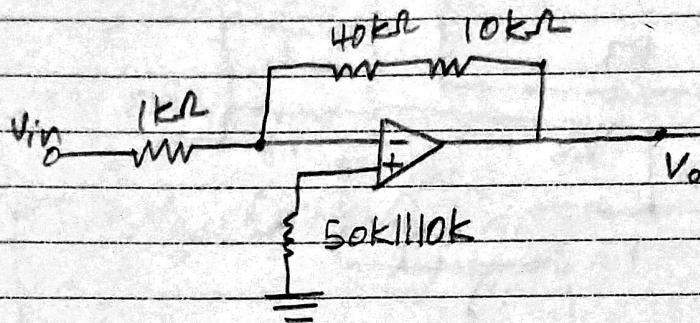

10.

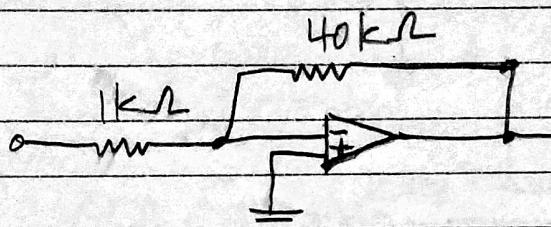

a) $\frac{V_o}{V_{\text{in}}} = \frac{40k}{1k} = 40$

b)

$$f_c = \frac{1M}{4\pi} = 24,390.24$$

$$f_{\text{max}} = \frac{0.5}{1\mu} \cdot \frac{1}{2\pi(4)} = \boxed{19,844.37}$$

c)

$$f_c = \frac{1.5M}{1\mu} \cdot \frac{1}{2\pi(4)} = 5.97 \cdot 10^{10}$$

$$f_{\text{max}} = \frac{1}{1\mu} \cdot \frac{1}{2\pi(4)} = 3,978.87 \text{ lower}$$

d) $V_{o+total} = 41(7m) \mp 40(.1)$

Max = 4.287

Min = -3.713

e)

- i) Amp 6380
- ii) Amp 6570
- iii) Amp 6230

f)

