

1. The table below lists different cases for an NMOS transistor with $V_t=1V$. In each case the voltages at the source, gate, and drain (relative to the circuit ground) are specified. You are required to complete the table entries. Note that V_{ov} is called the overdrive voltage and is equal to $(|V_{GS}|-|V_t|)$.

| V_S | V_G | V_D | $ V_{GS} $ | $ V_{OV} $ | $ V_{DS} $ | Region of Operation |
|-------|-------|-------|------------|------------|------------|---------------------|
| +1.0 | +1.0 | +2.0 | | | | |
| +1.0 | +2.5 | +1.5 | | | | |
| 0 | +2.5 | +1.0 | | | | |
| -1.0 | 0 | +1.0 | | | | |


2. The table below lists different cases for a PMOS transistor with $V_t=-1V$. In each case the voltages at the source, gate, and drain (relative to the circuit ground) are specified. You are required to complete the table entries. Note that V_{ov} is called the overdrive voltage and is equal to $(|V_{GS}|-|V_t|)$.

| V_S | V_G | V_D | $ V_{GS} $ | $ V_{OV} $ | $ V_{DS} $ | Region of Operation |
|-------|-------|-------|------------|------------|------------|---------------------|
| +2.0 | +2.0 | 0 | | | | |
| +2.0 | 0 | 0 | | | | |
| +2.0 | 0 | +1.5 | | | | |

3. Write in your own words the procedure to solve a circuit containing a MosFet transistor for DC currents and voltages.
4. Explain the differences between an NMOS transistor and a PMOS transistor.

5. In the circuits below, transistors are characterized by $|V_t|=2\text{V}$ and $k_n'(W/L)=1\text{mA/V}^2$, and $\lambda=0$.

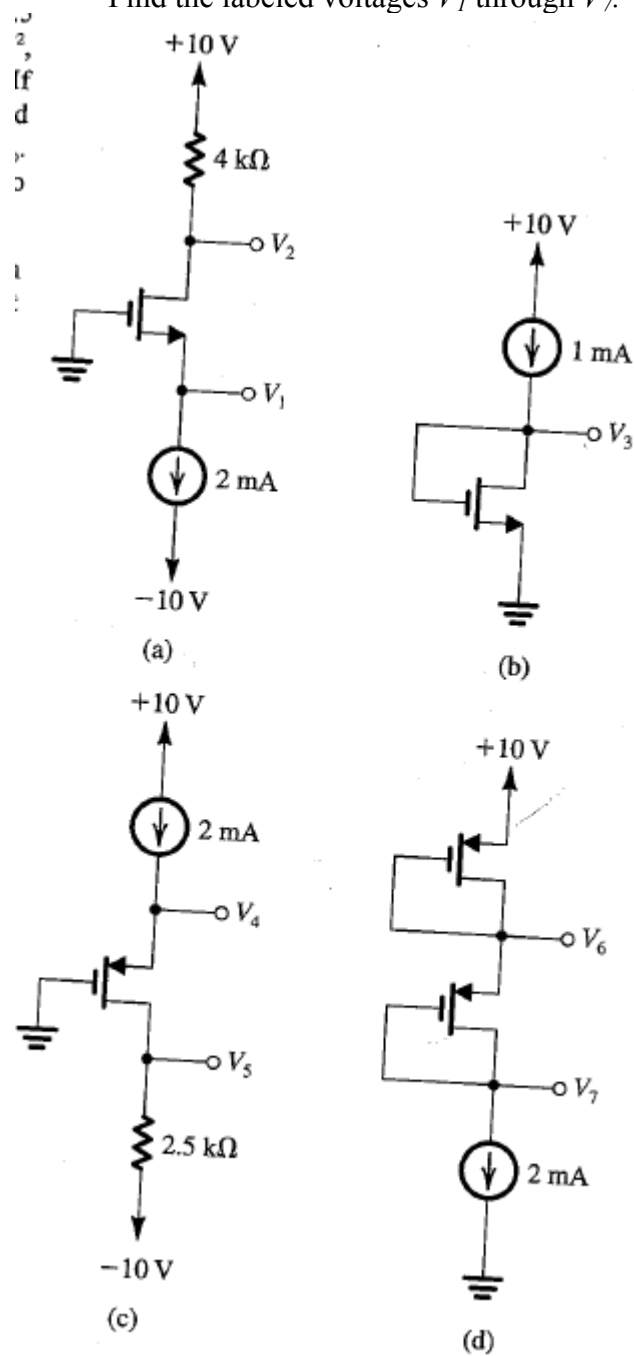- Find the labeled voltages V_1 through V_7 .



6. Use: $V_t=2V$
 $k_n'(W/L)=4mA/V^2$
 $\lambda=0$

For DC analysis, assume that the capacitors act as open. Assume saturation.


(a) Solve for the DC currents:

- I_1
- I_D
- I_S

(b) Solve for the DC voltages:


- V_G
- V_S
- V_o

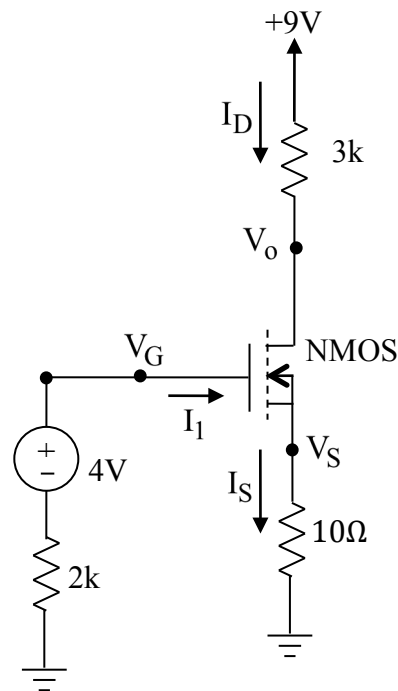(c) Prove or disprove the transistor is saturated.



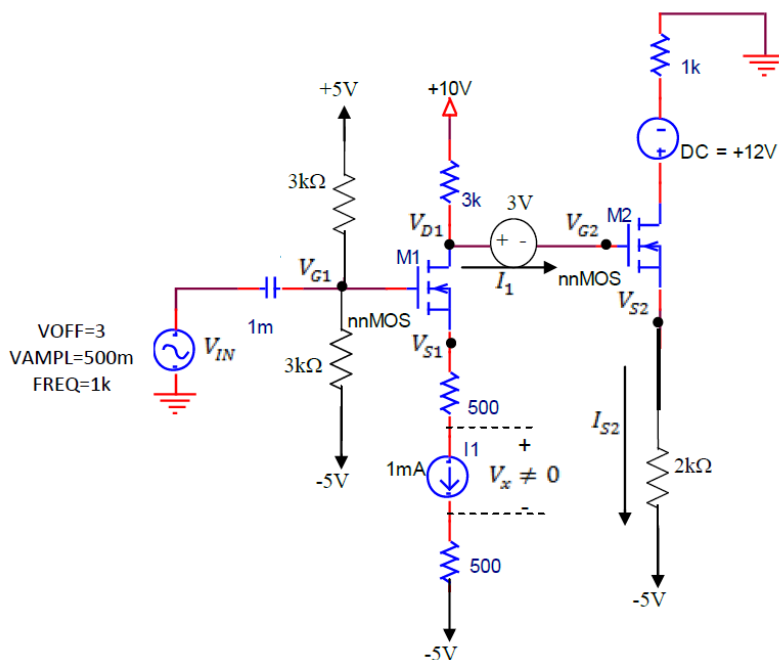7. Use: $V_t=2V$, $k_n'(W/L)=2mA/V^2$, $\lambda=0$. For DC analysis, assume that the capacitors act as an open. The current source is not ideal and has a voltage drop across it. Find:

- $I_1, I_{S2}, V_{G2}, V_{S2}, V_{S1}$
- Verify that transistor M1 is saturated




8. Use: $V_t = 1V$

$$k_n'(W/L) = 2A/V^2$$

$\lambda = 0$ for all transistors

The 4A current source is not ideal and may have a voltage drop across it.

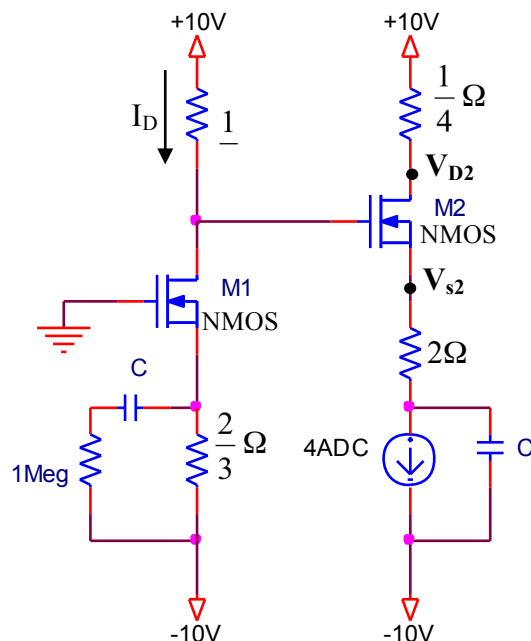For DC analysis, assume that the capacitors act as open.



Solve the circuit for the **DC** values:

- The Q-point for transistor M2
- V_{s2}
- I_D
- V_{D2}
- Verify that the transistor M2 is saturated.

9. Use: $V_t = 1V$


$$k_n'(W/L) = 2mA/V^2$$

$\lambda = 0$ for all transistors

The 1mA current source is not ideal and may have a voltage drop across it.

Solve the circuit for the **DC** values:

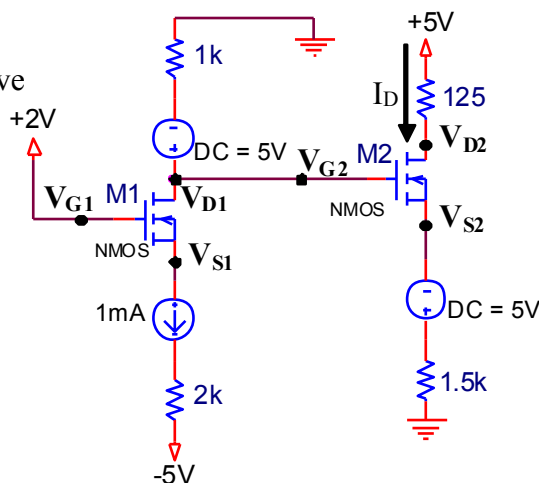- The Q-point for transistor M1
- V_{s1}
- I_D
- V_{D2}
- Verify that the transistor M2 is saturated.



10. Let $V_t = 2V$, $k_n'(W/L) = 180\mu A/V^2$. Assume $I_D = I_S = 10mA$, and $\lambda = 0$.

- Draw the small-signal equivalent circuit using the hybrid- π model and by assuming all capacitors become shorts. Remember to remove all DC sources when drawing the AC. V_{in} is an AC signal.
- Calculate the value for g_m .

