


1

8.

- a) The nominal value of  $B$  is about 126  
 b) The value of  $R_{\text{Collector}}$  is about  $3500\Omega$ . or is it  $87\Omega$ ?  
 c) As  $RC$  increases,  $B$  lowers, causing the transistor to fall into a saturation state.  
 d) For  $RC$  value  $1750\Omega$ ,  $I_C = 650\mu\text{A}$

9.

a)

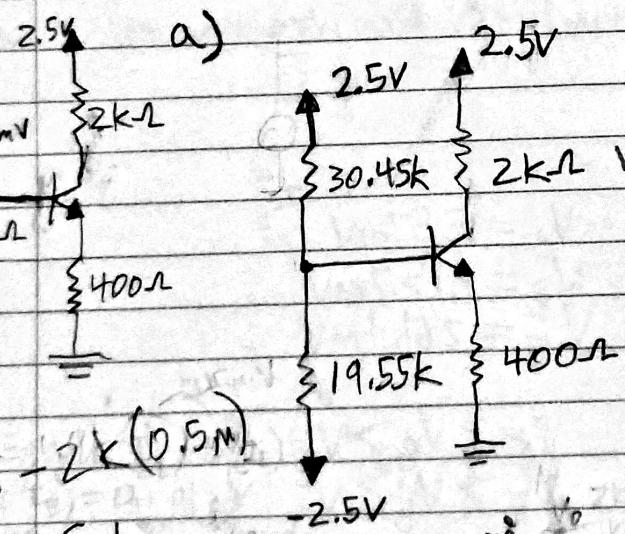

$$I_B = 5.194\mu\text{A} \quad I_C = 0.5\text{mA}$$

$$V_{BE} = .778 \quad \beta = 125$$

$$V_{Th} = \frac{2.5(19.55k) - 2.5(30.45k)}{19.55k + 30.45k}$$


$$V_{Th} = -545\text{mV}$$

$$R_{Th} = 11.9\text{k}\Omega$$

$$V_C = 2.5 - 2k(0.5\text{m}) = 1.5\text{V}$$

$$r_T = \frac{25\text{mV}}{5.194\mu\text{A}} = 4.83\text{k}\Omega$$
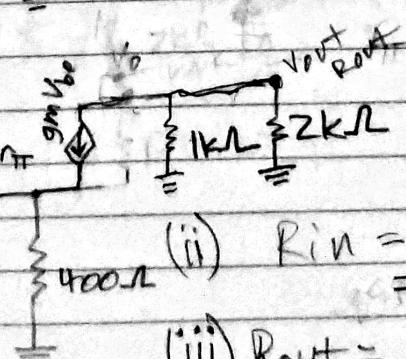
$$r_T = \frac{\beta}{483} = 26\text{mV}$$



$$(i) \quad V_o = 2.5 - 2k(0.5\text{m}) = 1.5\text{V}$$

$$(ii) \quad R_{in} = 11.9\text{k}\Omega \parallel (r_T + 400(\beta+1)) = 9.7\text{k}\Omega$$

$$(iii) \quad R_{out} = 2\text{k}\Omega$$

b)

iii)

Values compared

d)

ii)

C<sub>1</sub> effects the starting value for the bandwidth of the circuit. The higher the frequency the longer it takes to reach maximum value.


iii) Trace where -3 dB is less than 20 Hz, which I think is 100m.

10.

b) The peak value is reached a little faster but it takes longer to fall.

c) Any value with a starting value less than 20 Hz, so the 1pF or 1nF would work just fine

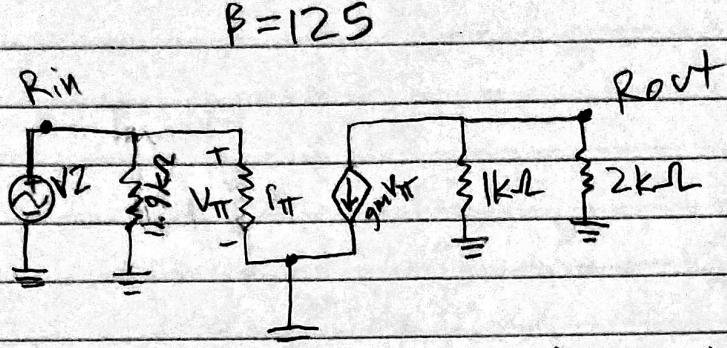g) The gain is much larger than 1.5V. The capacitors are blocking the DC effect on the biasing of the circuit.



$$\beta = 125$$

$$r_{TT} = \frac{25mV}{5.156mA} = 4848\Omega$$

$$V_{TT} = .778$$

$$R_{in} = 11.9k\Omega \parallel r_{TT} = 3445\Omega$$


$$R_{out} = 2k\Omega$$

$$g_m = \frac{\beta}{4848} = 26m$$

$$\frac{V_o}{V_2} = \left( \frac{(26m)(.778)1k\Omega}{3k} \right) 2k\Omega$$

$$= 17.3 V/V$$


9bi

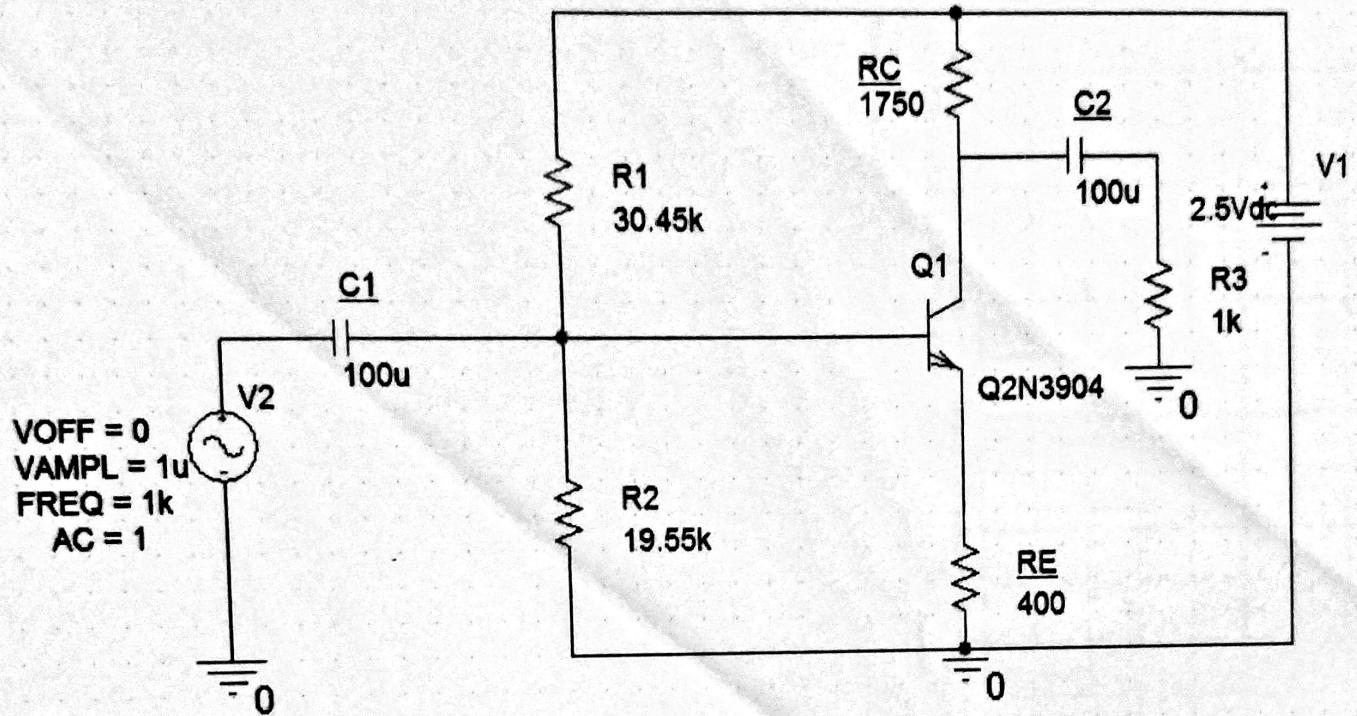

2/29/2016

9b ii

Printing Photo

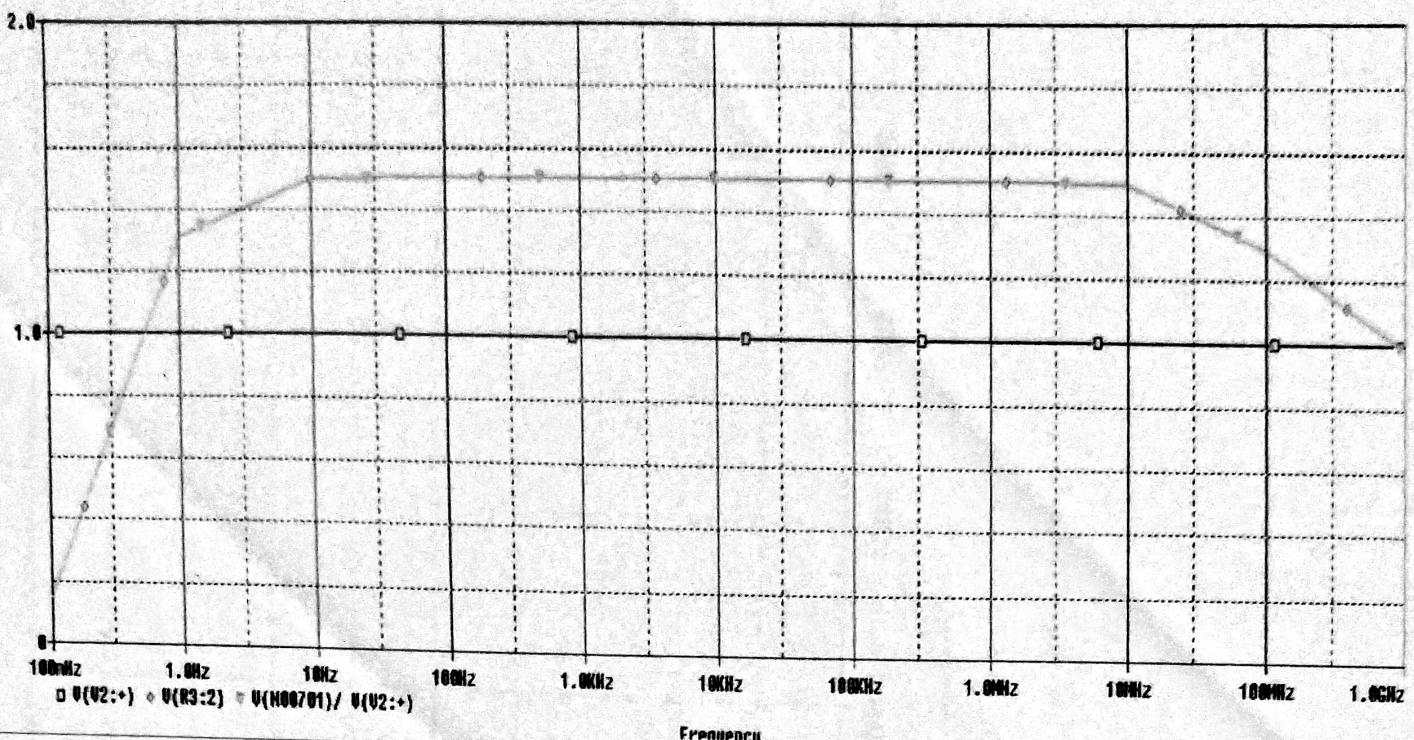


Edited at [LumaPic.com](http://LumaPic.com)

2/29/2016

qbiv

Printing Photo

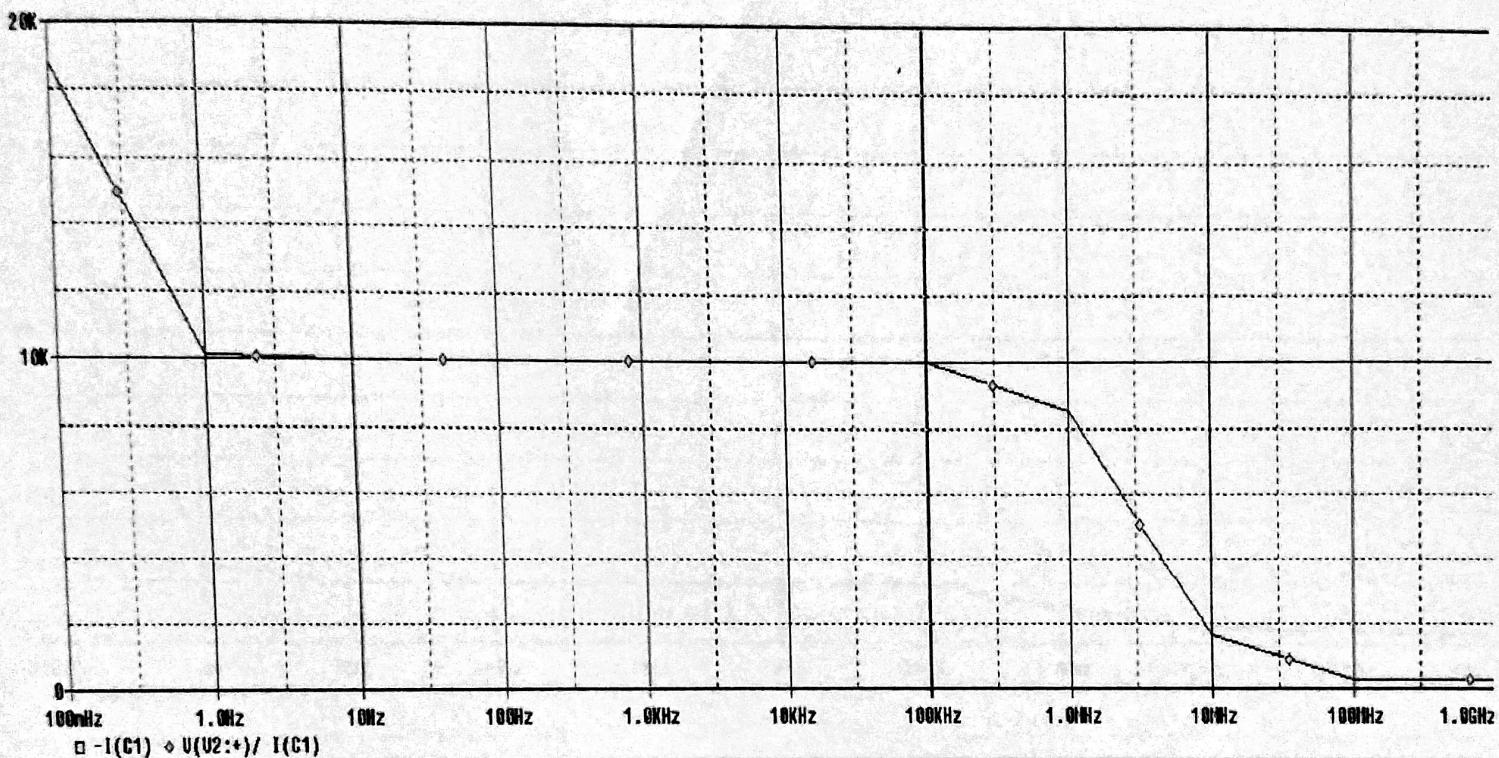


Edited at [LunaPic.com](#)

$R_{in} = 10k$  so that is right compared to  
hand analysis.

229/2016

9C

Printing Photo

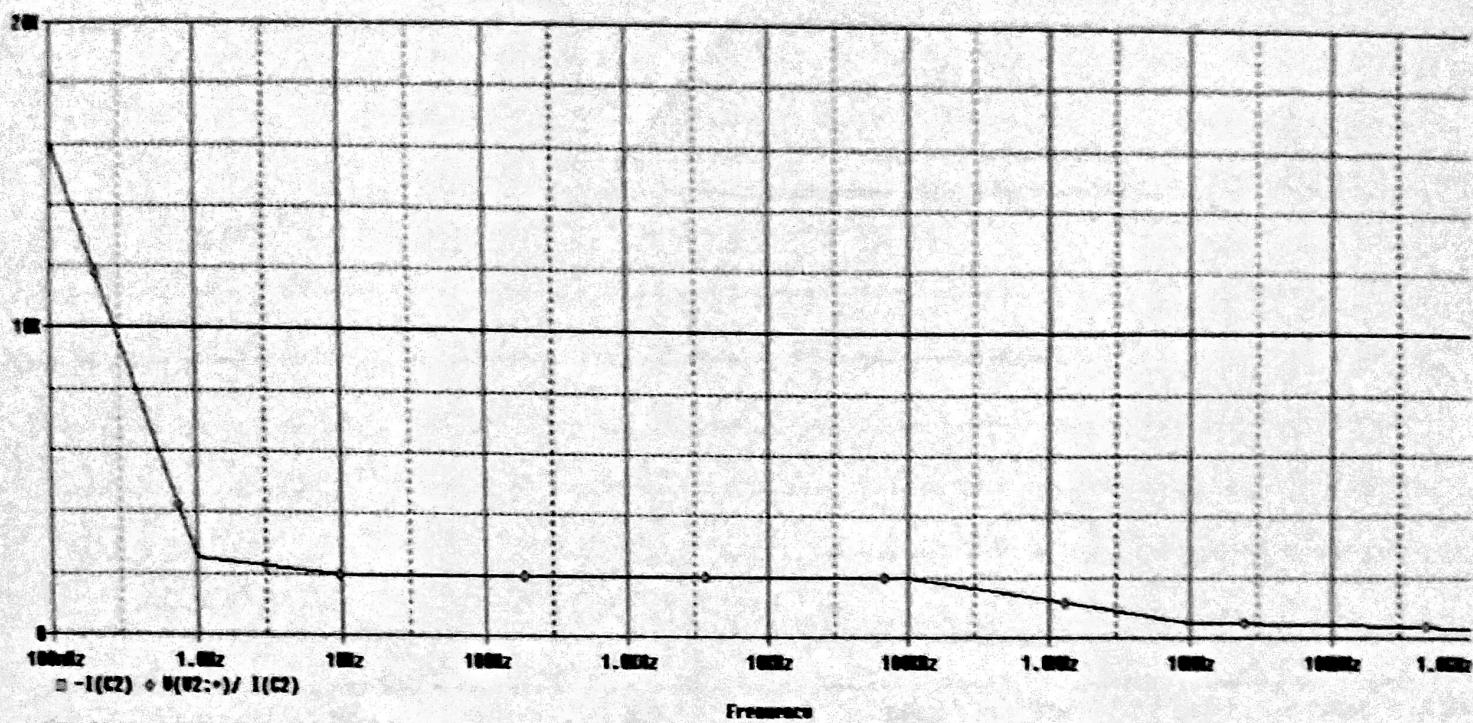


Edited at [LunaPic.com](#)

$R_{out} \approx 2k$  which is what I had in  
hand analysis

2/29/2016

9di

Printing Photo

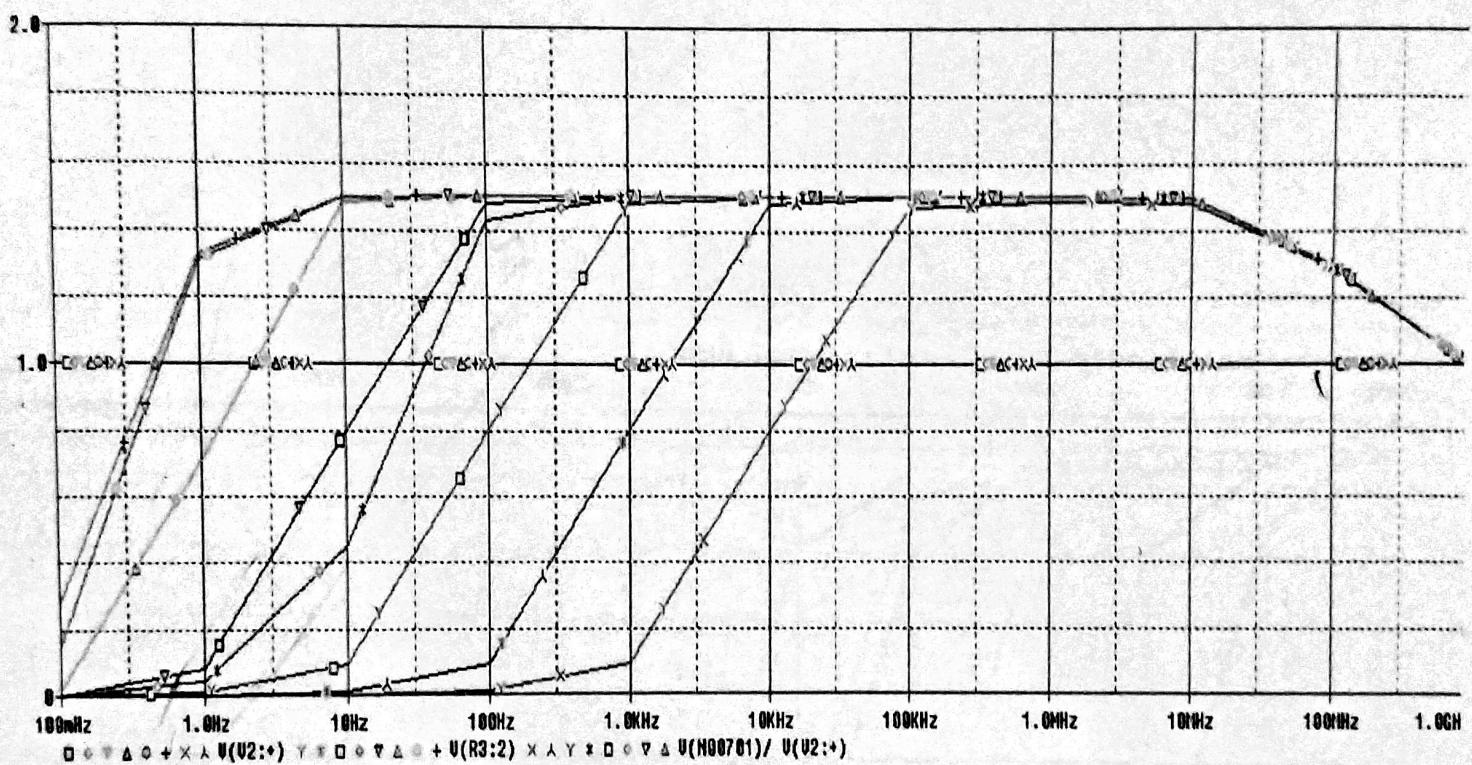


Edited at [LunaPic.com](#)

2/29/2016

10a

Printing Photo

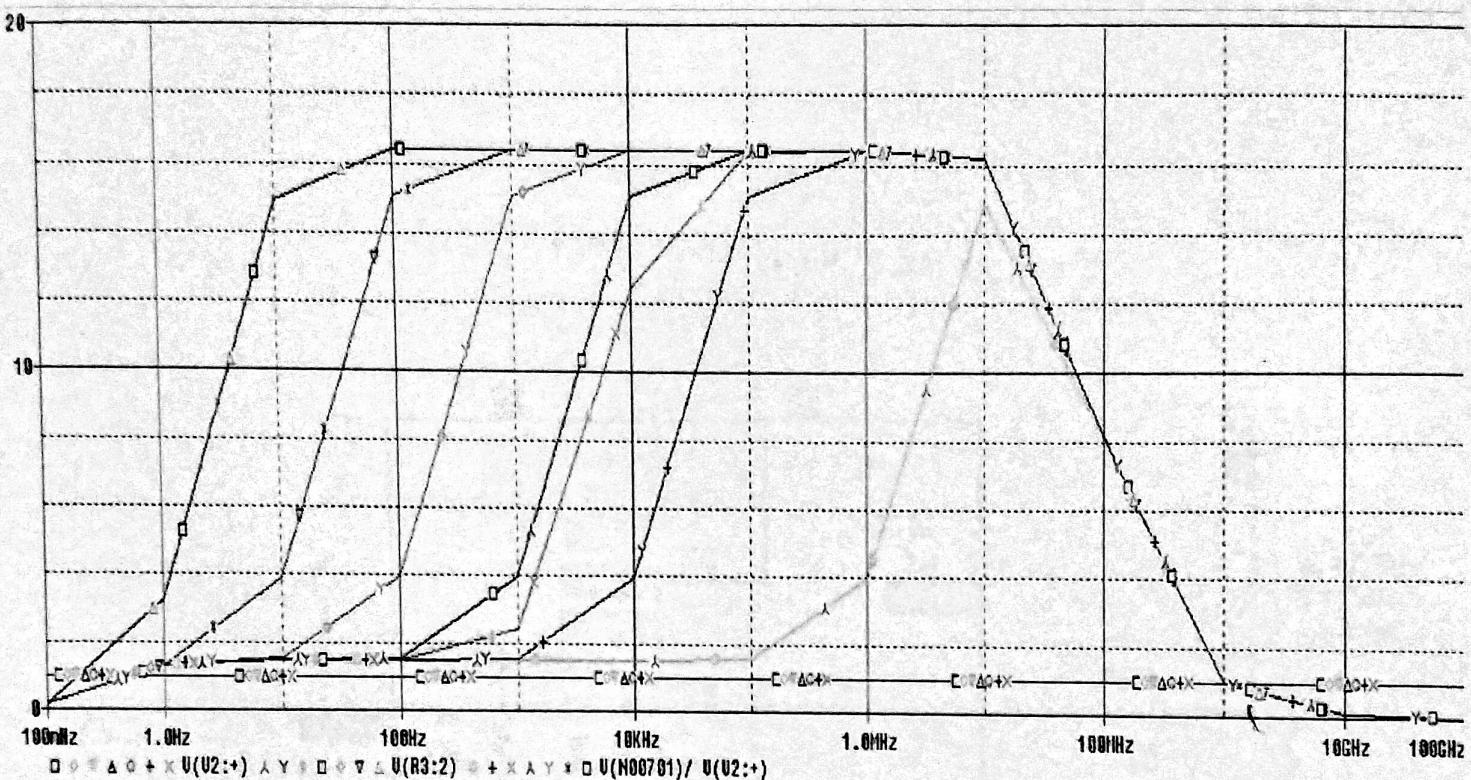


Edited at [LunaPic.com](http://LunaPic.com)


2/29/2016

Printing Photo

10e

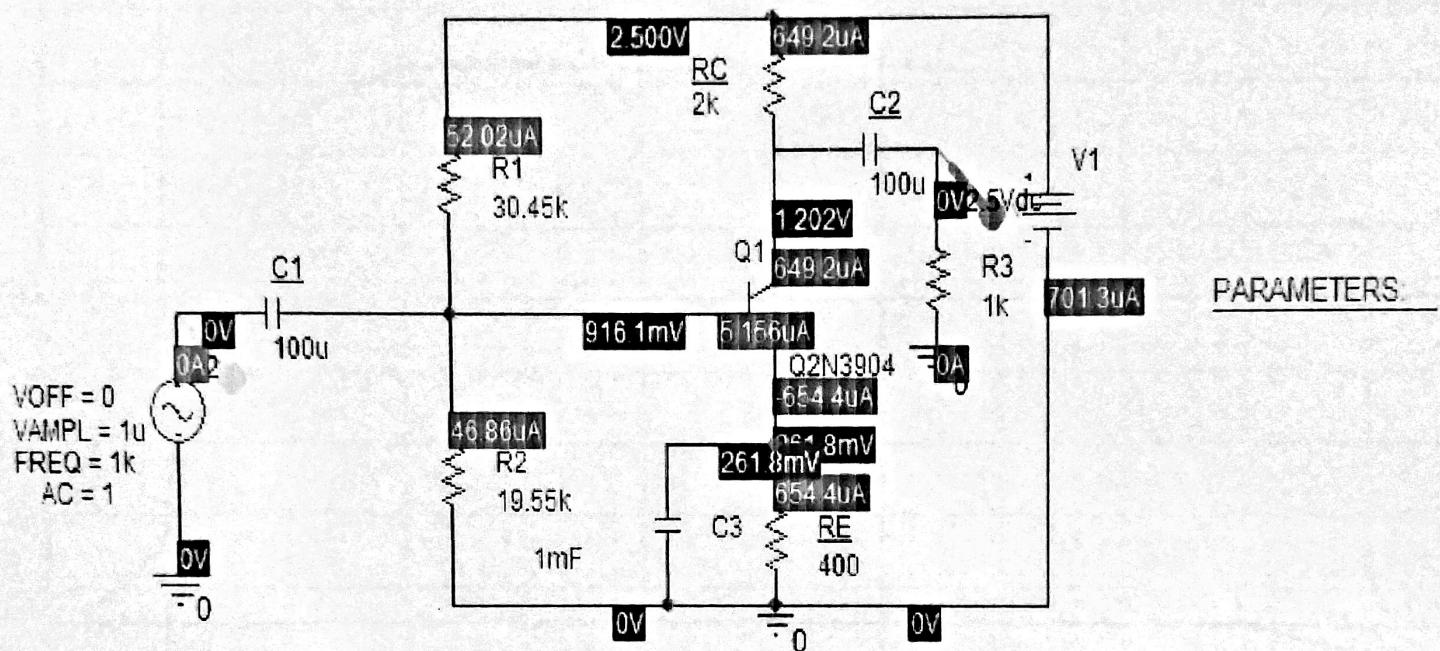

Valves are the same

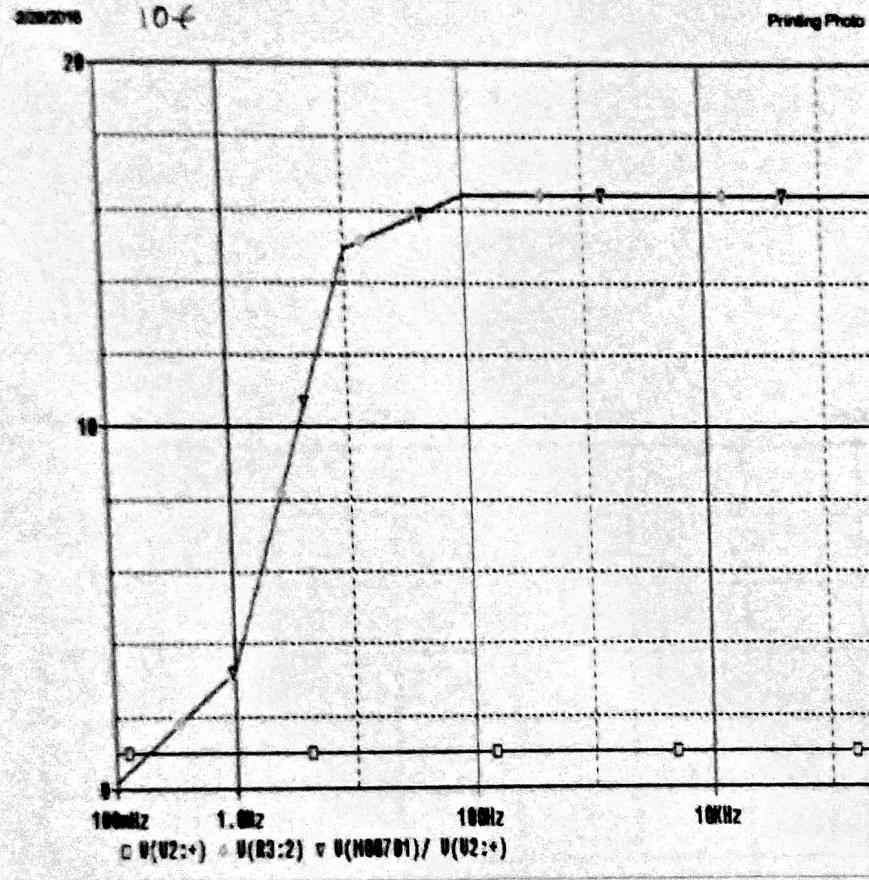


Edited at [LunaPic.com](#)

2/29/2016

10Hz

Printing Photo

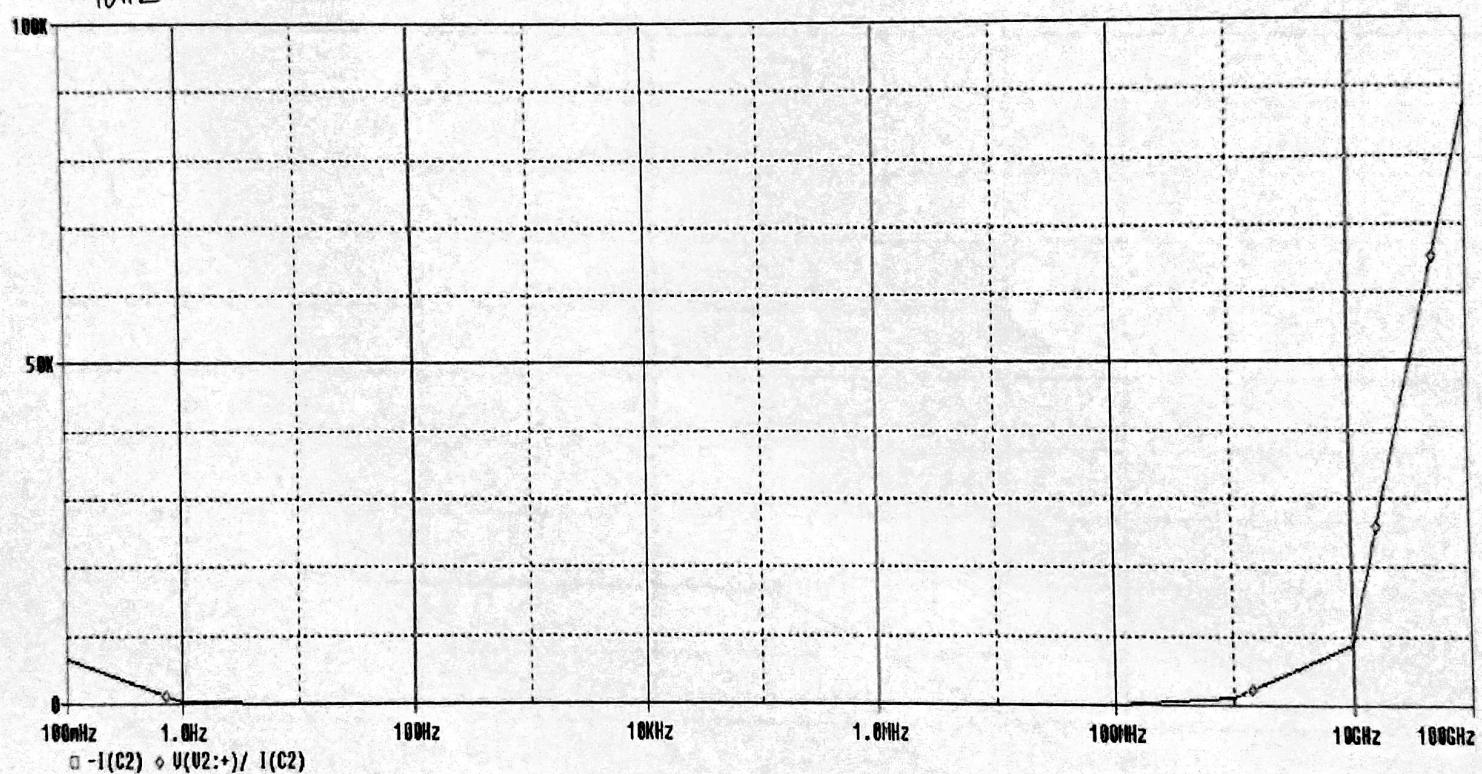


Edited at [LunaPic.com](#)

2/29/2016


10h 1

Printing Photo

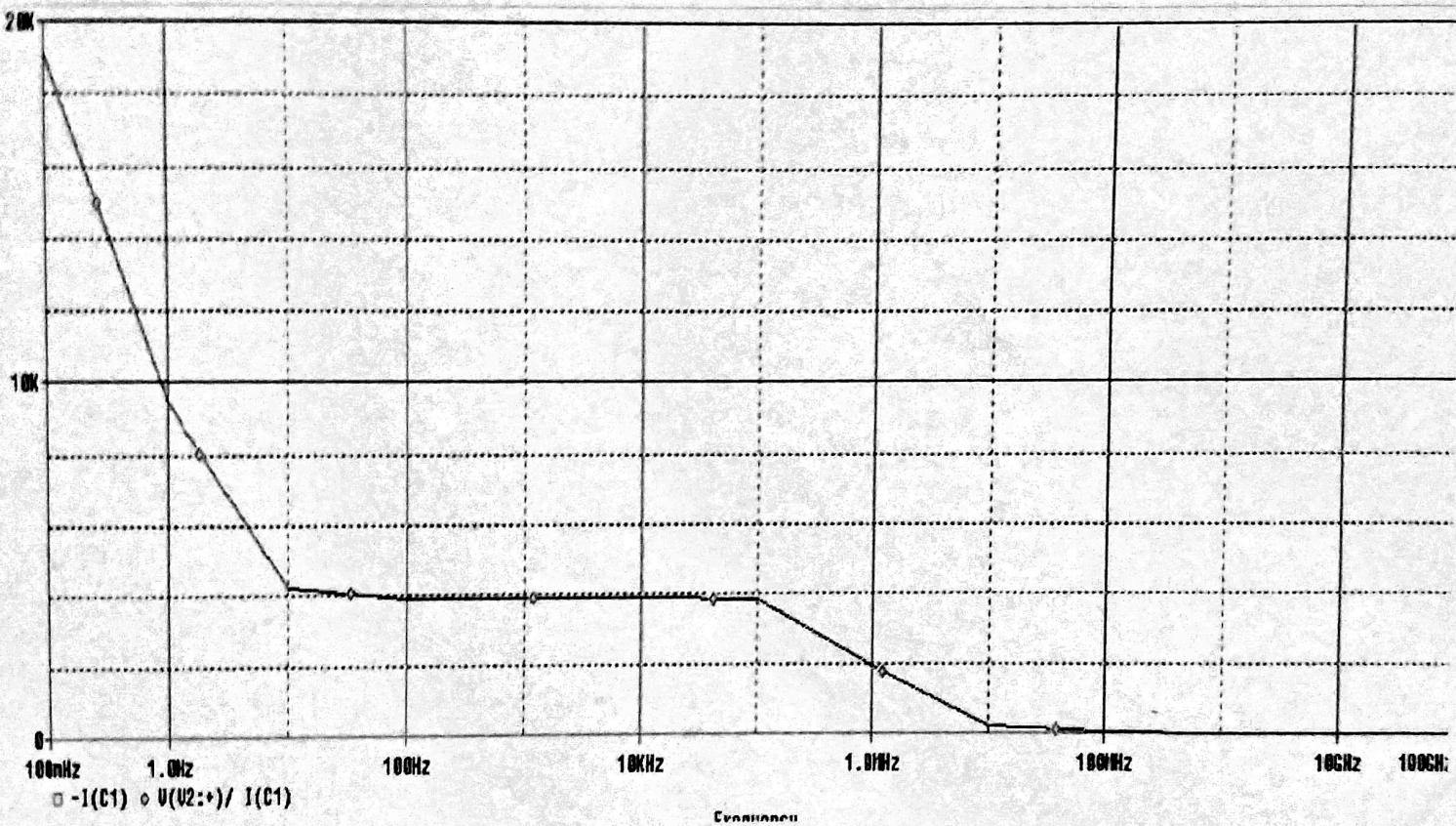


Edited at [LunaPic.com](#)

Homework #6

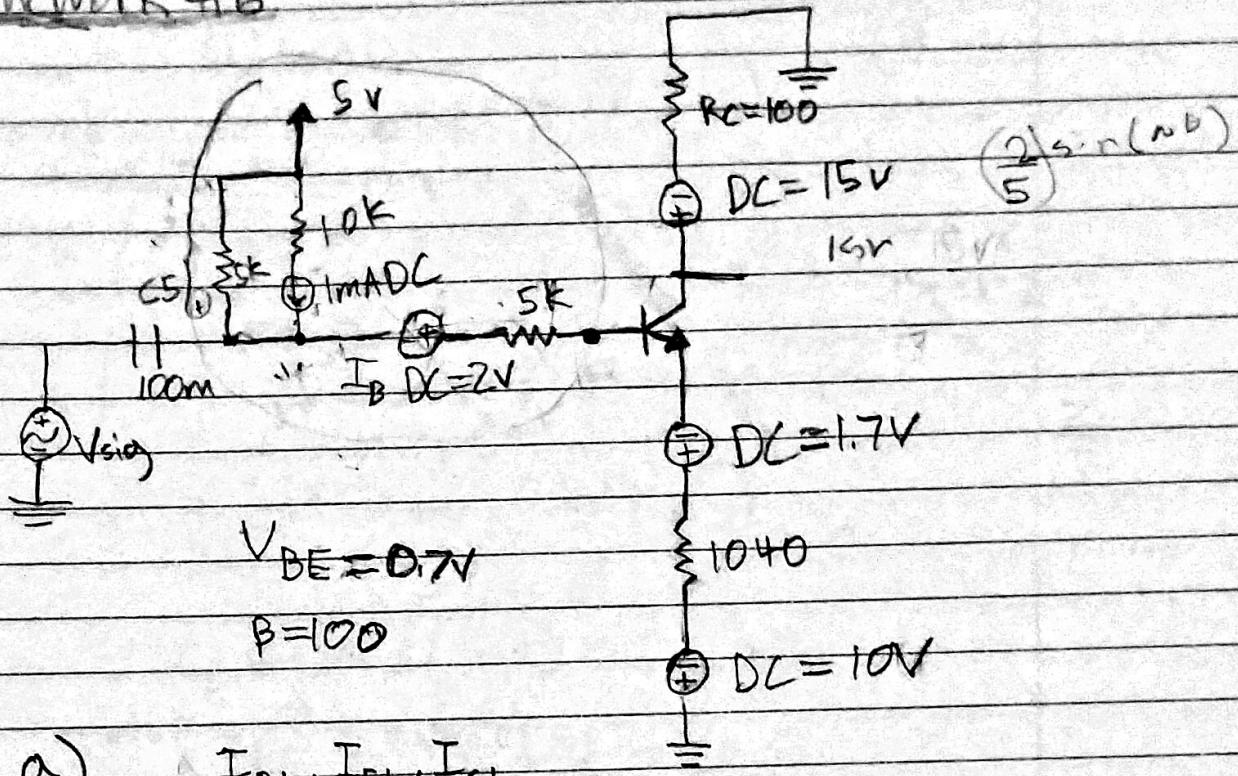

a)

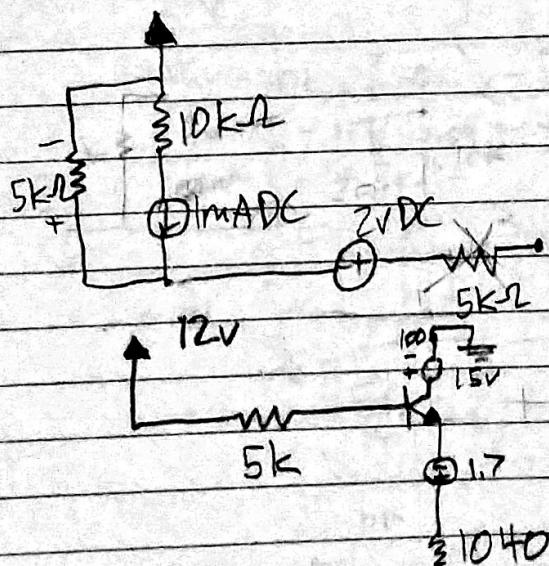

$$V_{Th} = 5 + 5k(I_{mA}) + 2 = 12\text{V}$$

$$R_{Th} = 10k\Omega$$

$$12 - 5k(I_B) - 7 + 1.7 - 1040(I_E) + 10 = 0$$

$$I_E \left( -\frac{5k}{1040} - 1040 \right) = -23$$

$$V_B = 12 - 5k(2\text{mA}) = 10\text{V}$$

$$I_E = 20.2\text{mA}$$

$$V_E = 9.3\text{V}$$

$$I_B = \frac{20.2\text{mA}}{101} = .2\text{mA}$$

$$V_C = -100(20\text{mA}) + 15 = 13\text{V}$$

$$I_C = 20\text{mA} \cdot 100 = 20\text{mA}$$

b)

$$V_C \geq V_B > V_E$$

$$13 \geq 10 > 9.3 \quad \checkmark$$

Active

2.

a) gain =  $\frac{V_C}{V_{sig}} = -5V_v$

$$V_C = 13V$$

$$15 - 13 = 2V_v$$

$$V_{sig\ Max} = \frac{2}{5} = 0.4V$$

b)  $-RC(20mA) + 15 = 10$

$$-RC(20mA) = -5$$

$$RC \leq 250\Omega$$


3.

$$V_{be} = 0.7 \quad \beta = 100$$

a)

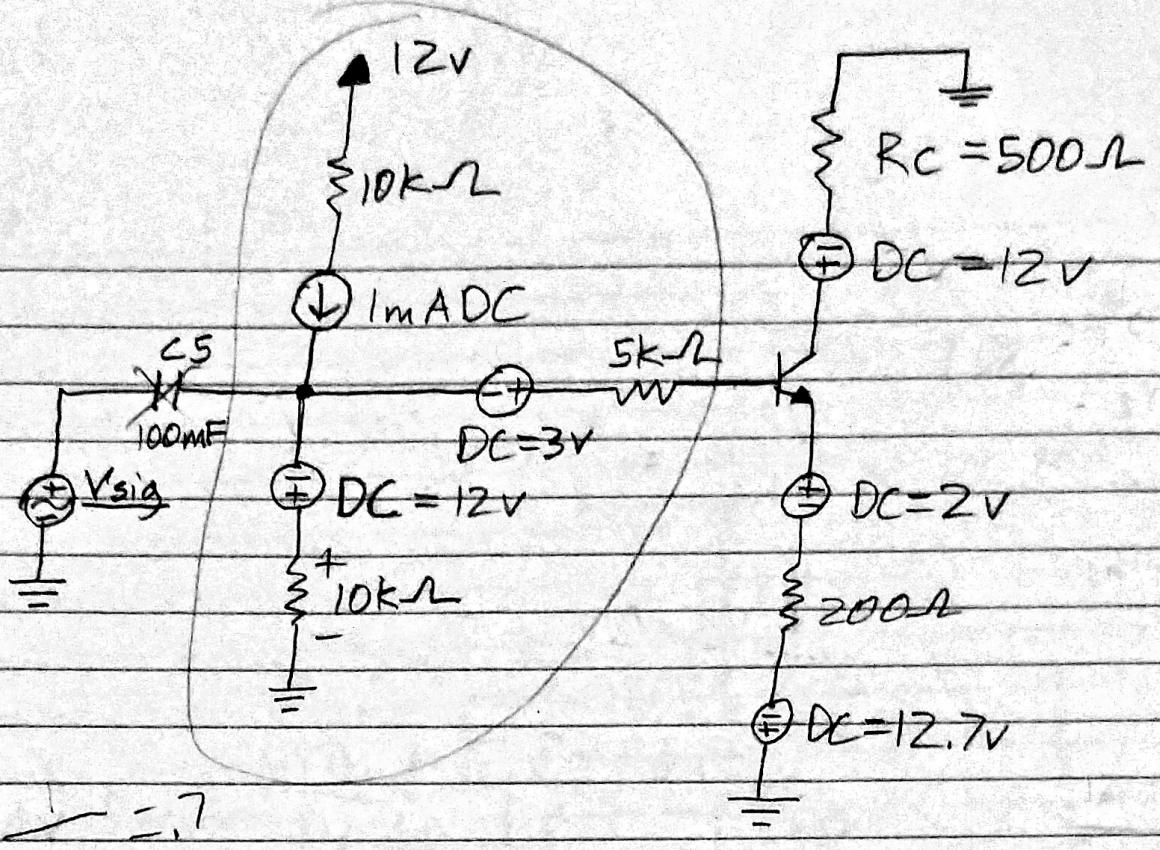
$$I_{B1}, I_{E1}, I_{C1}, V_{B1}, V_{E1}, V_{C1}$$





$$V_{Th} = 10k\Omega(1mA) - 12V + 3V = 1V$$

$$R_{Th} = 10k + 5k = 15k\Omega$$

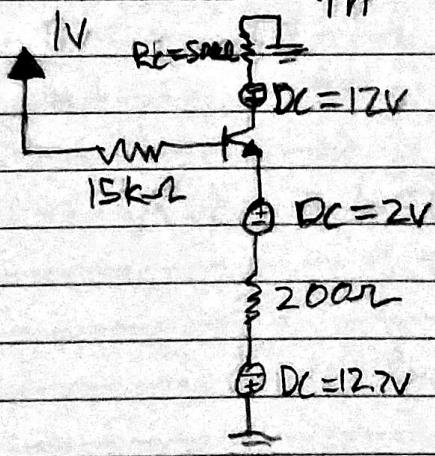

$$1V - 15k\Omega(I_B) - 0.7V - 2V - 200\Omega(I_E) + 12.7V = 0$$

$$I_E \left( \frac{-15k\Omega}{101} - 200\Omega \right) = -11V$$

$$I_E = 31.5mA$$

$$I_B = \frac{31.5mA}{101} = .313mA$$

$$V_B = 1V - 15k\Omega(.313mA) = -3.7V$$

$$V_E = -3.7 - 0.7V = -4.4V \quad I_C = .313mA \cdot 100 = 31.25mA$$

$$V_C = -500\Omega(31.25mA) + 12V = -3.63V$$

b)

$$V_C \geq V_B > V_E \quad \underline{\text{Active}}$$

$$-3.63 \geq -3.7V > -4.4V \checkmark$$

4.

a)

$$\frac{V_C}{V_{\text{sig}}} = -10 \text{ V/V}$$


$$V_{12} - V_C - V_B = 7 \text{ V}$$

$$\frac{-3.63 + 3.7}{10} = \frac{.07 \text{ V}}{10} = 7 \text{ mV}$$

b)

$$-RC(31.25 \text{ mA}) + 12 \text{ V} = -3.7 \text{ V}$$

$$RC \leq 502.4$$

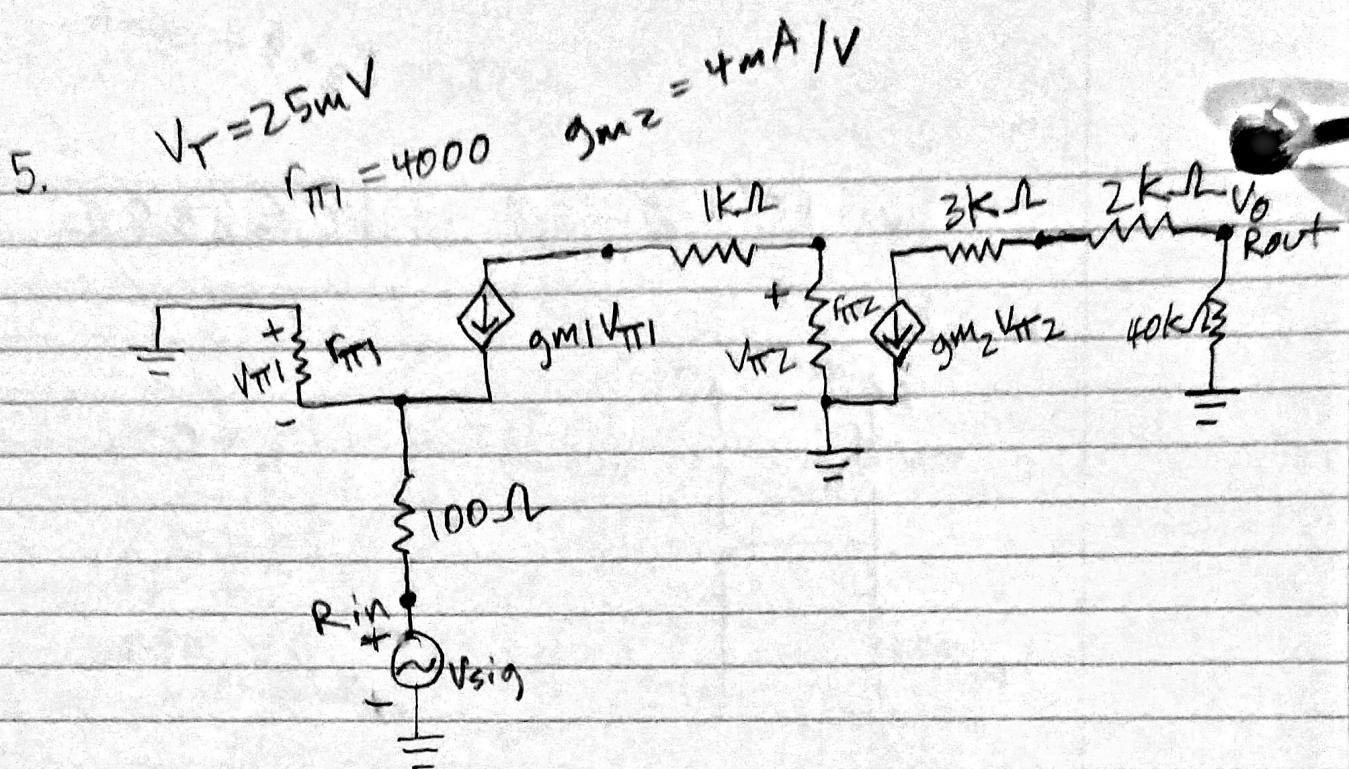

a)

$$R_{in} = 100\Omega + \frac{r_{TT1}}{\beta+1} = 140\Omega$$

b)  $R_{out} = 40k\Omega$

c)  $V_{TT1} = -\frac{V_{sig}(r_{TT1})}{100(\beta+1) + r_{TT1}}$

$$\beta = \frac{g_{m2}}{g_{m1}} \approx 25K$$

$$V_{TT1} = -V_{sig}(28)$$

$$V_{TT2} = g_{m1} V_{TT1} (r_{TT2})$$

$$g_{m1} = \frac{\beta}{4000} \\ = .025$$

$$V_{TT2} = -g_{m1} (V_{sig}(28)) (r_{TT2})$$


$$V_o = 4mA \left( (-(.025 (V_{sig}(28))) (25k)) (40k) \right)$$

$$\frac{V_o}{V_{sig}} = -28367$$

e)  $R_{out}$  would decrease in value, depending on value of  $r_o$ . But overall it will decrease.

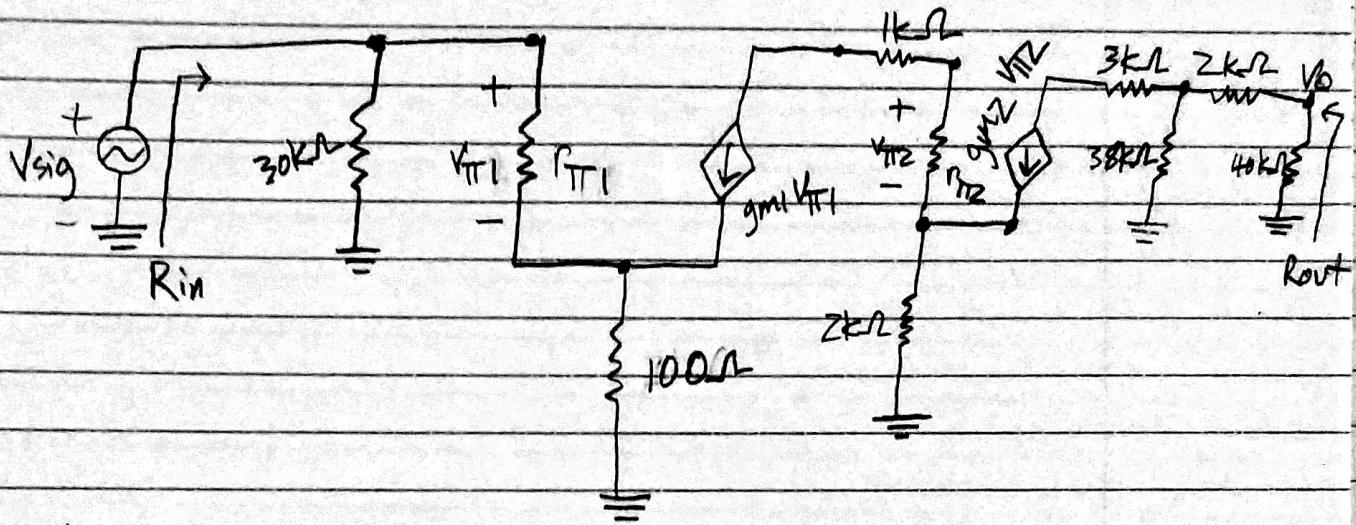d) Not ideal, too high for  $R_{out}$ , too low for  $R_{in}$

$$6. \quad g_{m2} = 2 \text{ mA/V} \quad r_{\pi 1} = 2000 \quad B = 100$$



a)

$$\begin{aligned} R_{in} &= 30k\Omega \parallel (r_{\pi 1} + 100(B+1)) \\ &= 8622 \Omega \end{aligned}$$

$$b) R_{out} = 40k\Omega \parallel 40k\Omega = 20k\Omega$$

$$c) V_{pi1} = \frac{V_{sig}(r_{\pi 1})}{r_{\pi 1} + 100(B+1)}$$

e)  $R_{out}$  will decrease in value, depending on value of  $r_o$ , but overall it will decrease.


$$g_{m1} = \frac{B}{2k} = .05 \quad V_{pi2} = -g_{m1} (V_{sig}(165)) r_{\pi 2}$$

$$r_{\pi 2} = \frac{B}{g_{m2}} = 50k \quad V_o = \frac{((2 \text{ mA})(-.05)(V_{sig}(165))(50k))(38k)}{40k + 38k + 2k} (140k)$$


$$\frac{V_o}{V_{sig}} = 15.7k$$

d) Not very ideal, too high of  $R_{out}$ , too low of  $R_{in}$

7.

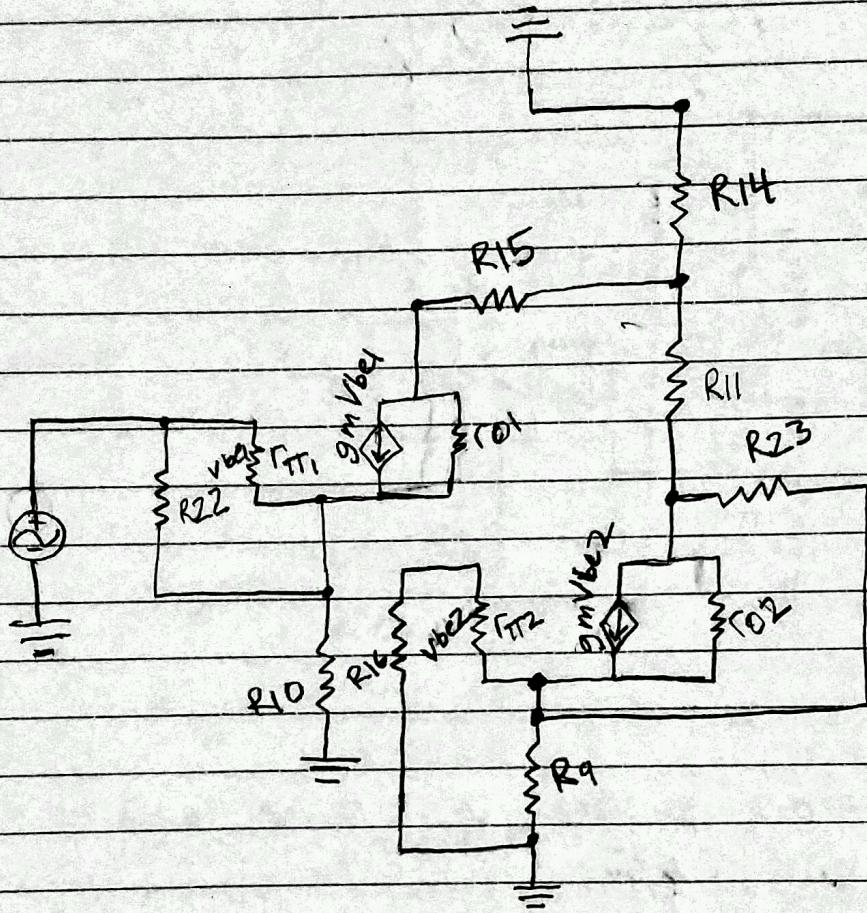


8.

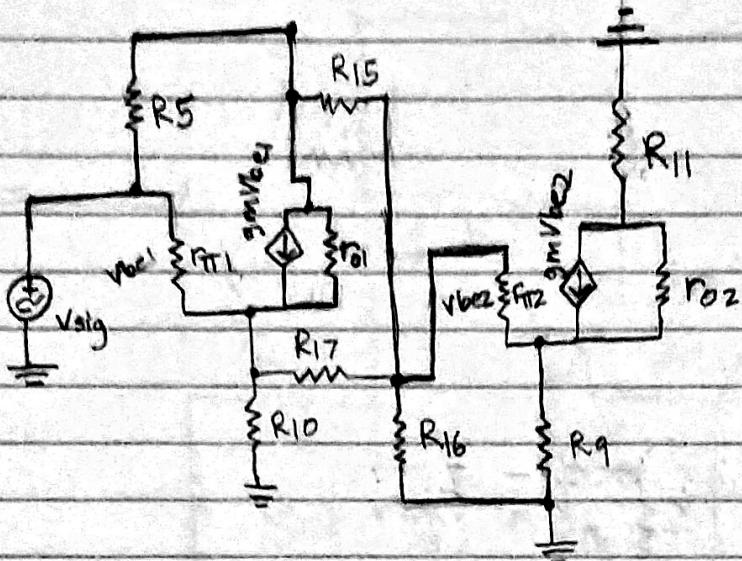

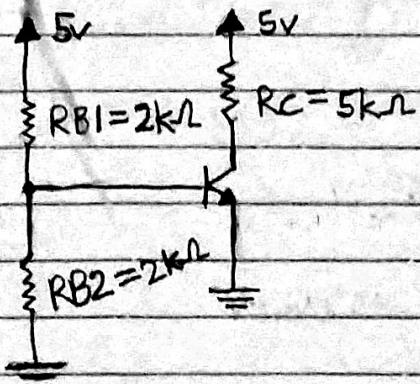9.

$$V_{BE} = 0.7 \quad \beta = 100 \quad V_{CE,SAT} = 0.2V$$




$$5V - I_C(5k\Omega) - 0.2 = 0$$

$$R_{Th} = \frac{(2k\Omega)(2k\Omega)}{2k\Omega + 2k\Omega} = 1k\Omega \quad I_C = 0.96mA$$

$$\beta_{forced} = \frac{0.96mA}{1.8mA}$$
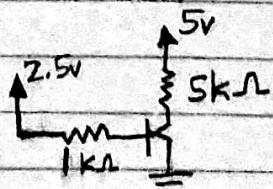
$$= .53 \quad V_{Th} = \frac{(5V)(2k\Omega)}{4k\Omega} = 2.5V$$




$$2.5V - 1k\Omega (I_B) - 0.7 = 0$$

$$I_B = 1.8mA$$

$$I_C = I_B \cdot \beta = 180\text{mA}$$


$$5V = RC(180\text{mA}) = 0.7 \quad RC \leq 23.8\Omega$$
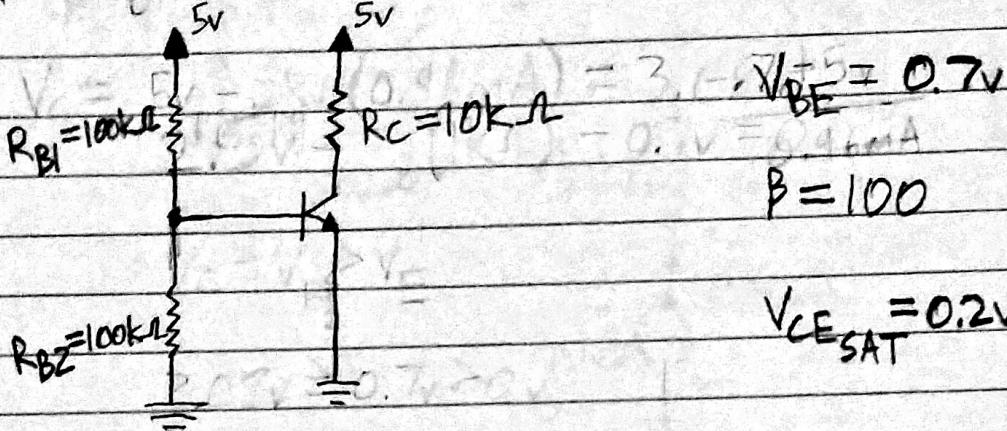
$$10. V_E = 2.5 - R_C(0.18\text{mA}) = .7$$



$$V_{Th} = \frac{5V(100k\Omega)}{200k\Omega} = 2.5V$$
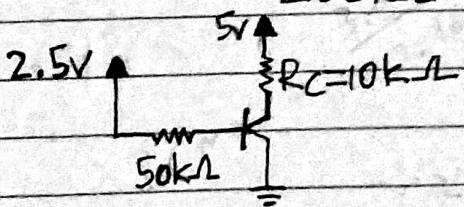
$$R_{Th} = \frac{(100k\Omega)(100k\Omega)}{200k\Omega} = 50k\Omega$$



$$\beta_{forced} = \frac{0.48\text{mA}}{36\text{mA}} = 13.33$$

$$I_C = I_B \cdot \beta = 36\text{mA}$$

$$5V - 10k\Omega(I_C) - 0.2V = 0$$

$$5V - RC(3.6\text{mA}) = .7V$$

$$V_B = 2.5V - 50k\Omega(36\text{mA}) = .7V \quad I_C = 0.48\text{mA}$$

$$RC \leq 1194.44\Omega$$

$$2.5V - 50k\Omega(I_B) - 0.7V = 0$$

$$V_C = 5V - 10k\Omega(0.48\text{mA}) = .2V$$

$$I_B = 36\text{mA}$$

$$V_E = 0V$$