

Nathan Donaldson
ECE 2280

Homework #4

1. 1) partially on because $V_{BE} \approx 0.7V$; $V_{CE} \geq 0.7V$

2) none $V_{BE} = 0.8V$, $V_{CE} = 0.1V$


3) partially on $V_{BE} = 0.7V$, $V_{CE} = 0.14V$

4) none $V_{BE} = 0.7V$, $V_{CE} = 0.1V$

5) partially on $V_{BE} = 0.7V$, $V_{CE} = 2.7V$

6) off $V_{BE} = 0$

2.

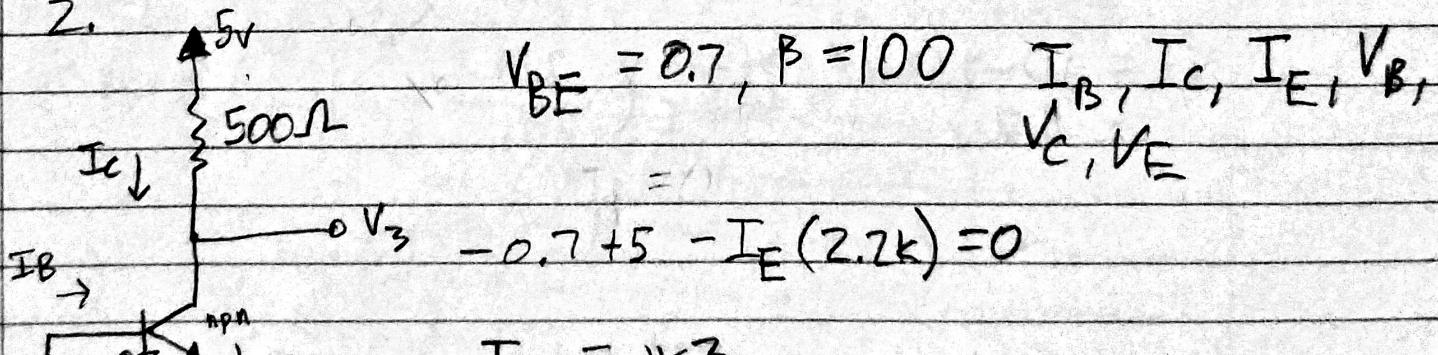

$$V_{BE} = 0.7, \beta = 100 \quad I_B, I_C, I_E, V_B, V_C, V_E$$

$$-0.7 + 5 - I_E(2.2k) = 0$$

$$I_E = \frac{4.3}{2.2k} = 1.95mA$$


$$I_B = \frac{I_E}{101} = 19.3mA$$

$$I_C = 100 \cdot 19.3mA = 1.93mA$$

$$V_E = V_B - 0.7 \\ = -0.7V$$

$$V_B = 0$$

$$V_C = -5 - 500I_C = 4.03V$$

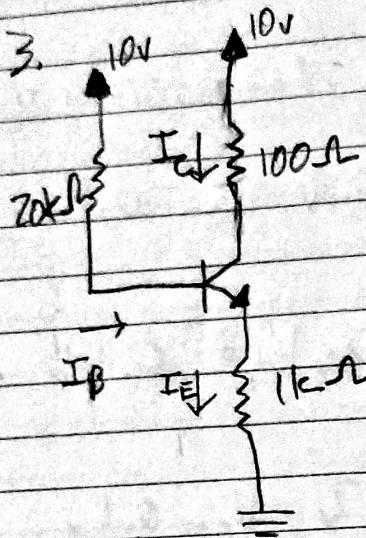

$$V_{BE} = -0.7 \quad \beta = 100$$

$$10V - I_B(20k\Omega) - 0.7V - I_E(1k\Omega) = 0$$

$$I_B = \frac{I_E}{101}$$

$$V_B = 10 - 7.69mA(20k\Omega)$$

$$= 8.5V$$

$$10V - \frac{I_E}{101}(20k\Omega) - 0.7V - I_E(1k\Omega) = 0$$

$$V_E = 8.5 - 0.7 = 7.8V \quad - \frac{I_E}{101}(20k\Omega) - I_E(1k\Omega) = -9.3$$


$$V_C = 10 - 7.69mA(100) \quad I_E \left(- \frac{20k\Omega}{101} - 1k\Omega \right) = -9.3$$

$$I_E = 7.76mA$$

$$I_B = \frac{7.76mA}{101} = 77mA$$


$$I_C = 100(77mA) = 7.69mA$$

4.

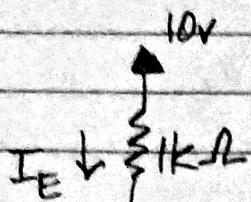

$$V_{BE} = 0.7 \quad \beta = 100$$
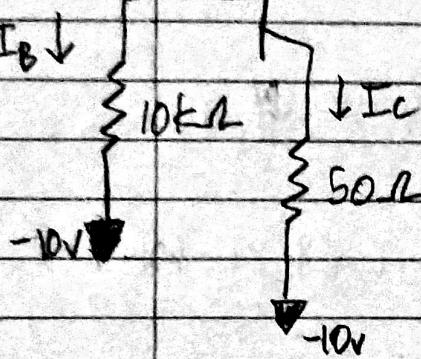
$$10 + I_B(10k\Omega) + 0.7 + I_E(1k\Omega) - 10 = 0$$



$$I_B = \frac{I_E}{101}$$

$$-10 - \frac{I_E}{101}(10k\Omega) + 0.7 - I_E(1k\Omega) - 10 = 0$$

$$-\frac{I_E}{101}(10k\Omega) - I_E(1k\Omega) = 19.3$$

$$V_B = -10 + I_B(10k\Omega) = -8.26V$$

$$I_E \left(\frac{10k\Omega}{101} - 1k\Omega \right) = 19.3$$

$$V_C = 10 - I_E(1k\Omega) = -9.13$$


$$I_E = 17.6mA$$

$$V_E = V_B + 0.7 = 7.6V$$

$$I_B = \frac{17.6mA}{101} = 176mA$$

$$I_C = 100(176mA) = 17.4mA$$


5.

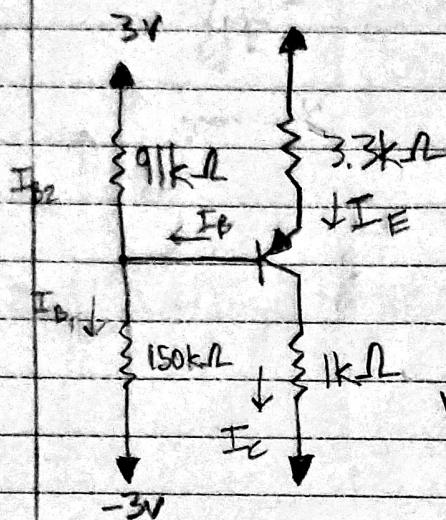

$$V_{BE} = 0.7 \quad \beta = 100$$

$$V_{Th} = \frac{3(150k) - 3(91k)}{150k + 91k} = 0.734V$$
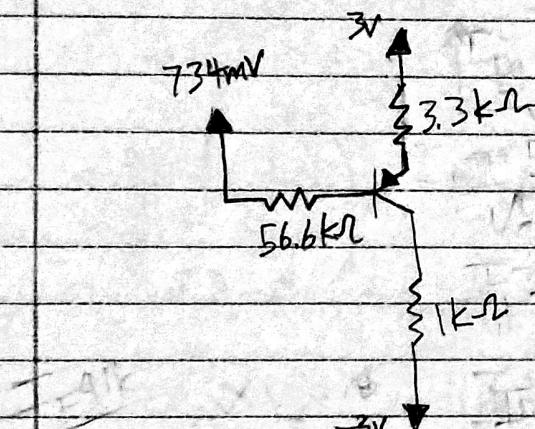
$$R_{Th} = \frac{(91k)(150k)}{91k + 150k} = 56.6k\Omega$$



$$734mV + I_B(56.6k) + I_E(1k) = 0$$

$$734mV + \frac{I_E(56.6k)}{101} + I_E(1k) - 3 = 0$$

$$I_E \left(\frac{56.6k}{101} + 1k \right) = 2.26$$

$$V_B = 734mV \cdot I_B(56.6k) = .96V$$


$$V_E = V_B + 0.7 = 1.66V$$

$$V_C = 3 - .396(3.3k) = -2.6V$$

$$I_E = 4mA$$

$$I_B = \frac{4mA}{101} = 40\mu A$$

$$I_C = 101(4mA) = 396mA$$

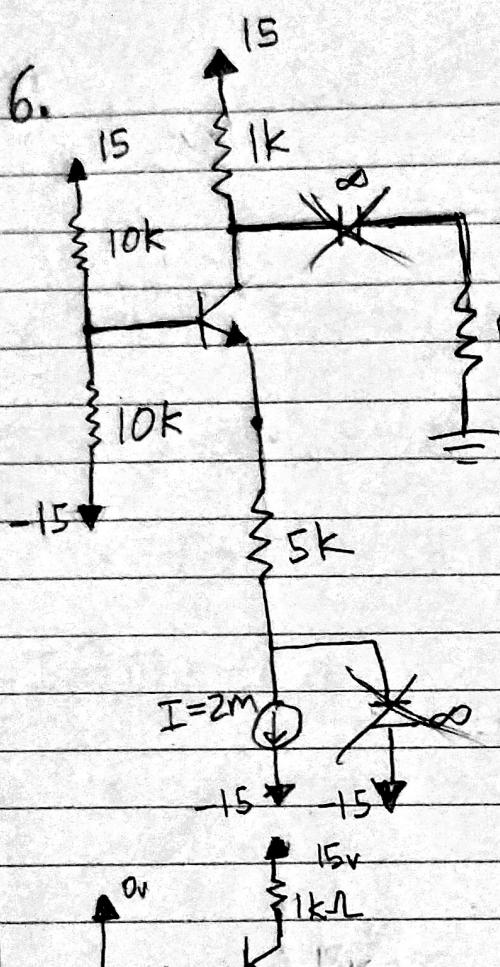

$$V_{BE} = 0.7V$$

$$\beta = 100$$

$$R_L = 1k \quad V_T = 25mV$$

$I_{B4}, I_{C4}, I_{E4}, V_{B4}, V_{C4}, V_{E4}$

$$I_E = 2mA$$

$$I_B = \frac{2mA}{101} = 19.8mA$$

$$I_C = 19.8mA(100) = 1.98mA$$

$$V_B = 0 - (1.98mA)(5k\Omega) = -99mV$$

$$V_E = V_B - 0.7 = -799mV$$

$$V_C = 15 - (1.98mA \cdot 1k) = 13.02V$$

7.

 $v_{B1}, v_{C1}, v_{B2}, v_{B3}, v_E$

15V

1kΩ

$$v_{BE} = 0.7 \quad \beta = 100 \quad V_T = 25mV$$

15V

1kΩ

$$15 - I_{B1}(50k\Omega) - 0.7 - B2 = 0$$

$$v_{B1} = 15V$$

$$v_{C1} = 15V$$

$$B2 - 0.7 - B3 = 0$$

$$0.7 \text{ each } v_{B2} = 14.4V$$

$$v_{B3} = 13.7V$$

$$v_{E3} = 17V$$

 $v_s \sim$

15V

15V

$$B3 - 0.7 - I_{E3}(4k\Omega) + 15 = 0$$

Q1

B1

Q2

B2

Q3

B3

 ∞

-15V

I_{E3}

4kΩ

$$I_{E1} = 683mA$$

$$I_{B1} = \frac{683mA}{101} = 6.8mA$$

$$I_{B3} = \frac{7mA}{101} = 69mA$$

$$I_{B2} = \frac{69mA}{101} = 683mA$$

$$B3 = B2 - 0.7$$

$$I_{C3} = 101 \cdot 69mA = 7mA$$


$$I_{E2} = 69mA$$

$$B3 = 15 - I_{B1}(50k\Omega) - 0.7 - 0.7$$

$$15 - I_{B1}(50k\Omega) - 0.7 - 0.7 - I_{E3}(4k\Omega) + 5 = 0$$

$$I_{E3} \left(\frac{50k\Omega}{101} - 4k\Omega \right) = 27.9 = 7mA$$

8.

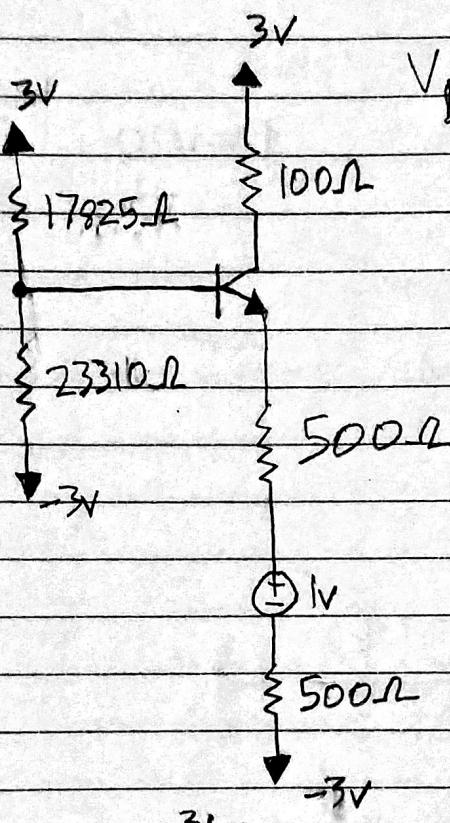


$$V_{BE} = 0.7 \quad \beta = 100$$

$I_B, I_C, I_E, V_B, V_C, V_E$

$$V_{Th} = \frac{3(23310) - 3(17825)}{23310 + 17825} = 400mV$$
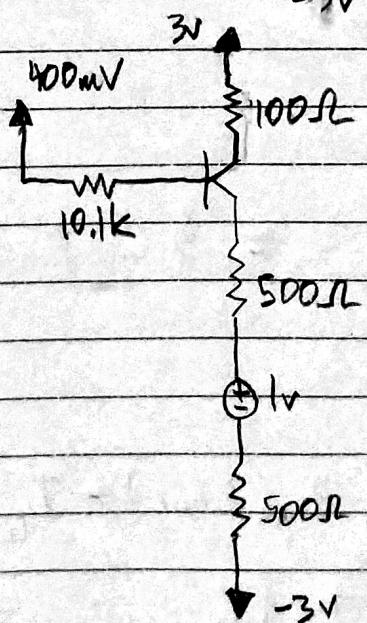
$$R_{Th} = \frac{(23310)(17825)}{23310 + 17825} = 10.1k$$



$$400mV - I_B(10.1k) - 0.7 - I_E(500) - I_E(500) + 3 = 0$$

$$I_E \left(-\frac{10.1k}{101} - 500 - 500 \right) = -1.7$$

$$I_E = 1.55mA$$

$$I_B = \frac{1.55mA}{101} = 15.35mA$$


$$I_C = 100(15.35mA) = 1.53mA$$

$$V_B = (15.35mA)(10.1k) = .25V$$

$$V_E = 0.25 - 0.7 = -0.45V$$

$$V_C = 2.85V$$


9.

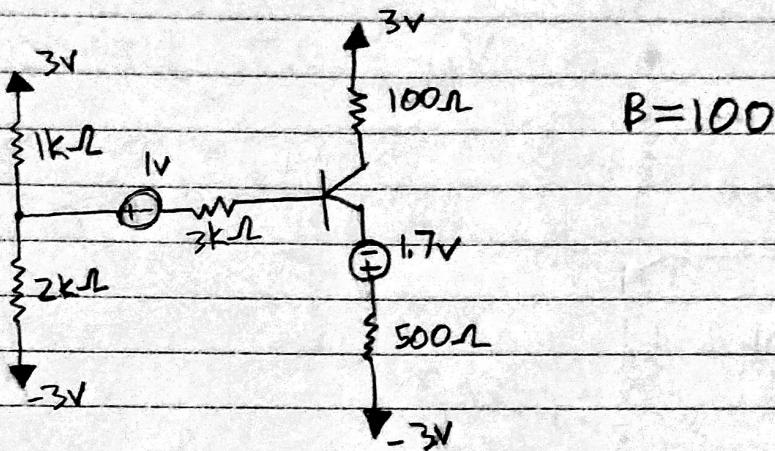

$$V_{Th} = \frac{3(2k) - 3(1k)}{1k + 2k} = 0V$$

$$V_{Th} = 0V$$
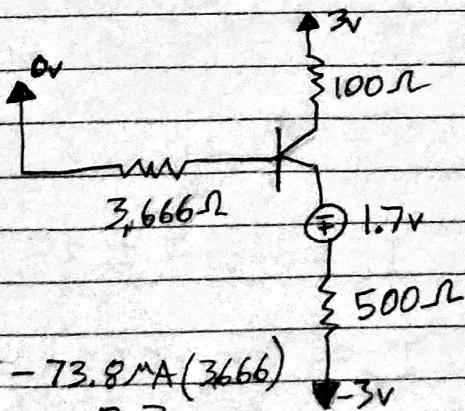
$$R_{Th} = \frac{(1k)(2k)}{1k + 2k} + 3k = 3,666\Omega$$



$$V_B = 1 - 73.8mA(3666) = -0.3V$$

$$0 - I_B(3,666) - I_E(500) + 1.7 = 0 \\ -0.7 + 3 = 0$$

$$I_E \left(\frac{-3666}{101} - 500 \right) = -4$$

$$I_E = 7.46mA$$

$$V_E = -0.3 - 0.7 = -1V$$


$$I_B = \frac{7.46mA}{101} = 73.8mA$$

$$V_C = 3 - 0.7 = 2.3 \\ = 2.3V$$

$$I_C = 100(73.8mA) = 739mA$$


10.

$$\beta = 99$$

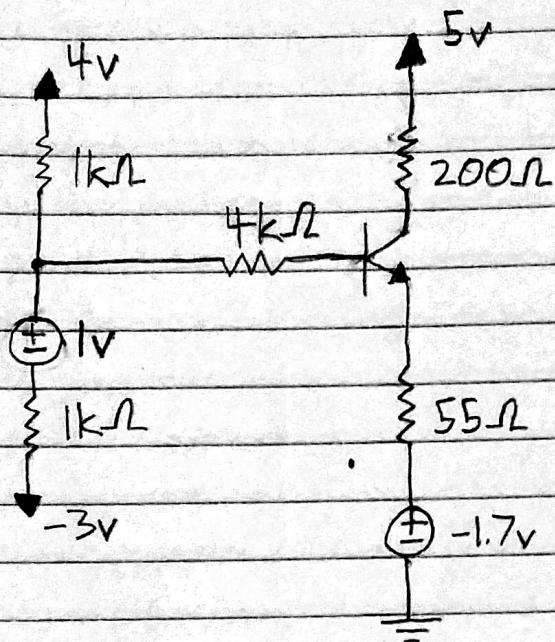

$$V_{Th} = \frac{((4V - 1V)1k\Omega) + (-3V + 1V)1k\Omega}{1k\Omega + 1k\Omega} = 2.5V$$
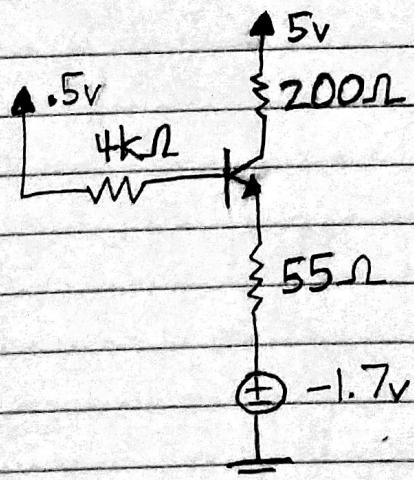
$$R_{Th} = \frac{(1k\Omega)(1k\Omega)}{1k\Omega + 1k\Omega} = 500\Omega$$



$$5 - I_B(4k\Omega) - 0.7 - I_E(55\Omega) - 1.7 = 0$$

$$I_E \left(\frac{4k\Omega}{100} - 55\Omega \right) = -1.9$$

$$I_E = 20mA$$

$$I_B = \frac{20mA}{100} = .2mA$$

$$V_B = (4k)(.2mA) - 0.7 = 0.1V \quad I_C = (99)(.2mA) = 19.8mA$$

$$V_E = 0.1 - 0.7 = -0.6V$$

$$V_C = (19.8mA)(200) - 1.7 - 5 - 0.7 = 1.04V$$