
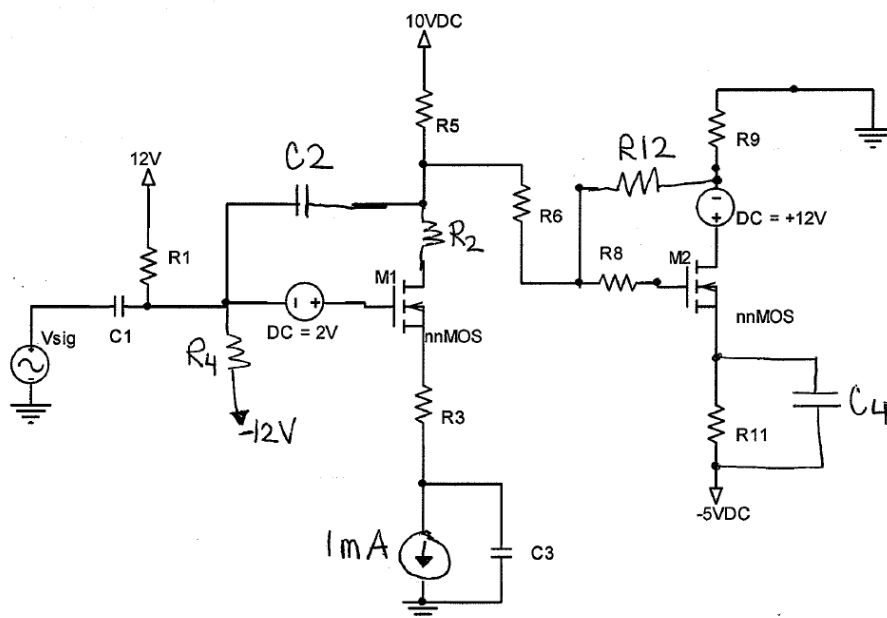


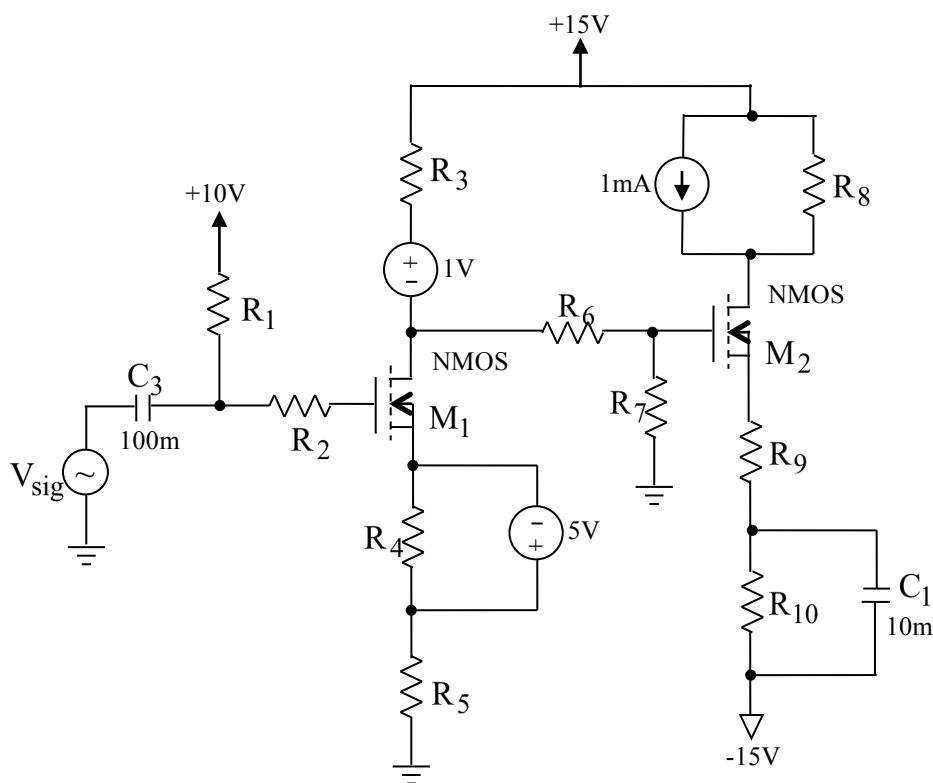1. For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , v_{gs2} , r_{o1} , etc.). $\lambda \neq 0$ for all transistors. (i.e. draw the small-signal with r_o included). $v_{sig} = 0.005 \sin(20t)$ AC. Draw the small-signal equivalent circuit **WITH** capacitors shown.



2. For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , v_{gs2} , etc.). $\lambda = 0.5$ for all transistors. Note that this will put a resistance (label it r_{o1} or r_{o2}) in parallel with the dependent source of the hybrid- π or model T. Let $v_{sig} = 0.005 \sin(20t)$ AC. Assume all capacitors are **SHORT** for the AC circuit.



3. Use: $V_t = 2\text{V}$

$$k_n' (W/L) = 3\text{mA/V}^2$$

V_{sig} is an AC source

Transistor 1 has DC values: $V_{GS} = 4\text{V}$, $I_D = 6\text{mA}$

Transistor 2 has DC values: $V_{GS} = 5.3\text{V}$, $I_D = 16.7\text{mA}$


$\lambda = 0$ (for all transistors)

For the following hybrid- π equivalent circuit, find the following values:

(a) R_{in} (input resistance –ignore the input source, V_{sig})

(b) R_{out} (output resistance–ignore R_L)

(c) midband gain, $\frac{V_o}{V_{sig}}$

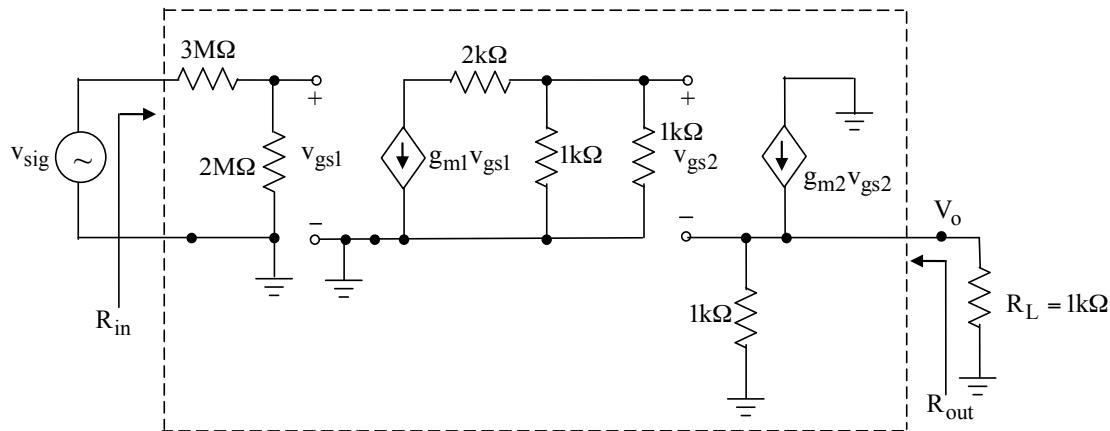


4. Let $V_t = 1\text{V}$, $k_n' (W/L) = 1\text{mA/V}^2$, V_{sig} is an AC source. Transistor 1 has DC values: $V_{GS} = 3\text{V}$, $I_D = 2\text{mA}$.

Transistor 2 has DC values: $V_{GS} = 5\text{V}$, $I_D = 8\text{mA}$. $\lambda = 0$ (for all transistors) and assume all transistors are saturated. For the following hybrid- π equivalent circuit, find the following values:

(a) R_{in} (input resistance –ignore the input source, V_{sig})

(b) R_{out} (output resistance–ignore R_L)

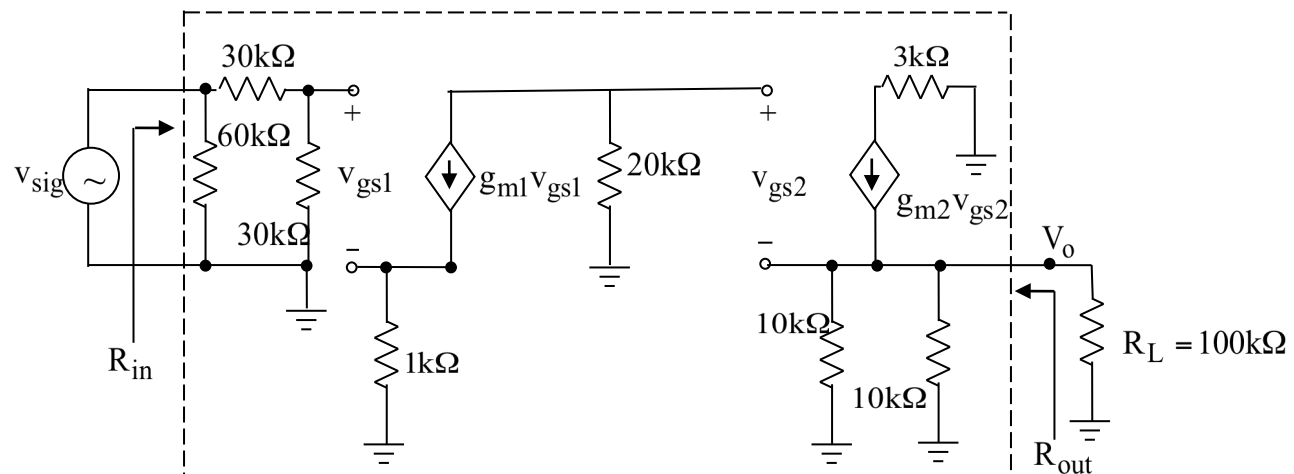
(c) ideal midband gain, $\frac{V_o}{V_{sig}}$



5. Use: $V_t=1V$, $k_n'(W/L)=2mA/V^2$, v_{sig} is an AC source, $\lambda=0$ and all are saturated transistors
 Transistor 1 has DC values: $V_{GS}=1.5V$, $I_D=0.25mA$
 Transistor 2 has DC values: $V_{GS}=13.5V$, $I_D=156.25mA$

For the following hybrid- π equivalent circuit, find the following values:

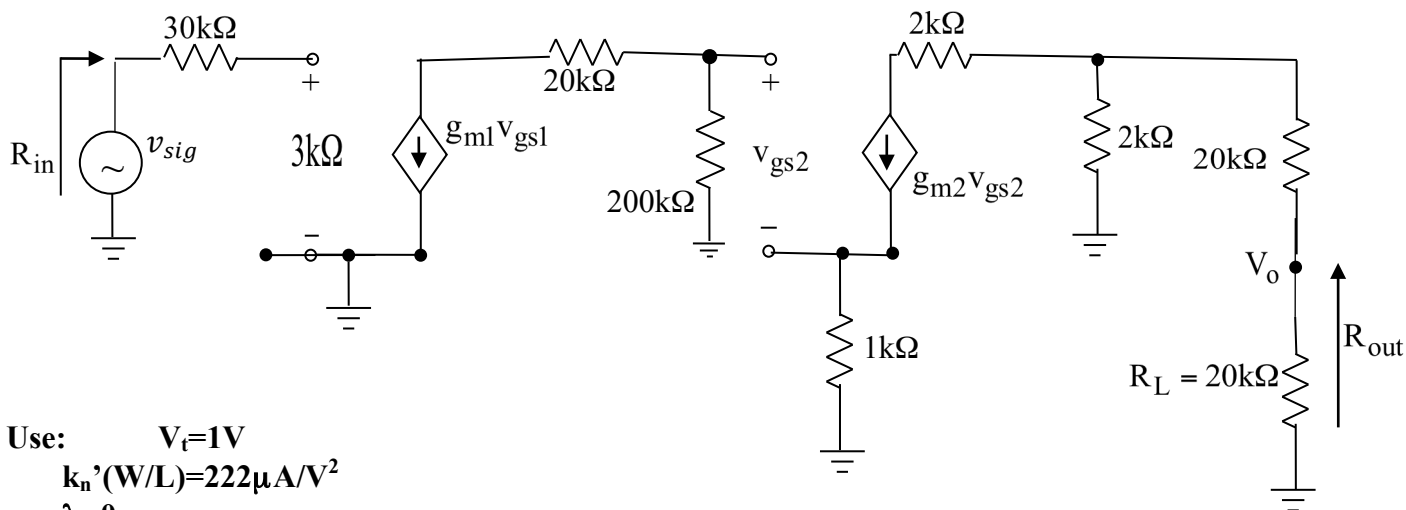- (a) R_{in} (input resistance – ignore the input source, v_{sig})
 (b) R_{out} (output resistance – ignore the load resistor, R_L)
 (c) ideal overall midband gain, $\frac{V_o}{v_{sig}}$



6. Use: $V_t=1V$
 $k_n'(W/L)=222\mu A/V^2$
 $\lambda=0$
 $V_{IN} = 3+0.002\sin(20t)$

For DC analysis, assume that the capacitors act as an open. The current source is not ideal and has a voltage drop across it.


- (a) Solve for the DC currents:
 a. I_1
 b. I_S

- (b) Solve for the DC voltages:
 a. V_{G2}
 b. V_{S2}
 c. V_{S1}

- (c) Verify that transistor M2 is saturated.


- (d) State the DC bias point for transistor M1.

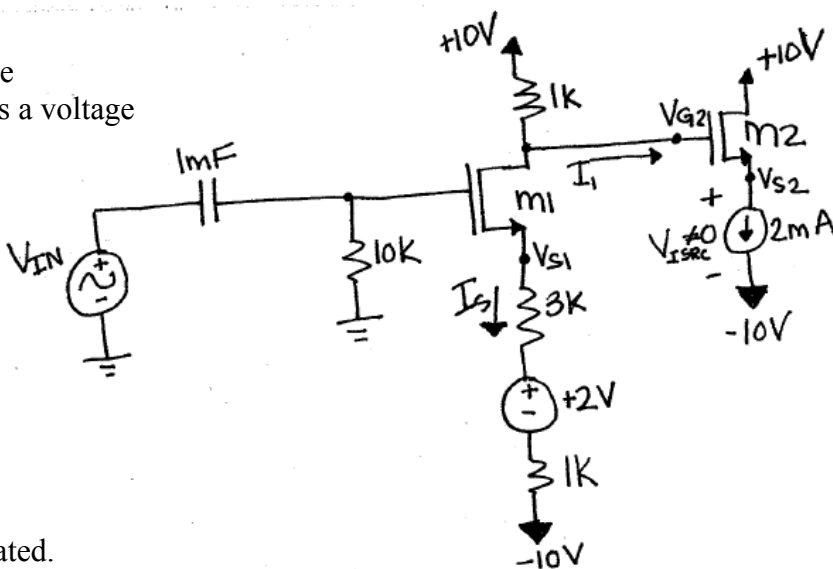- (e) Assuming that the transistor amplification is $V_{S2}/V_1 = -4V/V$. Assume the input frequency is operating within the circuits operating range. What is the **total** (AC and DC) instantaneous output for V_{S2} using the V_{IN} value stated above.



7. Use: $V_t=1V$, $k_n'(W/L)=1mA/V^2$, $\lambda=0$, $V_{IN} = (5+10m\sin(20t))V$
 For DC analysis, assume that the capacitors act as an open. The current source is not ideal and has a voltage drop across it.

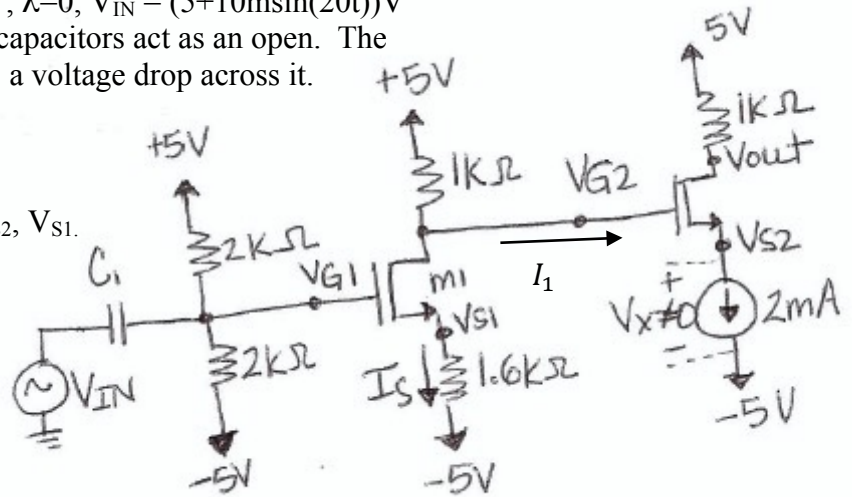- (a) Solve for the DC currents I_1 , I_S .
 (b) Solve for the DC voltages V_{G2} , V_{S2} , V_{S1} .
 (c) Verify that transistor M2 is saturated.
 (d) State the DC bias point for transistor M1.




- (e) Assuming that the transistor amplification is $V_{out}/V_{IN} = +5V/V$. Assume the input frequency is operating within the circuits operating range. Assume that the amplification does not pull the transistors out of saturation. Draw a rough sketch of the **total instantaneous value** seen at V_{out} using the V_{IN} value stated above.


8. $V_t=1V$, $k_n'(W/L)=10mA/V^2$, V_{sig} is an AC source, $\lambda=0$ and assume all transistors are saturated.
 Transistor 1 has DC values: $V_{GS}=9V$, $I_D=3.2A$
 Transistor 2 has DC values: $V_{GS}=1.18V$, $I_D=162\mu A$

For the following hybrid- π equivalent circuit, find the following values:

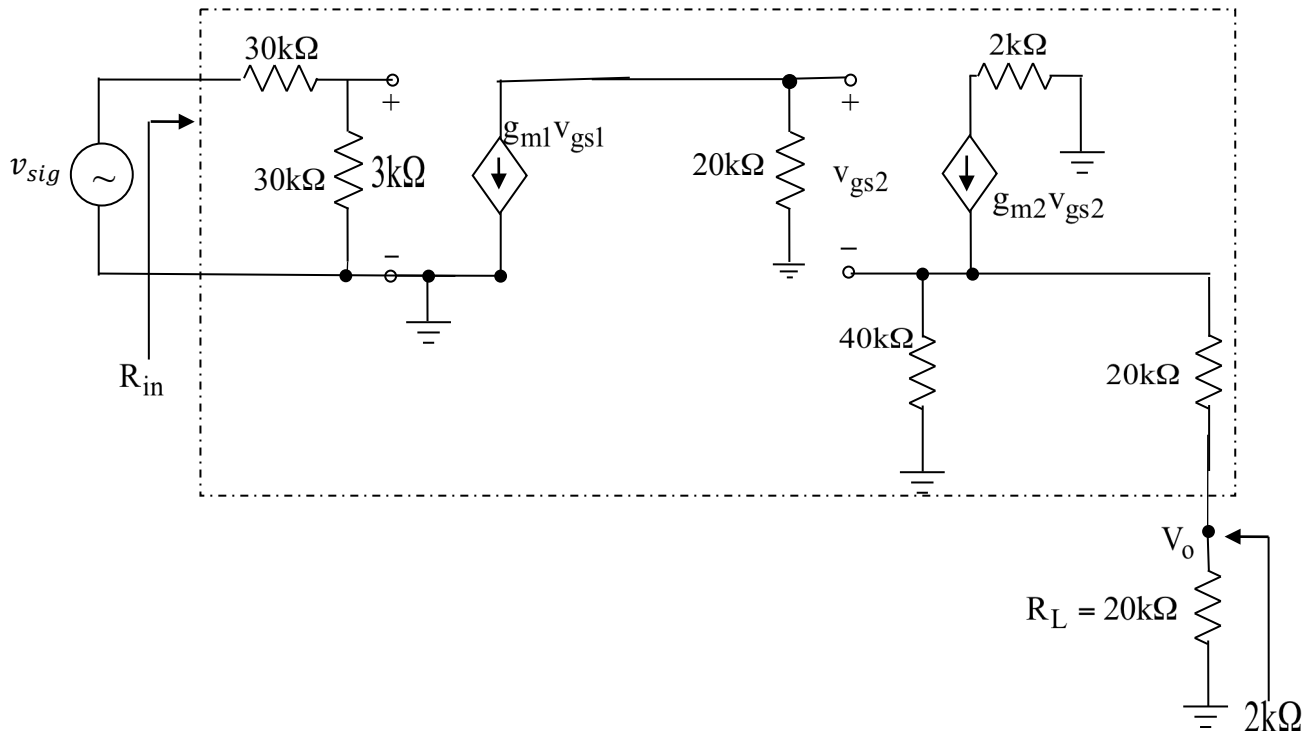- a. R_{in} (input resistance –ignore the input source, V_{sig})
 b. R_{out} (output resistance-**ignore** R_L)
 c. Find the ideal overall midband gain, $\frac{V_o}{v_{sig}}$ (make sure to include R_L).



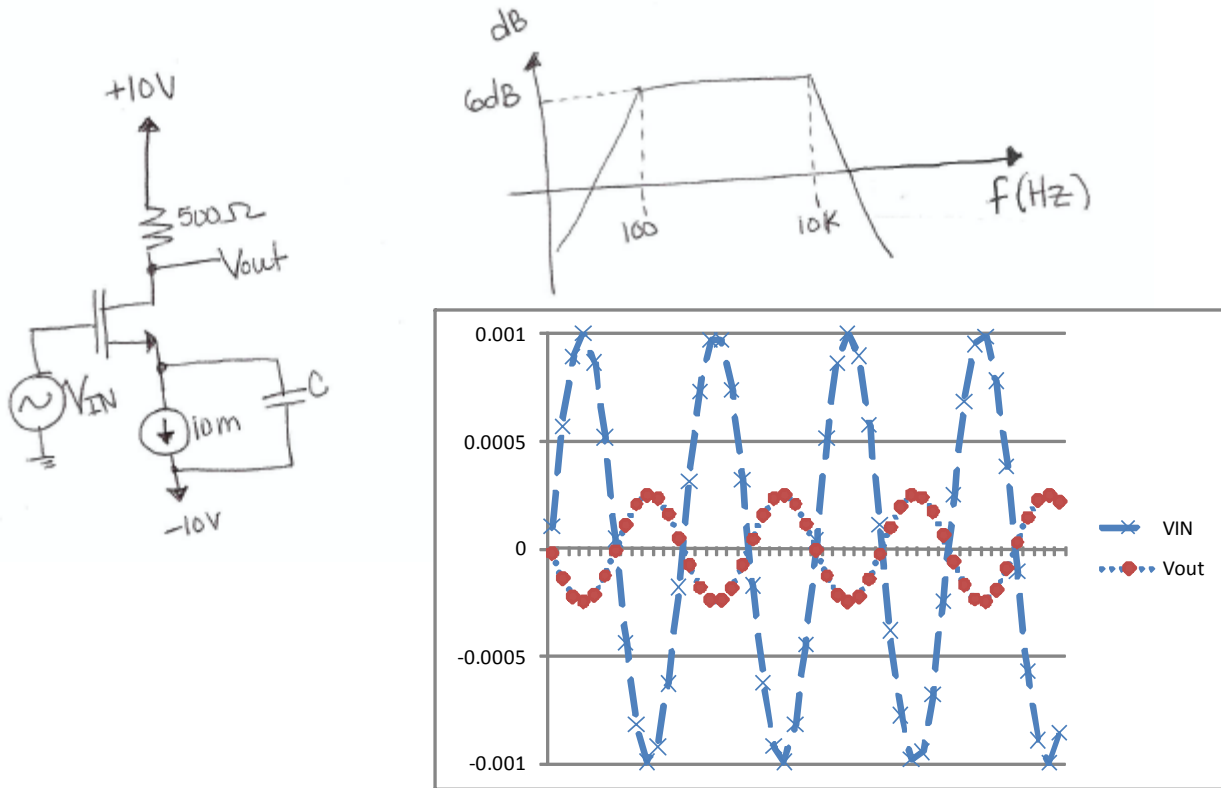9. Let $V_t=2V$, $\lambda=0$, $k_n'(W/L)=1mA/V^2$, $V_{IN} = 5+1m\sin(\omega t)$. This amplifier was designed to achieve an overall gain of $-2V/V$. The magnitude Bode plot of the amplifier is shown below. An AC graph(DC is removed) of V_{in} and V_{out} is shown for an input frequency of 100kHz. Why is the output peak not 2mV?



10. Let $V_t=2V$, $\lambda=0$, $k_n'(W/L)=2mA/V^2$, $V_{IN} = 5+50m\sin(\omega t)$. Assume that the capacitor acts as an open for DC operation and a short for AC operation. This circuit has distortion seen in the AC amplification. Explain in detail why it is distorted.

