

# Introduction to Electrical & Computer Engineering

## Kirchhoff's Laws (KCL, KVL)



**Dr. Cynthia Furse**  
**University of Utah**

# Kirchhoff's Current Law (KCL)

**Sum of currents entering a node = 0**

**OR**

$$i_1 - i_2 - i_3 + i_4 = 0$$

**Sum of currents leaving a node = 0**


**OR**

$$-i_1 + i_2 + i_3 - i_4 = 0$$

**Sum of currents leaving = sum of  
Currents entering a node**

$$i_1 + i_4 = i_2 + i_3$$
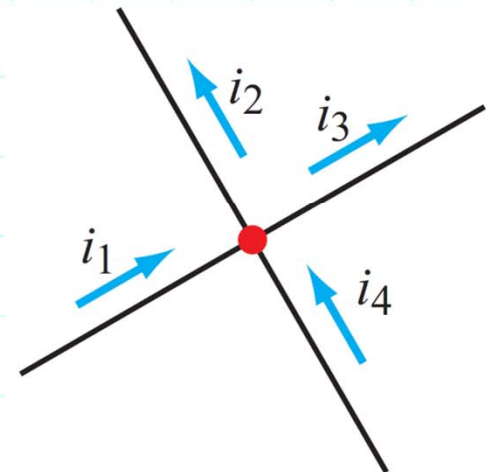
$$\sum_{n=1}^N i_n = 0 \quad (\text{KCL}),$$





# Kirchhoff's Voltage Law (KVL)

**Sum of voltages around a closed path = 0**

**OR**

$$-V_{DC} + V_1 + V_2 = 0$$


**Sum of voltage drops = sum of voltage rises**

$$V_{DC} = V_1 + V_2$$

$$\sum_{n=1}^N v_n = 0 \quad (\text{KVL}),$$

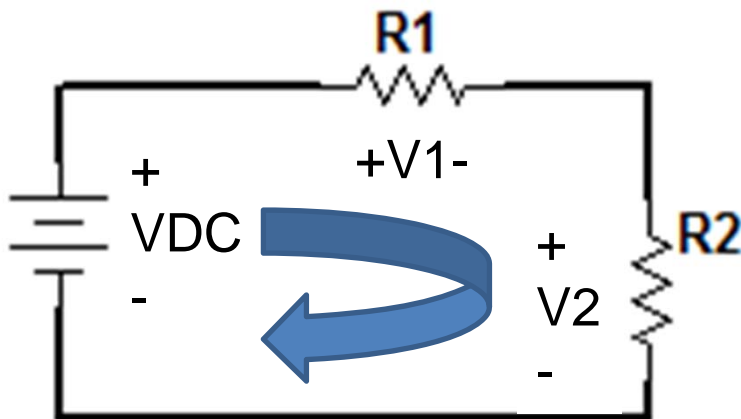
## Sign Convention

- Add up the voltages in a systematic clockwise movement around the loop.
- Assign a positive sign to the voltage across an element if the (+) side of that voltage is encountered first, and assign a negative sign if the (−) side is encountered first.



**Circuits**, Second Edition by Fawwaz T. Ulaby and Michel M. Maharbiz, © NTS Press, Used with Permission by the Publisher

# Applying KCL and KVL

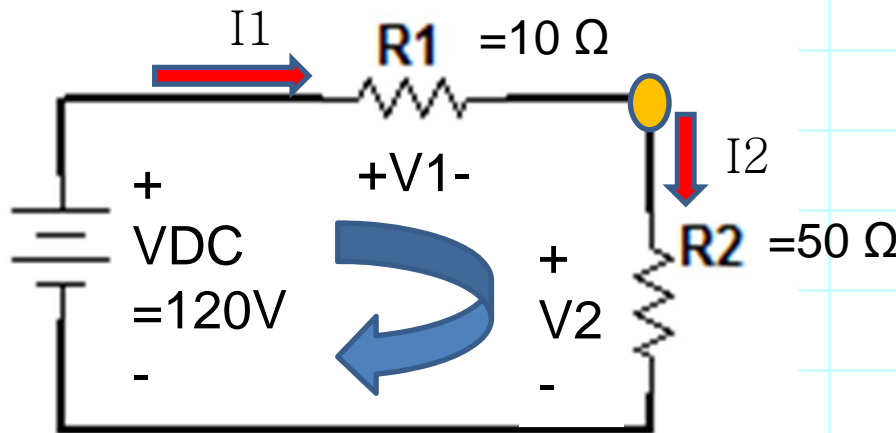

$$-V_{DC} + V_1 + V_2 = 0 \quad (1)$$

**What is KNOWN?**

$V_{DC} = 120V$ ,  $R_1 = 10\Omega$ ,  $R_2 = 50\Omega$

**What is Unknown?**

$V_1, V_2$

**2 Unknowns need 2 Equations**

**Ohm's Law gives 2 more equations**

**But 2 more unknowns ( $I_1, I_2$ )**

$V_1 = (I_1)(R_1)$  and  $V_2 = (I_2)(R_2)$  (2,3)

**Node Equation gives one more eqn:**


$I_1 = I_2$  (4)

**Four unknowns ( $V_1, V_2, I_1, I_2$ )**

**Four Equations (1,2,3,4)**

**OK! Now we can solve it!**

# Applying KCL and KVL

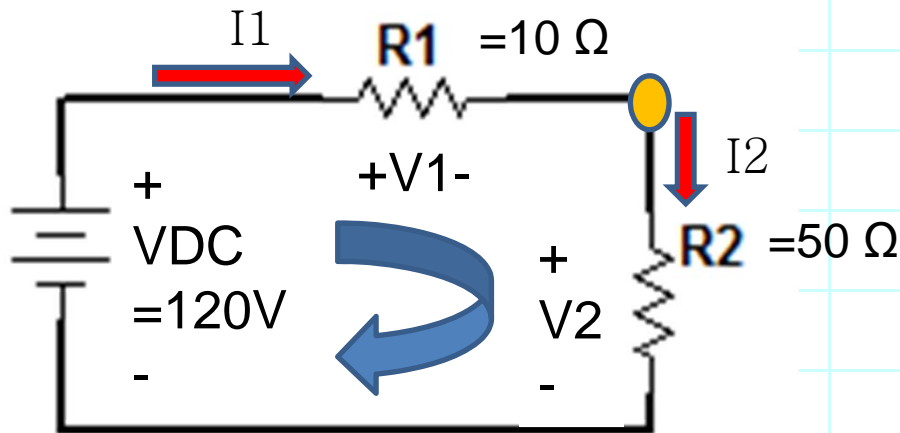

$$-V_{DC} + V1 + V2 = 0$$

$$V_{DC} = 120V, R1 = 10\Omega, R2 = 50\Omega$$

$$V1 = (I1)(R1) \text{ and } V2 = (I2)(R2)$$

$$I1 = I2 = I$$

Substituting:

$$-120V + (I)(10\Omega) + (I)(50\Omega) = 0$$

$$I = 120V / (10 + 50\Omega) = 2A$$


Then

$$V1 = (2A)(10\Omega) = 20V$$


$$V2 = (2A)(50\Omega) = 100V$$

Check:  $V_{DC} = ? V1 + V2$  Yes!

# KCL and KVL Cookbook

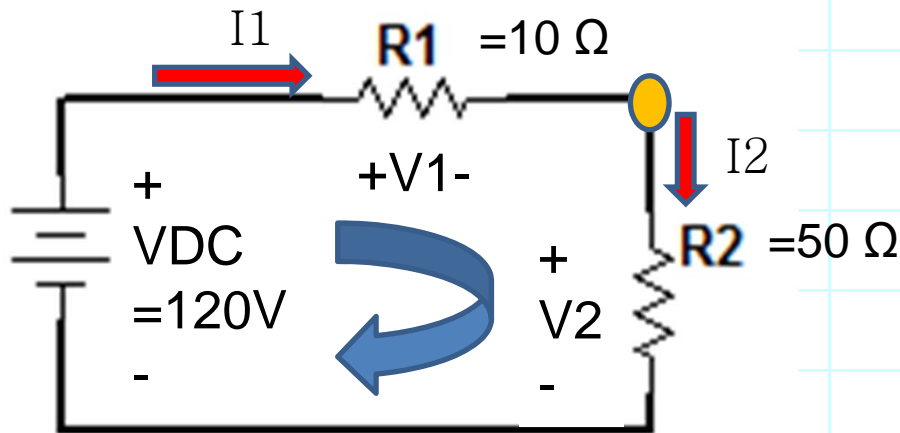

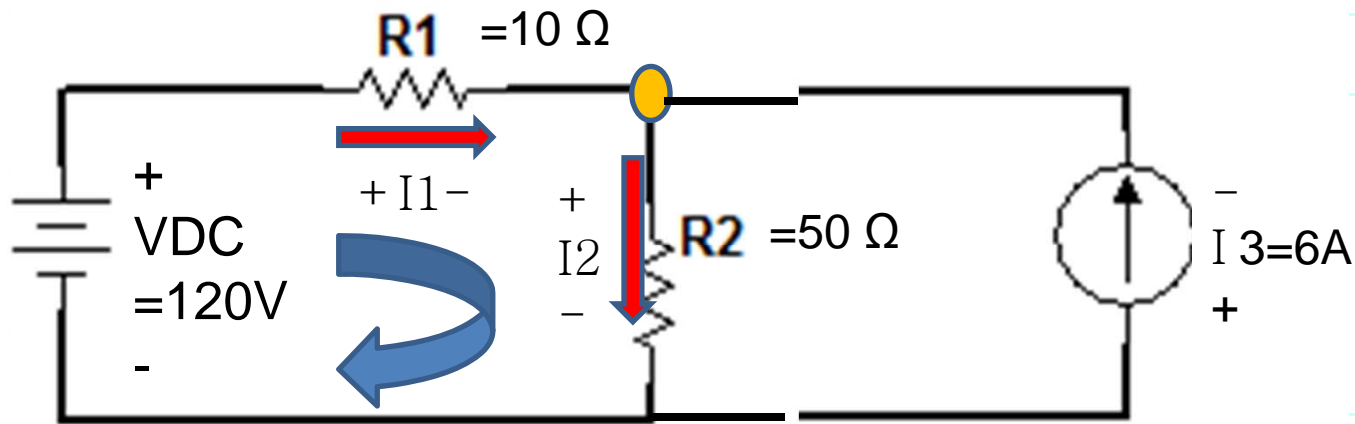1. Write all KNOWN values
2. Keep track of all unknown values (Need as many independent equations as unknowns)
3. Write all KVL (Loop) equations. Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many KCL (node) equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current.
6. Solve for the unknowns



1. Write all KNOWN values  $V_{DC}=120V$ ,  $R_1=10\Omega$ ,  $R_2=50\Omega$ ,  $I_3=6A$
2. Keep track of all unknown values  $I_1$ ,  $I_2$   
(Need as many independent equations as unknowns)
3. Write all KVL (Loop) equations.  $-V_{DC} + (I_1)(R_1) + (I_2)(R_2) = 0$  (1)  
Each loop must pick up at least ONE new element. Current sources are not counted as 'new' elements.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many KCL (node) equations as needed to fill in unknowns. Each KCL equation must pick up at least ONE new current.  $I_1 + I_3 = I_2$  (2)
6. Solve for the unknowns

## 6. Solve:

$$-120V + (I_1)(10\Omega) + (I_2)(50\Omega) = 0$$

$$I_1 + 6A = I_2$$

Substitute to remove variables:

$$-120V + (I_1)(10\Omega) + (I_1 + 6A)(50\Omega) = 0$$

$$-120V + (I_1)(10\Omega) + (I_1)(50\Omega) + (6A)(50\Omega) = 0$$

Solve for remaining variable:



$$I_1 = (120V - (6A)(50\Omega)) / (10\Omega + 50\Omega) = -3A$$

Go back to original equations to find other variables


$$I_2 = -3A + 6A = 3A$$



# Interpret / Reality Check:

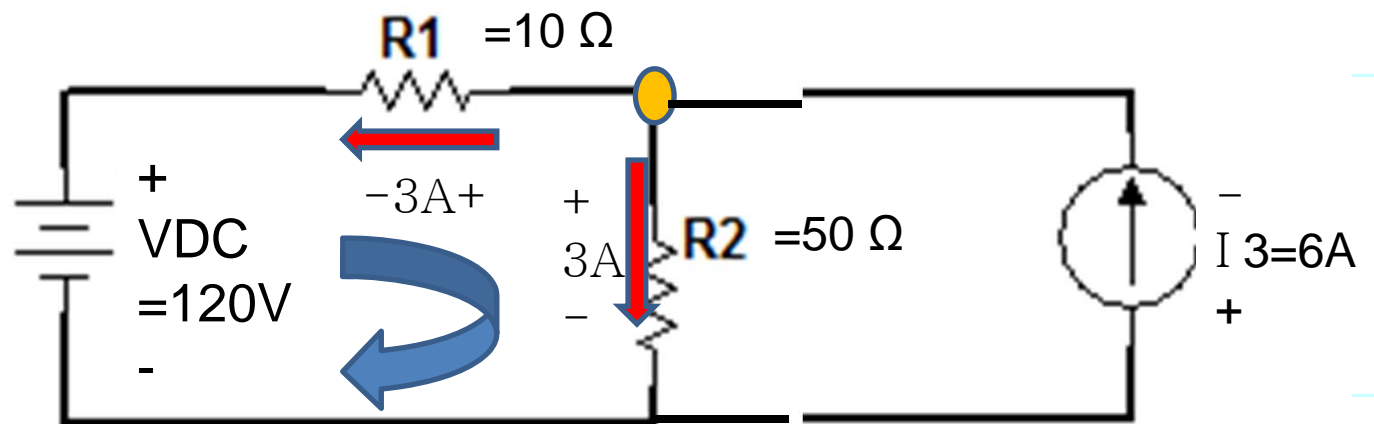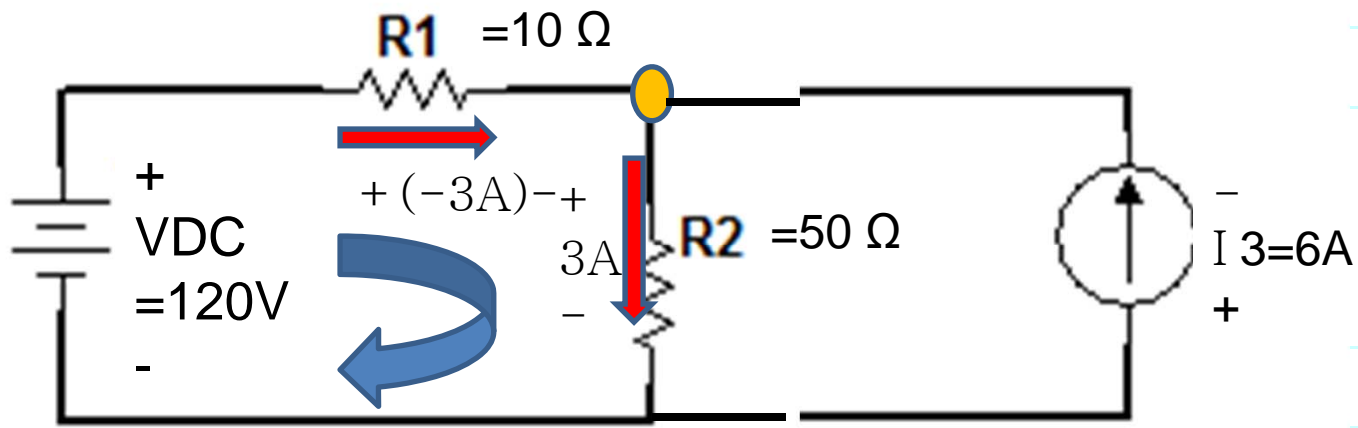


# KCL and KVL Cookbook

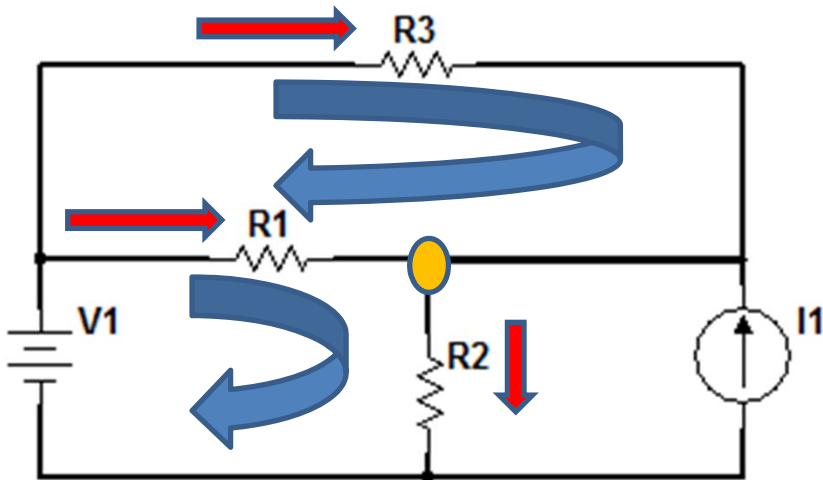


1. Write all KNOWN values
2. Keep track of all **unknown** values  
(Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations.  
Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current.
6. Solve for the unknowns.

# KCL and KVL Cookbook

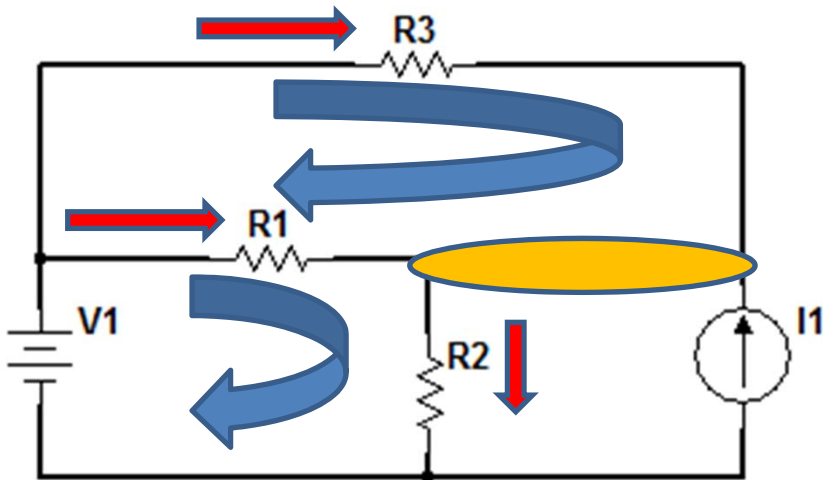


1. Write all KNOWN values
2. Keep track of all **unknown** values  
(Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations.  
Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current.
6. Solve for the unknowns.

# KCL and KVL Cookbook

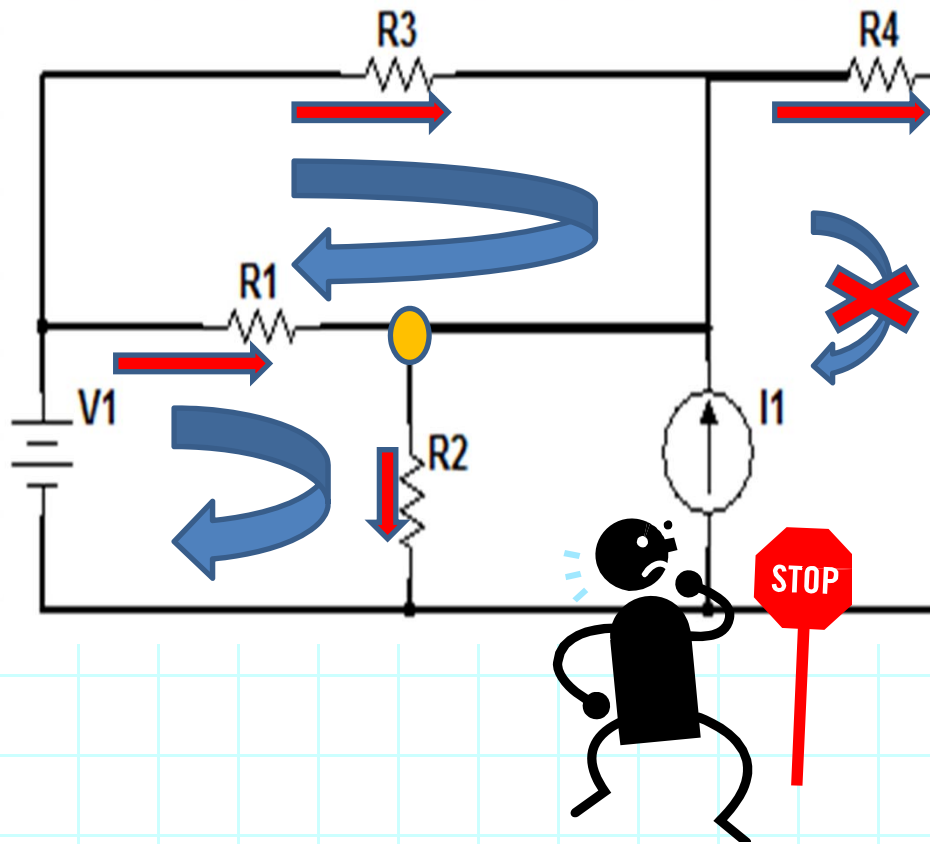

1. Write all KNOWN values
2. Keep track of all **unknown** values (Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations. Each loop must pick up at least one new element. **Current sources can't be in loops.**
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current.
6. Solve for the unknowns.


# KCL and KVL Cookbook

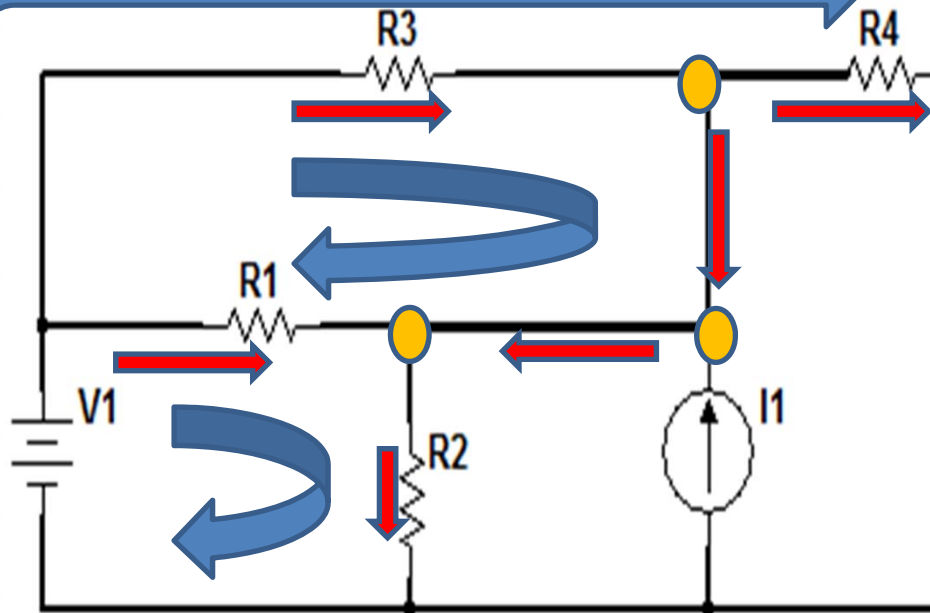

1. Write all KNOWN values
2. Keep track of all **unknown** values (Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations. Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current.
6. Solve for the unknowns.




# KCL and KVL Cookbook

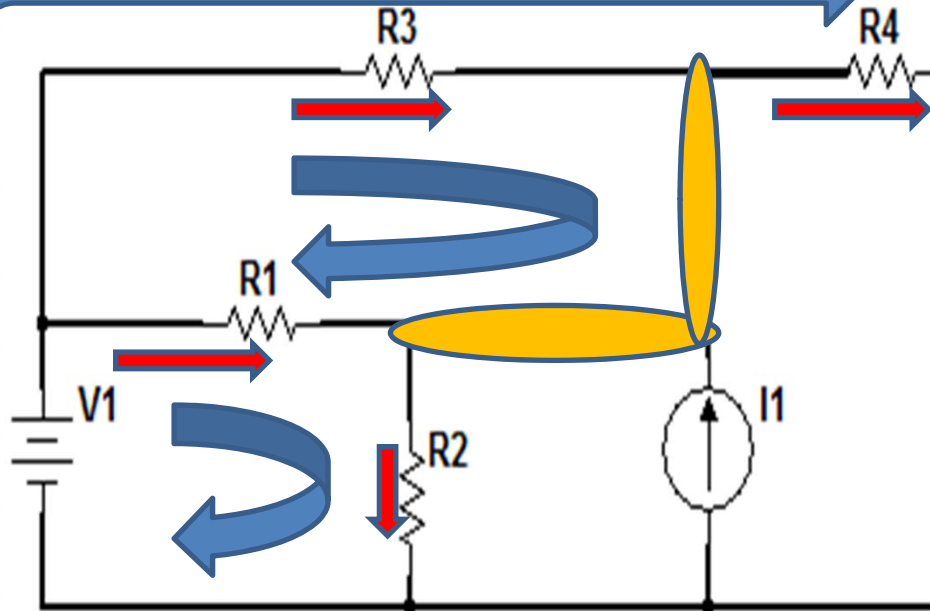

1. Write all KNOWN values
2. Keep track of all **unknown** values (Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations. Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current.
6. Solve for the unknowns.


# KCL and KVL Cookbook

## Does this work? NO!

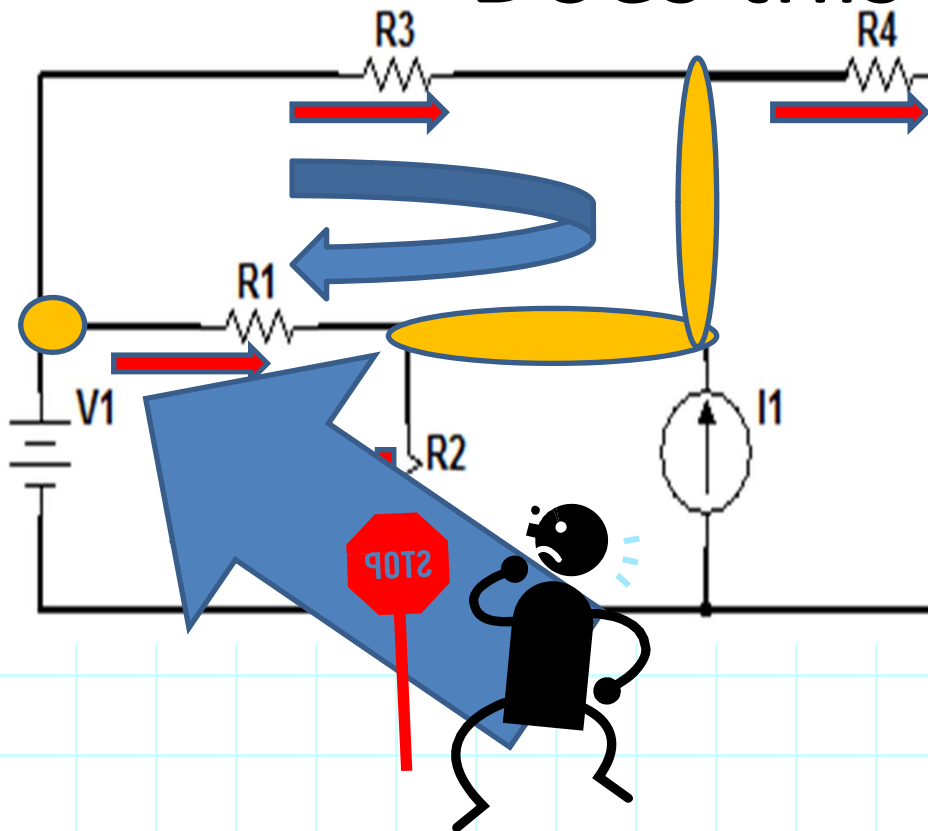

1. Write all KNOWN values
2. Keep track of all **unknown** values (Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations. Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current. Shorts combine nodes. **Nodes touching voltage sources can't be used.**
6. Solve for the unknowns.

# KCL and KVL Equations

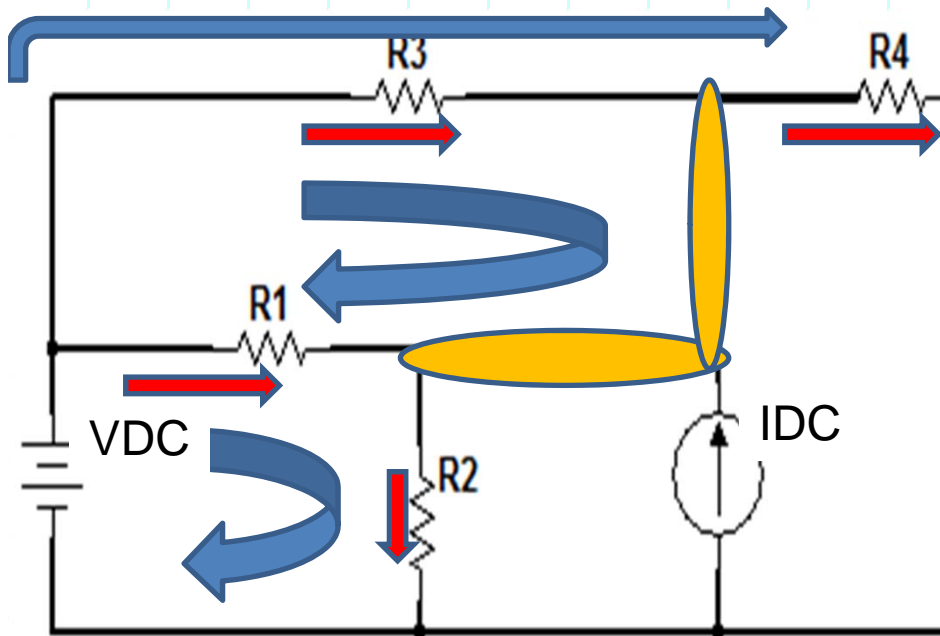

Loops:

$$-V_{DC} + I_1 R_1 + I_2 R_2 = 0$$


$$I_3 R_3 - I_1 R_1 = 0$$

$$-V_{DC} + I_3 R_3 + I_4 R_4 = 0$$

Node:

$$I_3 - I_4 + I_1 - I_2 + I_{DC} = 0$$

# KCL and KVL Matrix Math

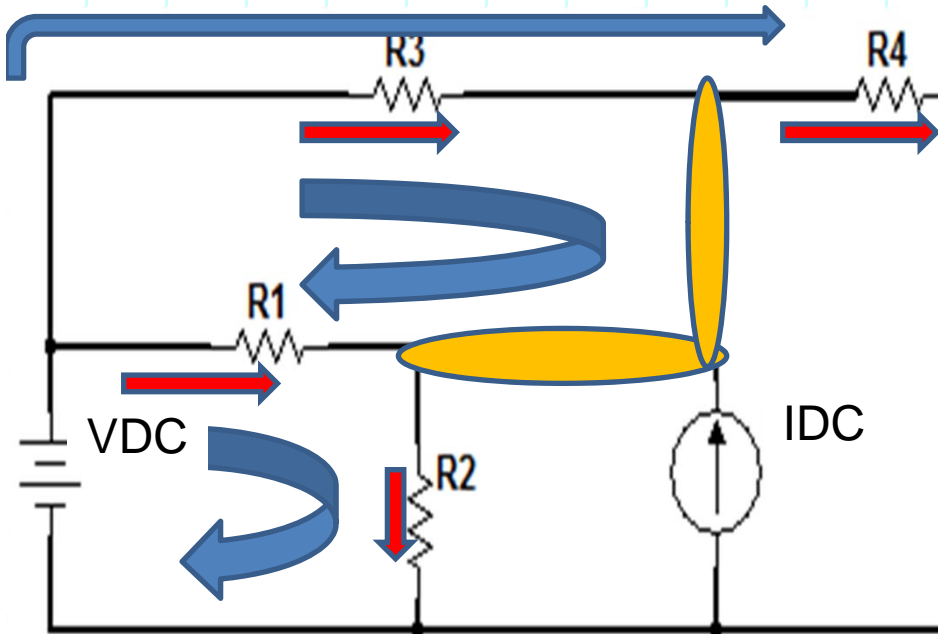

$$-V_{DC} + I_1 R_1 + I_2 R_2 = 0$$

$$I_3 R_3 - I_1 R_1 = 0$$

$$-V_{DC} + I_3 R_3 + I_4 R_4 = 0$$

$$I_3 - I_4 + I_1 - I_2 + I_{DC} = 0$$

$R_1$	$R_2$	0	0	$I_1$	=	$V_{DC}$
$-R_1$	0	$R_3$	0	$I_2$		0
0	0	$R_3$	$R_4$	$I_3$		$V_{DC}$
1	-1	1	-1	$I_4$		$-I_{DC}$

Next, use Gaussian Elimination

OR

Matlab matrix solution

# Kirchhoff's Current Law (KCL)

**Sum of currents entering a node = 0**

**OR**

$$i_1 - i_2 - i_3 + i_4 = 0$$

**Sum of currents leaving a node = 0**


**OR**

$$-i_1 + i_2 + i_3 - i_4 = 0$$

**Sum of currents leaving = sum of  
Currents entering a node**

$$i_1 + i_4 = i_2 + i_3$$
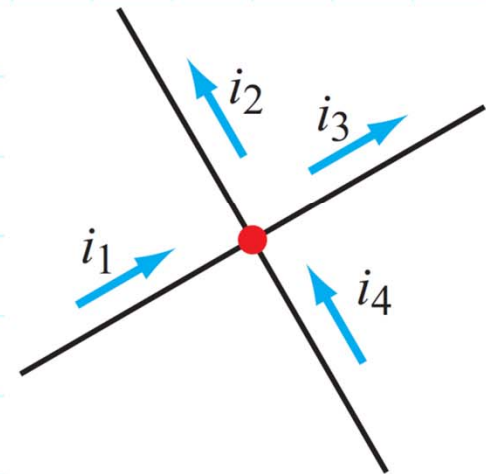
$$\sum_{n=1}^N i_n = 0 \quad (\text{KCL}),$$





# Kirchhoff's Voltage Law (KVL)

**Sum of voltages around a closed path = 0**

**OR**

$$-V_{DC} + V_1 + V_2 = 0$$


**Sum of voltage drops = sum of voltage rises**

$$V_{DC} = V_1 + V_2$$


$$\sum_{n=1}^N v_n = 0 \quad (\text{KVL}),$$
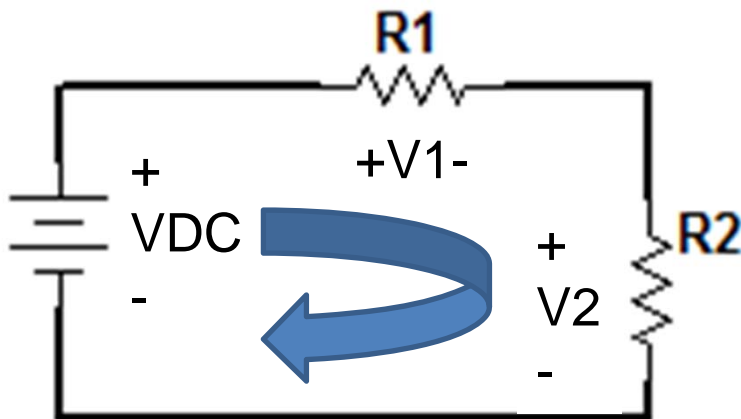
## Sign Convention

- Add up the voltages in a systematic clockwise movement around the loop.
- Assign a positive sign to the voltage across an element if the (+) side of that voltage is encountered first, and assign a negative sign if the (−) side is encountered first.



# KCL and KVL Cookbook

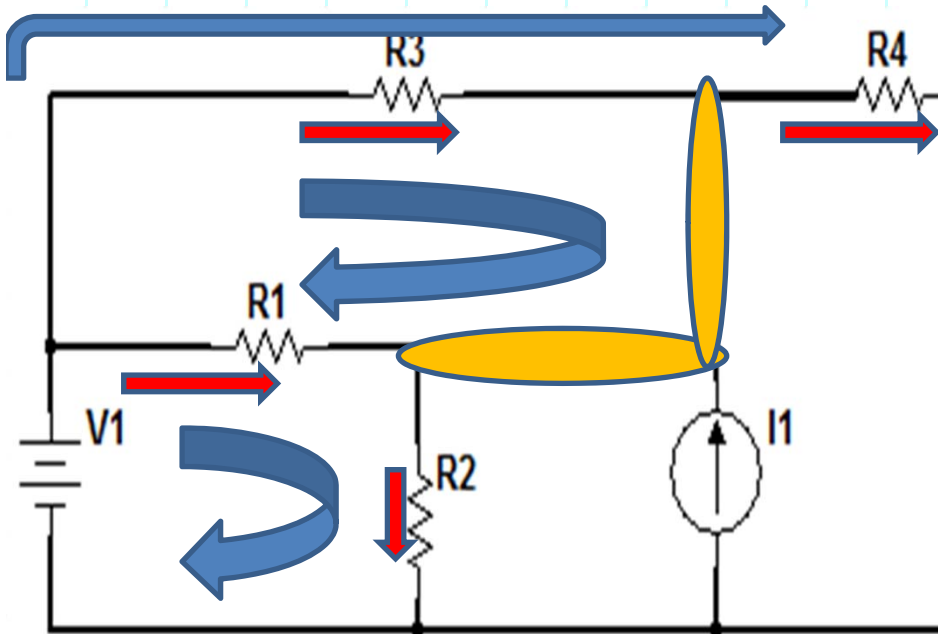

Another Way ...



1. Write all KNOWN values
2. Keep track of all **unknown** values (Need as many independent equations as unknowns)
3. Write all **KVL (Loop)** equations. Each loop must pick up at least one new element. Current sources can't be in loops.
4. Apply Ohm's Law (I prefer to do this 'as I go', for convenience)
5. Apply as many **KCL (node)** equations as needed to fill in unknowns. Each KCL equation must pick up at least one new current. Shorts combine nodes. Nodes touching voltage sources can't be used.
6. Solve for the unknowns.

# Red Canyon (Bottom of Thunder Mountain) Near Bryce Canyon, Utah

