

	Simulation		Hand Analysis	
	Stage 1	Stage 2	Stage 1	Stage 2
$I_C$	93.34mA	47.21mA	94mA	47mA
$I_B$	888.6nA	500nA	900nA	500nA
$I_E$	94.23mA	47.7mA	95mA	48mA
$V_C$	12.67V	12.64V	12.7V	12.6V
$V_B$	2.485V	2.492V	2.5V	2.5V
$V_E$	1.885V	1.909V	2V	2V
Gain	10mV/V	14mV/V	10mV/V	14mV/V

Full circuit Gain = 85

$R_{in}$ :

$$I_{in} = \frac{2.485197250 - 2.48430902}{1k}$$

$$= 888.23\text{nA}$$



$$R_{in} = \frac{2.48430902}{888.23\text{nA}}$$

$$= 2.796\text{M}\Omega$$

Stage 1

$$\underline{R_{out}}: = \frac{12.6396 - 87.4\text{mV}}{87.4\text{mV}} \cdot 50\text{k} = 7.23\text{k}\Omega$$

Stage 2

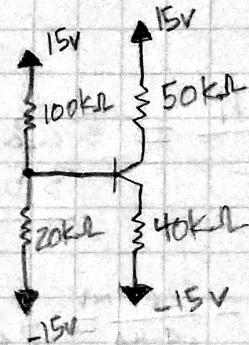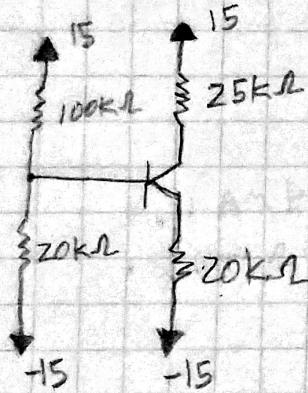

$$V_{Th} = \frac{(15)(20\text{k}\Omega) - (15)(100\text{k}\Omega)}{100\text{k} + 20\text{k}} = -10\text{V}$$


$$V_{Th} = \frac{15(20\text{k}) - 15(100\text{k}\Omega)}{100\text{k} + 20\text{k}\Omega}$$

$$= -10\text{V}$$

$$R_{Th} = 16.6\text{k}\Omega$$

$$-10 - I_B(16.6\text{k}) - 0.7 - I_E(40\text{k}) \stackrel{H(s)}{=} 0$$
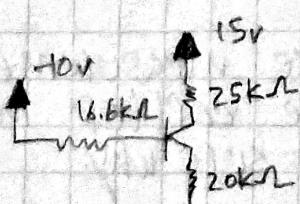
$$R_{Th} = \frac{100\text{k} \cdot 20\text{k}}{100\text{k} + 20\text{k}} = 16.6\text{k}\Omega$$



$$V_{B_1} = -10 - (16.6\text{k}\Omega I_B) = -15\text{V}$$

$$V_{E_1} = 2\text{V}$$

$$V_{C_1} = 15 - I_C(25\text{k}\Omega) = 12.7\text{V}$$

$$V_T = -15\text{V}$$

$$V_{E_2} = 2\text{V} \quad I_{E_2} = 148\text{mA}$$

$$V_{B_2} = -2.5\text{V} \quad I_{B_2} = 500\text{nA}$$

$$V_{C_2} = 12.6\text{V} \quad I_{C_2} = 47\text{mA}$$


$$-10 - I_B(16.6\text{k}\Omega) + 15 = .7 - I_E(20\text{k}\Omega) = 0$$

$$I_{E_1} \left( \frac{-16.6\text{k}\Omega}{10\Omega} - 20\text{k}\Omega \right) = -4.3 = 295\text{mA}$$

$$I_{B_1} = \frac{I_E}{10\Omega} = 900\text{nA}$$

$$I_C = 94\text{mA}$$

## Full circuit

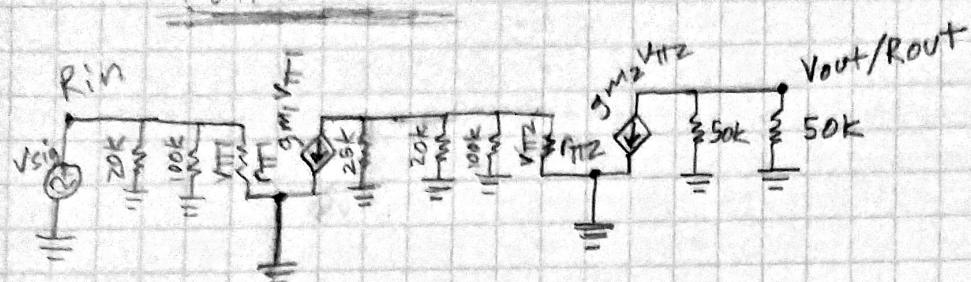

$$V_{out} = \frac{(g_{m2}v_{\pi2})(50k)}{50k+50k} (50k)$$

\* Don't know how  
to find exact


$$R_{out} = 50k \parallel 50k = 25k \Omega$$

$$R_{in} = (20k \parallel 100k) \parallel r_{\pi1} = \frac{16.6k(r_{\pi1})}{16.6k + r_{\pi1}}$$

values without any  
given variables.

$$v_{\pi2} = \frac{(g_{m1}v_{\pi1})(100k \parallel r_{\pi2})}{25k \parallel 20k + 100k \parallel r_{\pi2}}$$
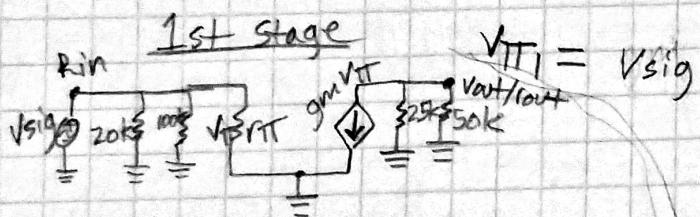
$$r_{\pi2} = \frac{(g_{m1}v_{\pi1}) \frac{(100k)(r_{\pi2})}{100k + r_{\pi2}}}{11.11k + \frac{(100k)(r_{\pi2})}{100k + r_{\pi2}}}$$




$$V_{out} = \frac{(g_m v_{\pi})(25k)}{75k} (50k)$$

$$v_{\pi} = v_{sig}$$

$$\frac{V_{out}}{V_{sig}} = \frac{(g_m)(25k)}{75k} (50k)$$

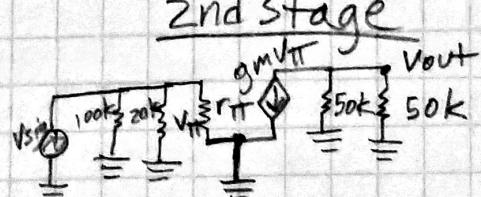
$$\frac{V_{out}}{V_{sig}} = (g_{m2}) \frac{\frac{(100k)(r_{\pi2})}{100k + r_{\pi2}}}{11.11k + \frac{(100k)(r_{\pi2})}{100k + r_{\pi2}}} \frac{100k}{50k}$$



$$V_{out} = \frac{(g_m v_{\pi}) 50k}{50k}$$


$$\frac{V_{out}}{V_{sig}} = \frac{(g_m) 50k}{100k} \frac{100k}{50k}$$

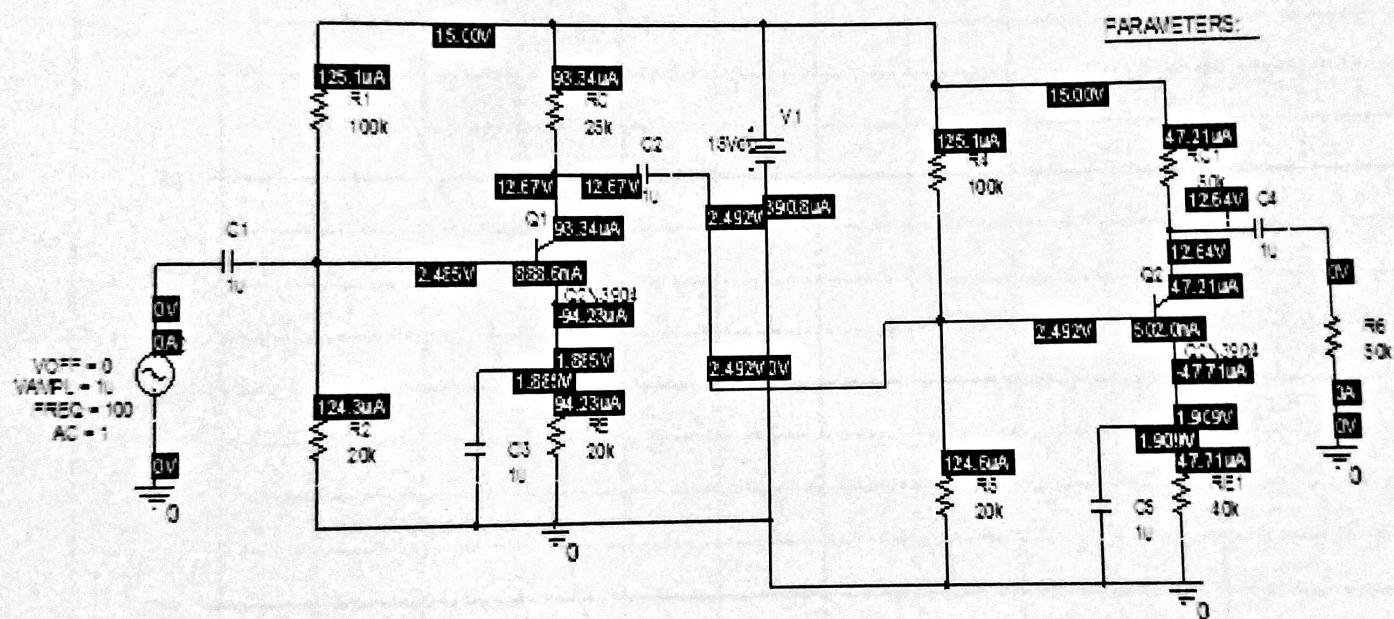Verification of DC voltages and currents for active mode.




(A) Lab3 Experiment 2 Sim. (active)


Impedance Vs. Frequency

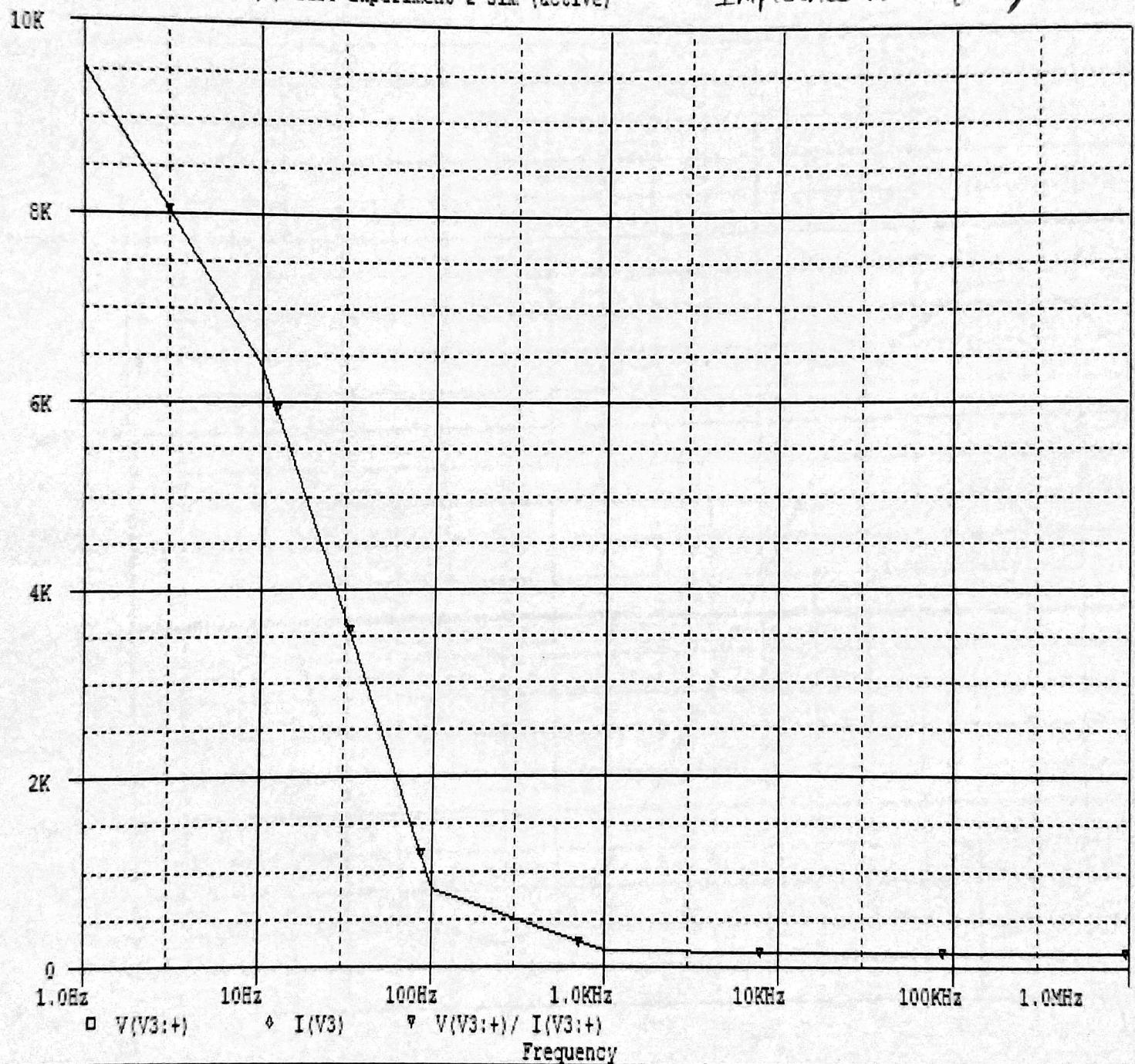

(a) Lab3 Experiment 2 Sim (active)

Gain at 100Hz

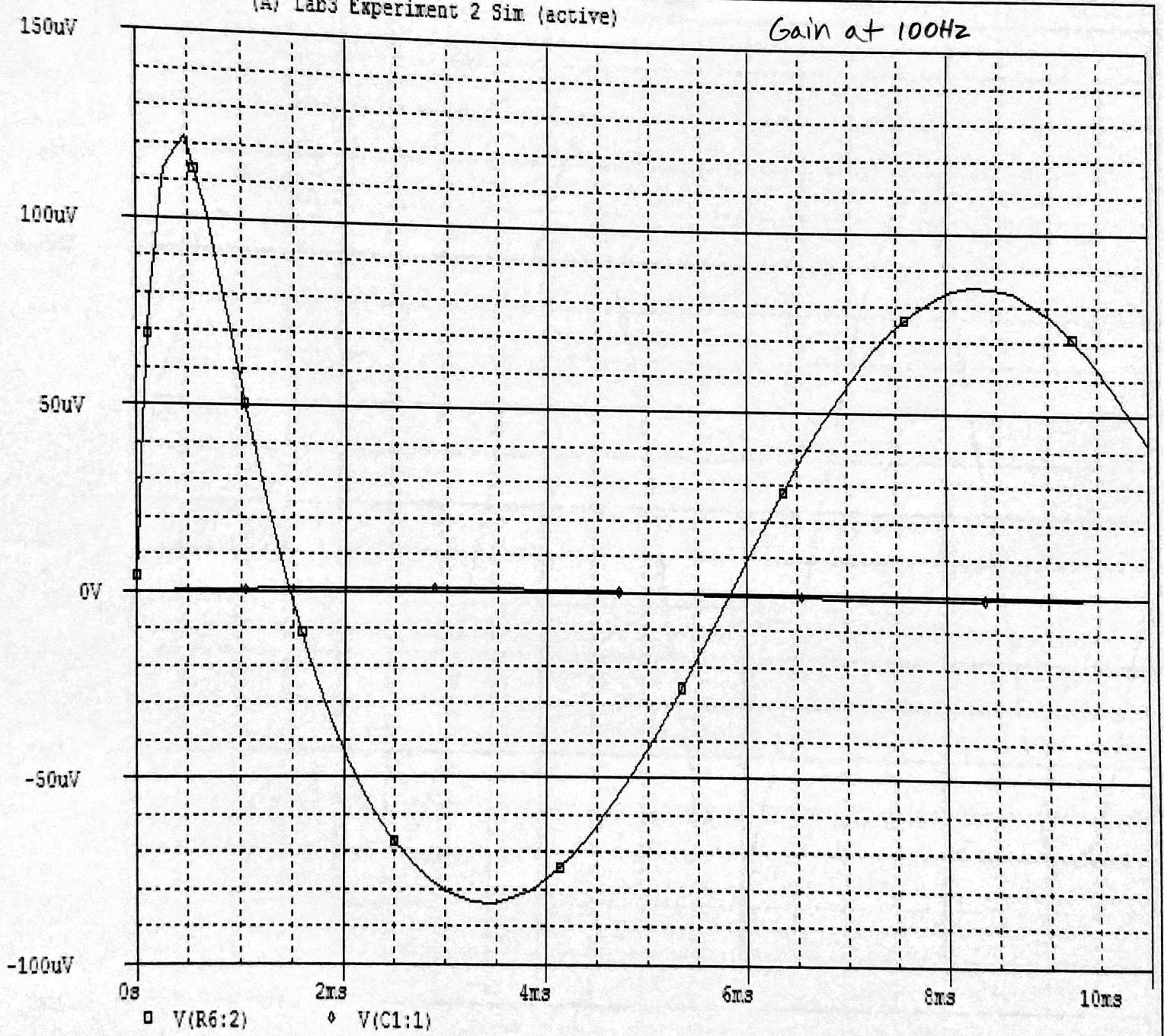

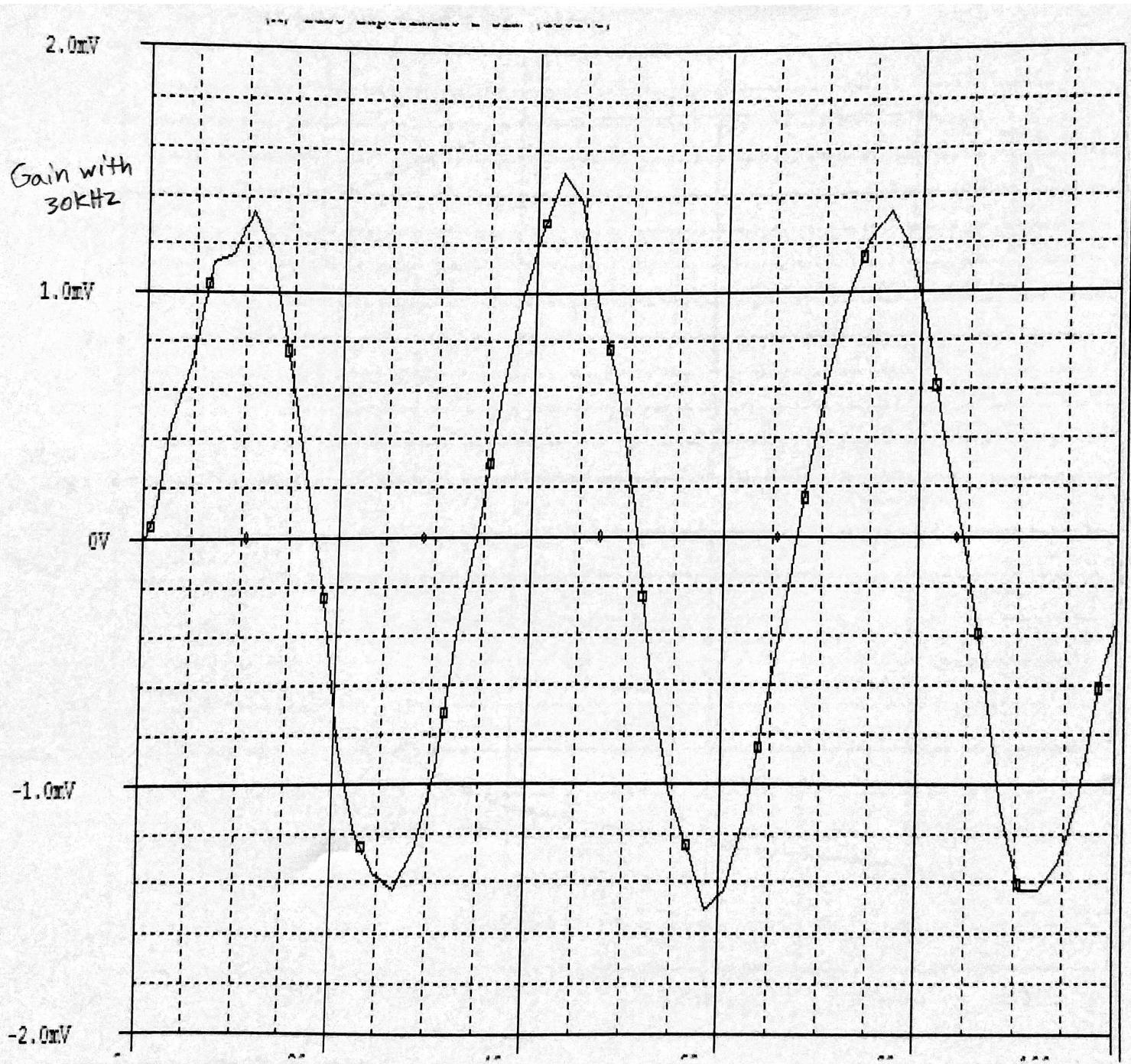

(A) Lab3 Experiment 2 Sim (active)

