

Lab #3 BJT Transistors

Nathan Donaldson 2/17/16
ECE2280

Parts

100 μ F capacitor
0.1 μ F capacitor

Experiment 1: Transistor Diode Test

a) Lead 2 is the base

b)

Transistor is a PNP resistor because base is - lead in both cases.

c)




From transistor diagram, the assumptions are correct.

d)

This is useful for finding the type of transistor you will be using.

Experiment 2: DC operation of BJT

1.

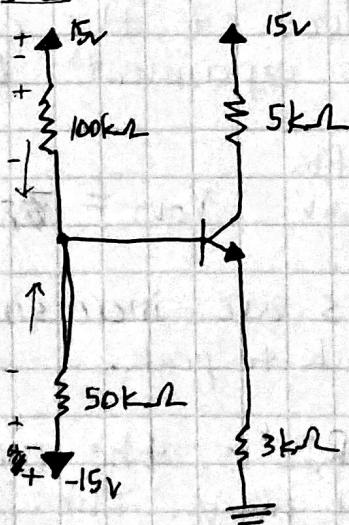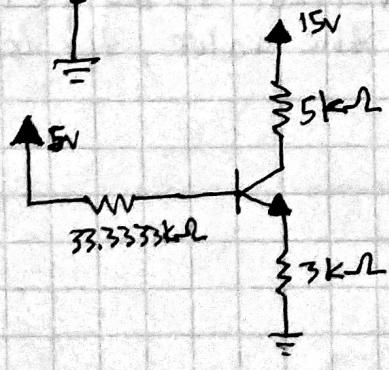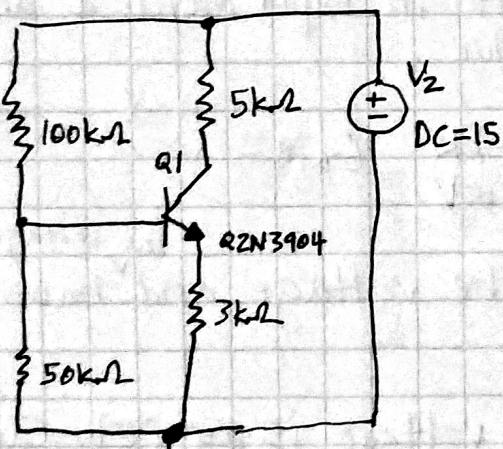

$$V_{Th} = \frac{15V(100k\Omega) - 15V(50k\Omega)}{100k\Omega + 50k\Omega} = 5V$$

$$R_{Th} = \frac{100k\Omega \cdot 50k\Omega}{100k\Omega + 50k\Omega} = 33.333k\Omega$$

$$5V - I_B(33.333k\Omega) - I_E(3k\Omega) - 0.7V = 0$$

$$I_E \left(\frac{33.333k\Omega}{15V} - 3k\Omega \right) = -4.3V$$

$$I_E = 1.3mA$$

$$I_B = \frac{1.3}{15V} = 8.8mA$$

$$I_C = 8.8mA \cdot 150 = 1.3mA \quad V_C = 15 - 1.3mA(5k\Omega) = 8.5V$$


2N3904


		RED + - BLK	Meter shows conduction?
1	2		
1	3	open	open 0.7V
2	3	open	open open
2	1	open	open
3	1	open	
3	2	.7V	

Nathan


3/4/2016

Printing Photo

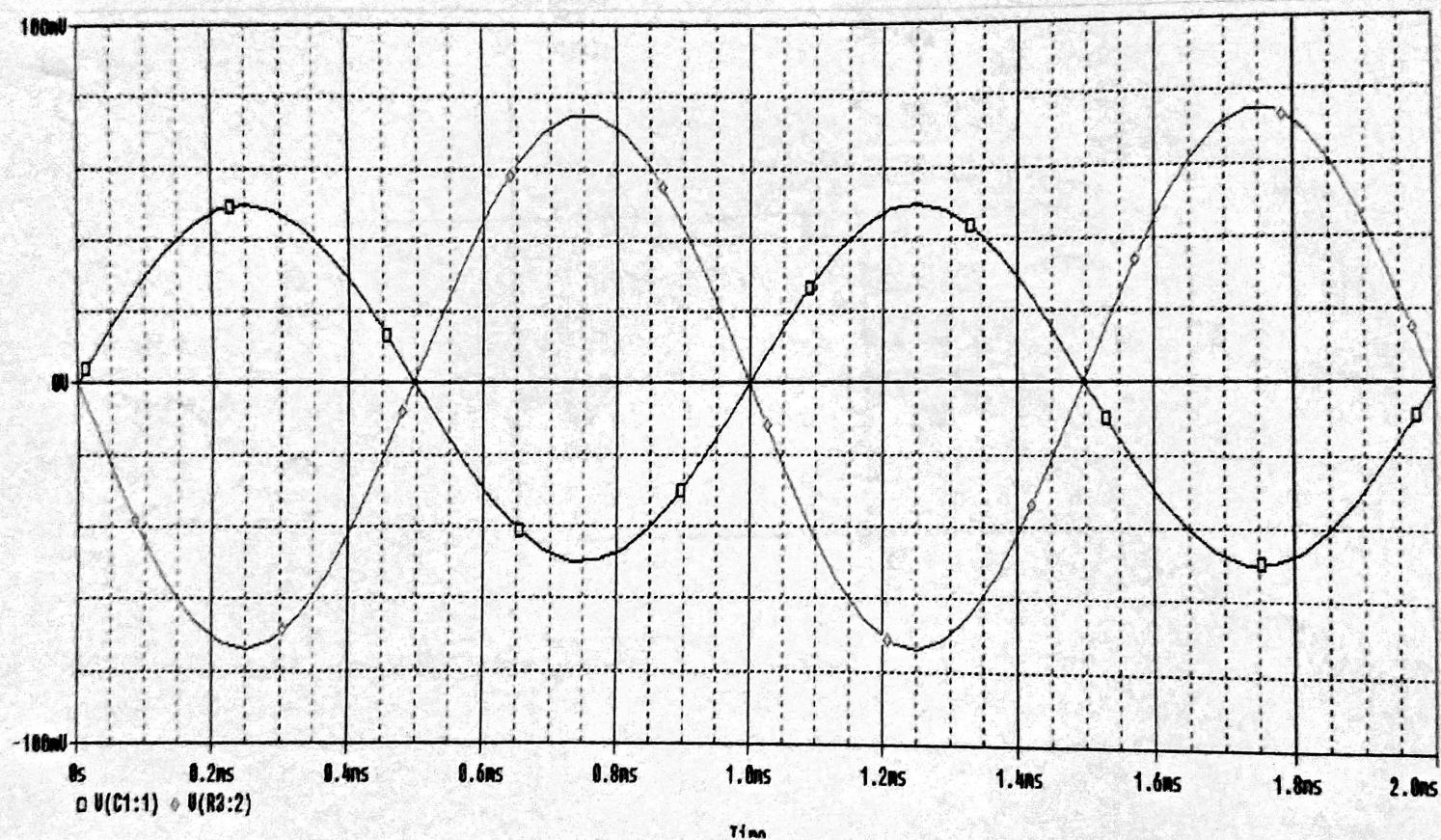

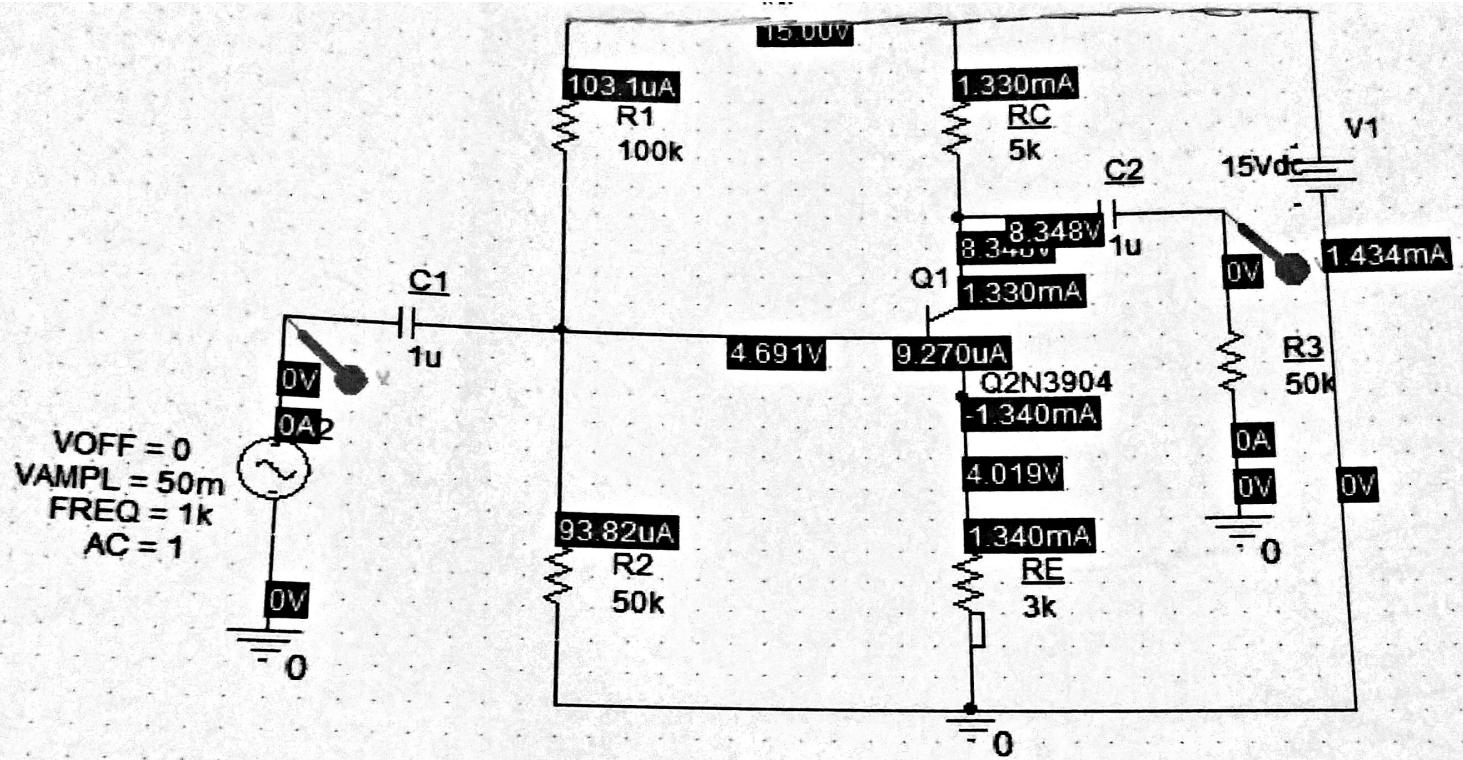

Values are same for DC attributes.

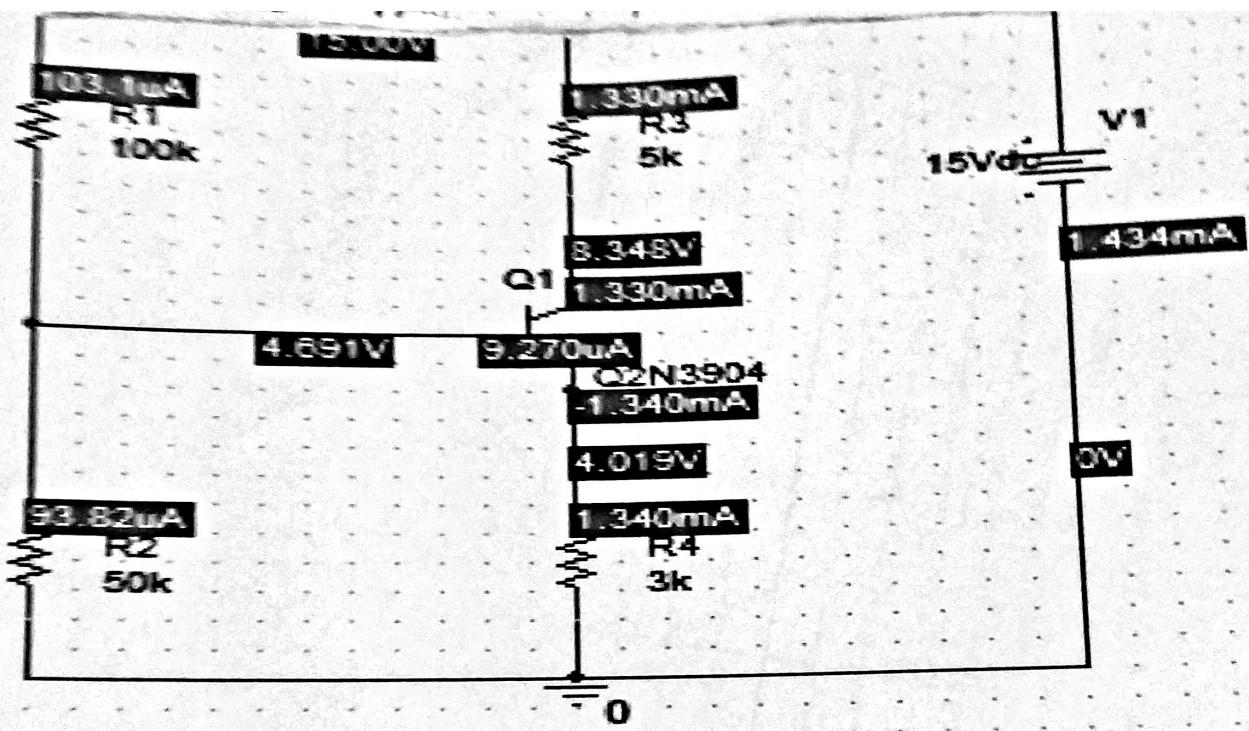

I_E is about the same as hand analysis.

I_B is a little higher on here compared to hand analysis's.

I_C is about the same as hand analysis's.

V_B is about the same as hand analysis's.

V_E is about the same as hand analysis's.

V_C is a little lower compared to hand analysis's.

$$3. V_B = 4.6V \quad 5 - I_B (33.333k\Omega) = 4.6V$$

3/3/16

$$V_C = 6.6V$$

$$I_B = 12mA$$

$$V_E = 4V$$

$$I_B = \frac{I_E}{151}$$

$$I_E = I_B (151)$$

$$15 - I_C (5k) = 6.6V$$

$$I_E = 1.8mA$$

$$I_C = 1.7mA$$

I_E is higher in the ^{physical} measurements.

I_B is also higher in the physical measurements.

I_C is a little bit higher in the physical measurements.

Experiment 3: Simulations

1.

The DC values of the circuit in experiment 1 are the same as this experiment's DC values.

$$\text{Vin} = 100mV \quad V_{out} = 74mV \quad \text{Gain} = \frac{74mV}{100mV} = 7.4$$

2. The capacitors are increasing the voltage and have a smaller peak to peak.

3. The higher R_2 is, the more voltage is output. Same for the other way. The lower the value, the lower the voltage.


4.

Matthew D

3/4/2016


Printing Photo

3.

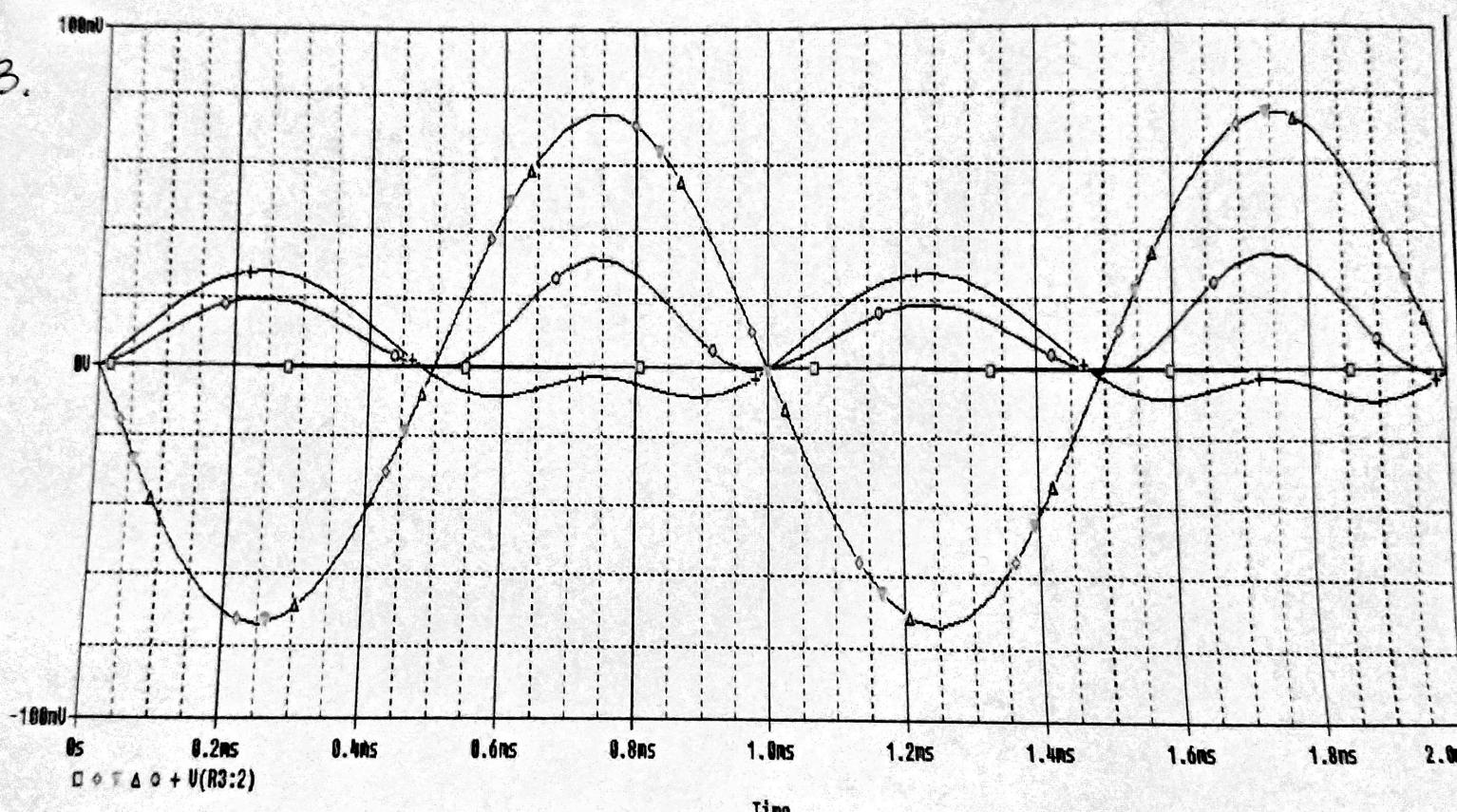

3/4/2016

Printing Photo

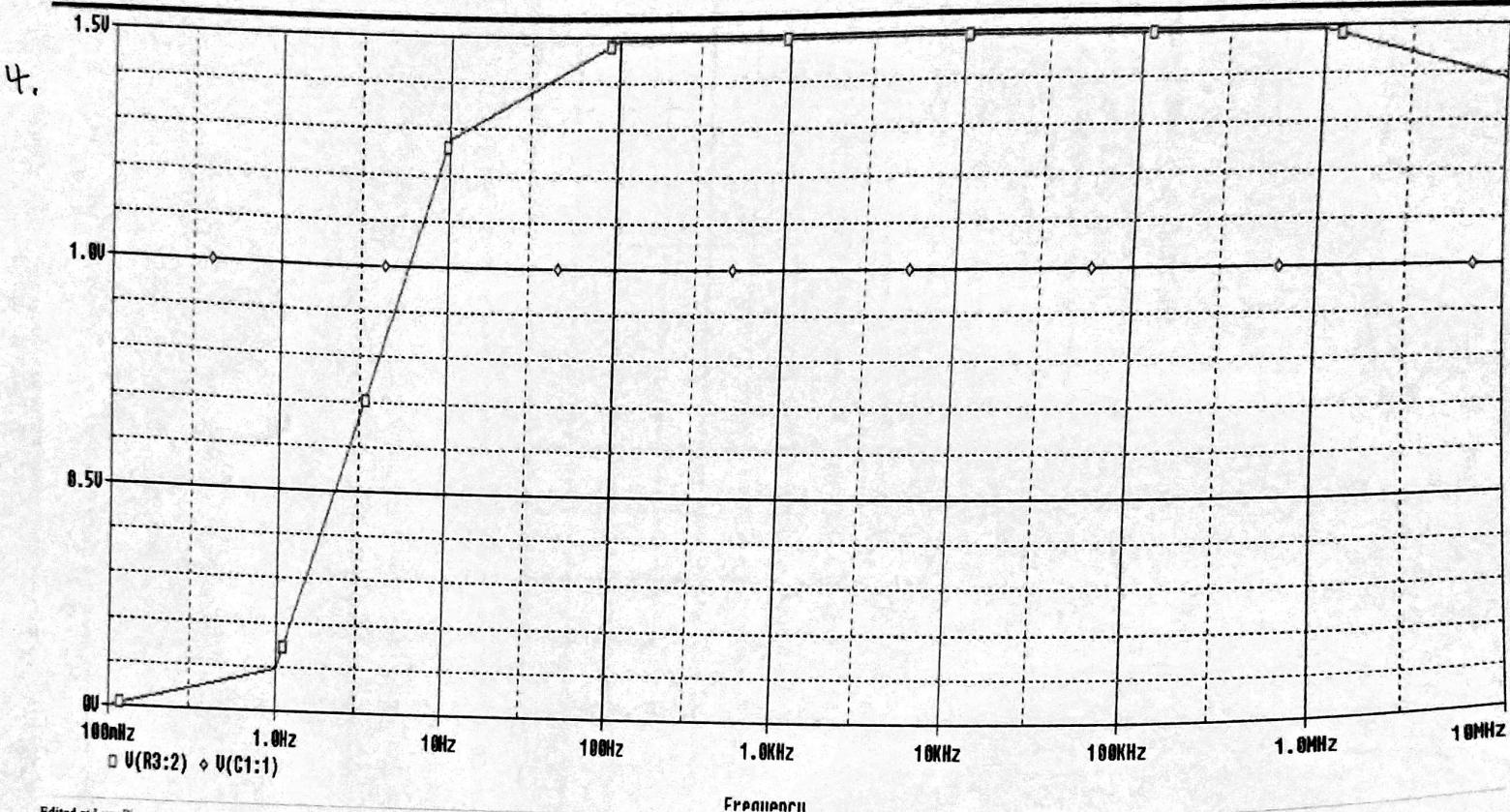


Edited at [LunaPic.com](#)

$$g_{\text{min}} = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1.5}{1} = 1.5$$

** Profile: "SCHEMATIC1-Lab3 Experiment 2 Sim" [C:\OrCAD\OrC...
Date/Time run: 03/03/16 12:49:15

Temperature: 27.0

(A) Lab3 Experiment 2 Sim (active)

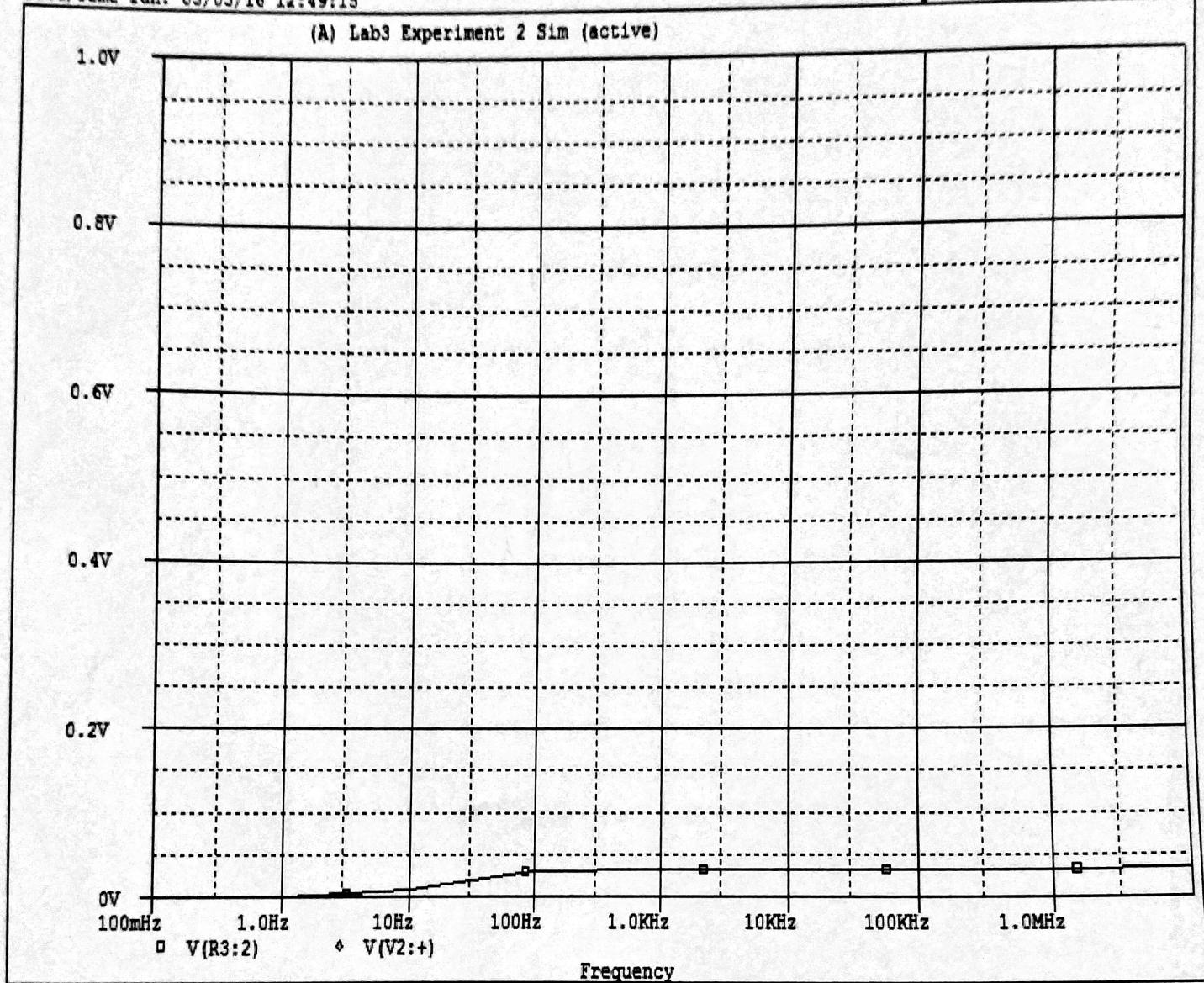

Date: March 03, 2016

Page 1

Time: 12:51:33

	Gain	Rin	Rout
Sim	1.5*	92.8Ω	1.0433MΩ
Meas	1.5	106kΩ	69.45MΩ

* Everybody's seems to be way off.

5. why is it attenuating?

Basic Ohm's law: The resistance is lower, therefore the voltage drop is smaller. $V = I \cdot R$.

6.

$$I_{in} = \frac{V_{test} - V_{in}}{R_{test}} \quad R_{in} = \frac{V_{in}}{I_{in}}$$

$$V_{in} = 4.64V$$

$$V_{test} - V_{in} = 320mV$$

$$R_{in} = \frac{4.64V}{50mA} = 92.8\Omega$$

7.

$$R_o = \frac{V_{Th} - V_L}{V_L} \cdot 50k \quad V_{Th} = 0 \quad V_L = 75mV$$

?

$$\frac{1.64V - 75mV}{75mV} \cdot 50k = 1.0433M\Omega$$

Pk-to-Pk voltage at Rout is 150mV

Experiment 3: Measurements of BJT Circuits

1.

$$\begin{aligned}\text{Peak-to-Peak of } V_{in} &= 103\text{mV} \\ \text{Peak-to-Peak of } V_{out} &= 155\text{mV}\end{aligned}$$

$$\text{Gain} = 1.5$$

2.

$$(1.5)(0.708) = 1.062$$

$$\text{Gain} = 1.062$$

$$\frac{103}{V_{out}} = 1.062$$

$$\text{Peak-to-Peak of } V_{out} = 96.98\text{mV}$$

3.

23.3 Hz is the starting frequency for the bandwidth of the circuit with a V_{in} of 103mV and V_{out} of 96.98mV.
(Peak-to-Peak) (Peak-to-Peak)

4.


$$I_{in} = \frac{V_{test} - V_{in}}{2k} = \frac{5.4\text{mV} - 5.3\text{mV}}{2k} = 50\text{nA} \quad R_{in} = \frac{5.3\text{mV}}{50\text{nA}}$$

R_{in} is off by a factor $R_{in} = 106k$ of 1k, so very far off

$$R_o = \frac{8.34\text{V} - 6\text{mV}}{6\text{mV}} \cdot 50\text{k} = 69.45\text{M}\Omega$$

About 68 million more than in the simulation. A little better.

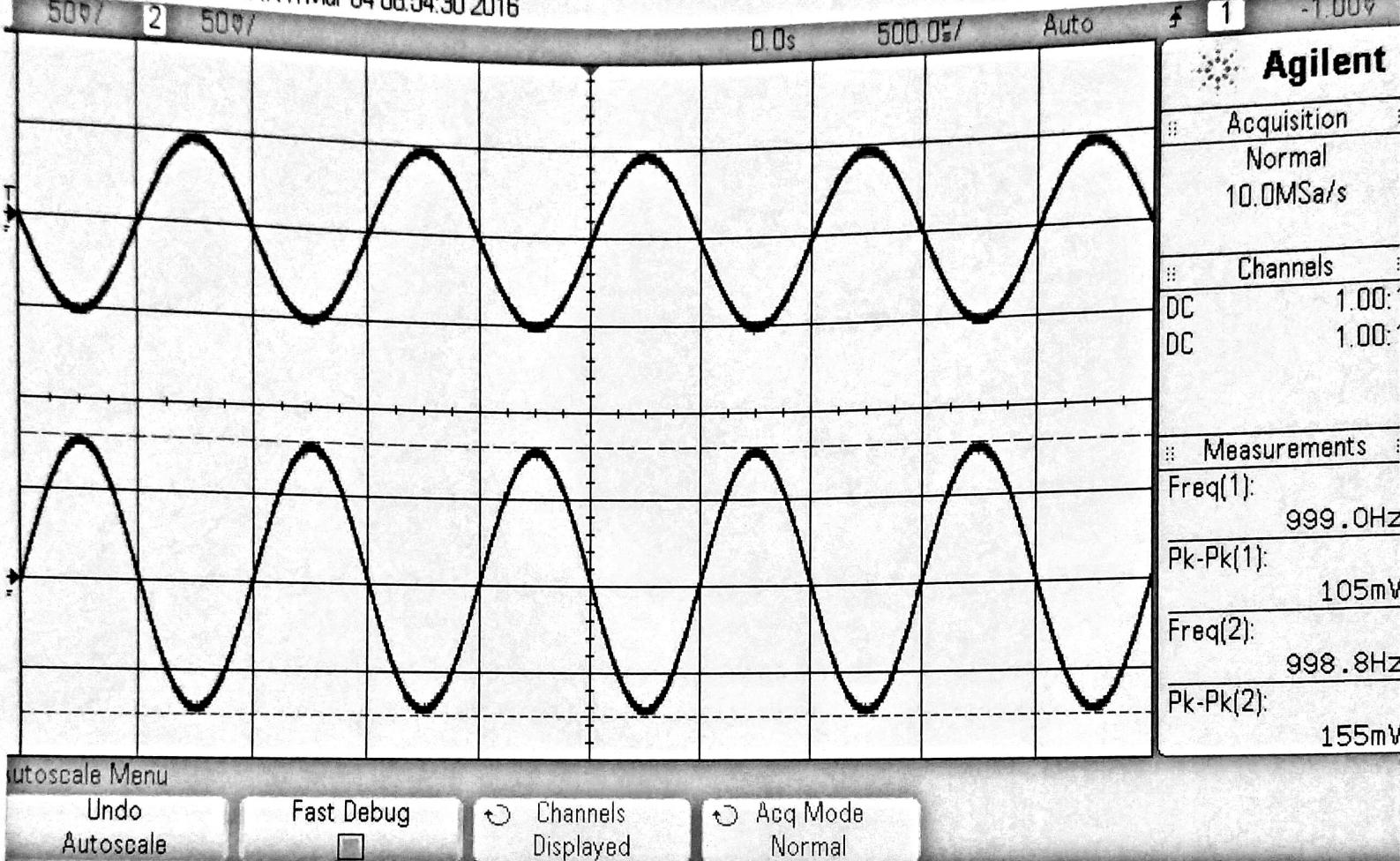SO-X 2012A, MY53400844: Fri Mar 04 06:54:30 2016



5

$$V_{out} = 840mV$$

$$V_{in} = 60mV$$

$$\text{Gain} = \frac{840mV}{60mV} = 14$$

The gain is much higher due to the capacitor in the Emitter.

6. $\frac{V_{out}}{V_{in}} = \frac{102mV}{102mV} = 1$

$$\frac{R_{in}}{I_{in}} = \frac{V_{test} - V_{in}}{R_{test}} = \frac{35.1mV - 26.1}{10k} = .9mA$$

$$R_{in} = \frac{26.1mV}{.9mA} = 29k\Omega$$

R_{out} :

$$R_{out} = \frac{V_{Th} - V_L}{V_L} \cdot R_L = \frac{35.2mV - 35.18mV}{35.18mV} \cdot 50k = 28\Omega$$

The R_{in} value seems to be close to the given simulation and so does the R_{out} .

* It seems a lot of the resistance measurements are off by a lot for many people in the earlier measurements. I asked a few TA's and they are not sure why.

Also, grading rubric didn't make sense.