

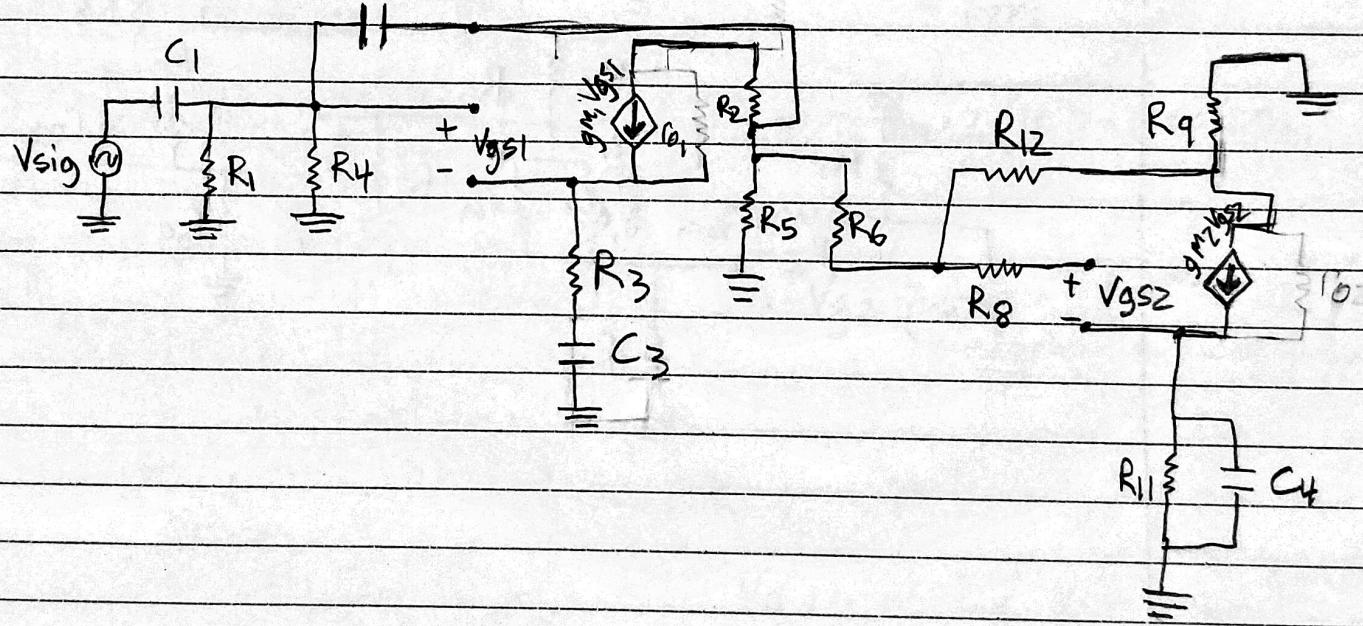


Homework 8


1.

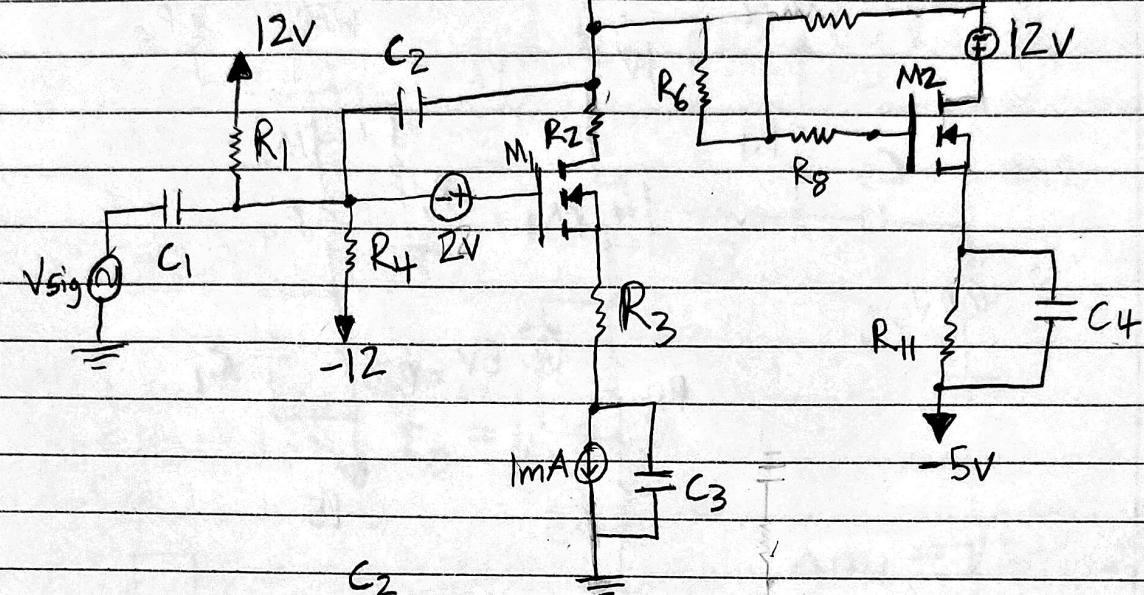

2.

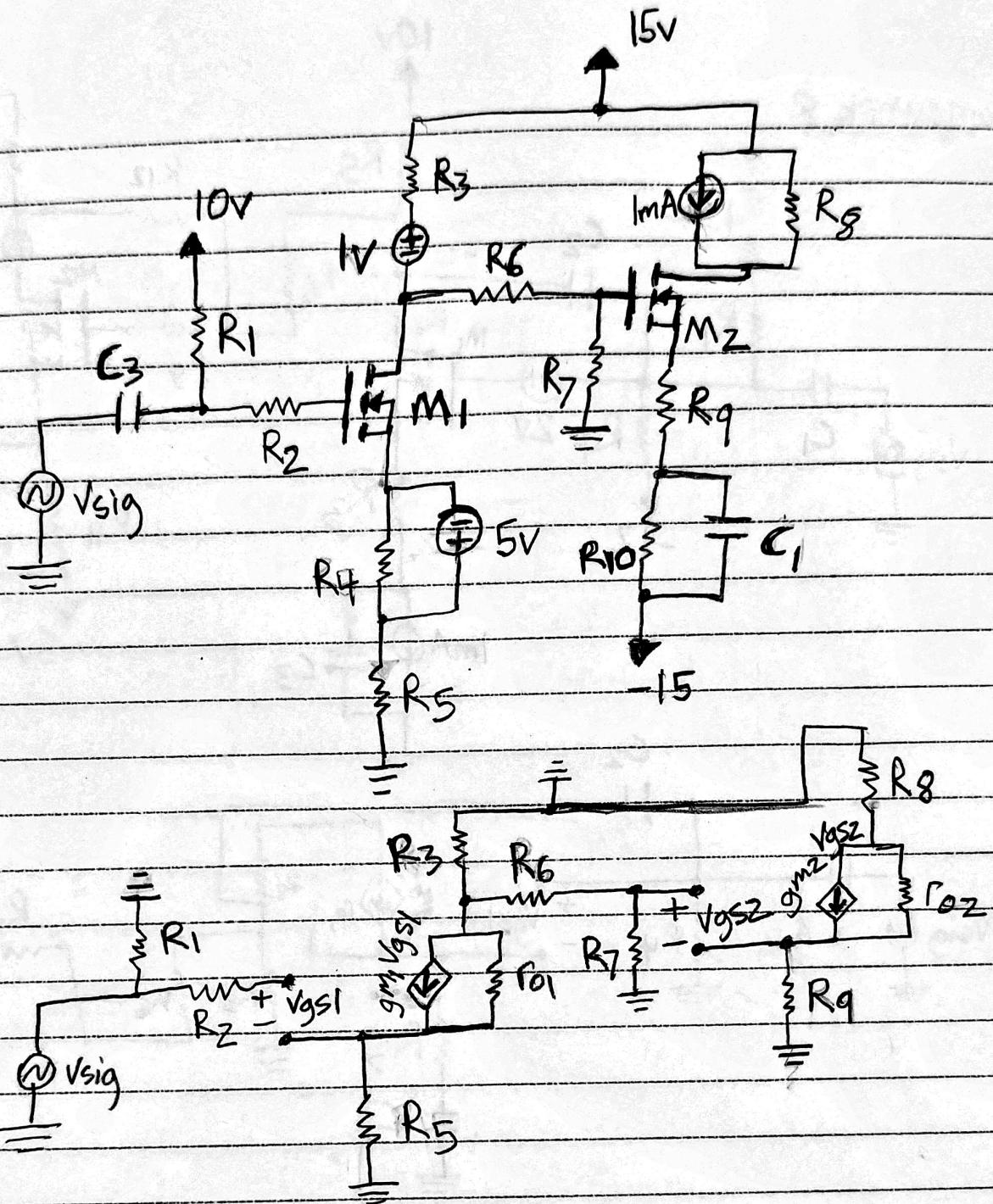

3.

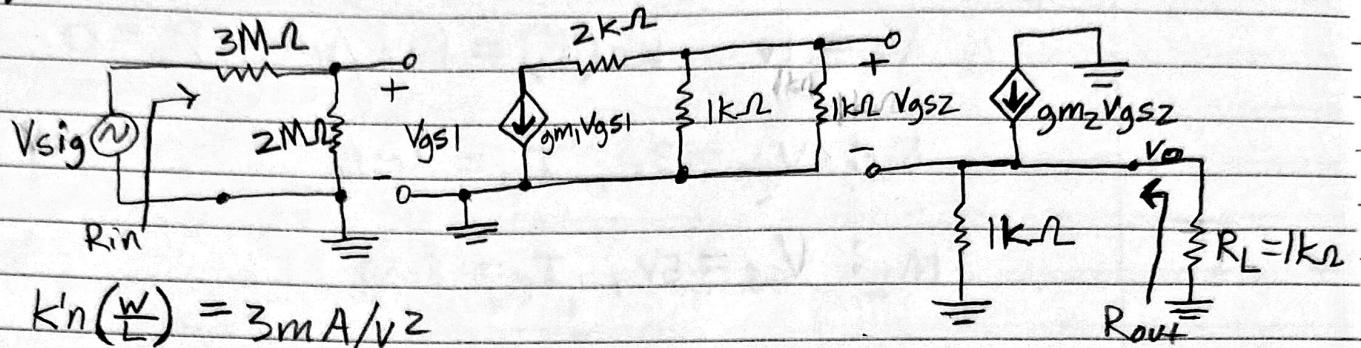

$$k' n \left( \frac{w}{L} \right) = 3 \text{ mA}/\sqrt{2}$$

$$M_1: V_{GS} = 4V, I_D = 6\text{mA}$$

$$M_2: V_{GS} = 5.3V, I_D = 16.7\text{mA}$$

$$\lambda = 0$$

$$g_{m1} = \sqrt{3m \cdot 2(6\text{m})} \\ = 6\text{m}$$

$$a) R_{in} = 5M\Omega$$

$$b) R_{out} = 1k\Omega \parallel \frac{1}{g_{m2}} \\ = 9\Omega$$

$$g_{m2} = \sqrt{3m \cdot 2(16.7\text{m})} = 10\text{m}$$

c)

$$V_{g2} = (-6\text{m}) \left( \frac{2M(V_{sig})}{5M} \right) \left( \frac{1}{1M} \right) \\ = -1.2V_{sig}$$

$$V_o = \frac{-g_{m2}V_{GS2}(1k\Omega)}{2k} \cdot 1k$$

$$V_{GS2} = V_{g2} - V_{S2}$$

$$V_{S2} = V_o$$

$$V_{GS2} = -1.2V_{sig} - V_o$$

$$V_o = \frac{(10\text{m})(-1.2V_{sig} - V_o)(1\text{M})}{2k}$$

$$V_{g2} = \frac{-g_{m1}V_{GS1}(1k\Omega)}{2k} (1k)$$

$$V_o = \frac{-12kV_{sig} - 10kV_o}{2k}$$

$$V_{GS1} = V_{g1} - V_{S1}$$

$$V_{S1} = 0$$

$$V_o = 6V_{sig} - 5V_o$$

$$V_{g1} = \frac{2M(V_{sig})}{5M}$$

$$6V_o = -6V_{sig}$$

$$-V_o = V_{sig}$$


$$-\frac{V_o}{V_{sig}} = 1$$

$$\boxed{\frac{V_o}{V_{sig}} = -1}$$

$$4. V_t = 1V \quad k_n(w) = 1mA/V^2 \quad \lambda = 0$$

$$M_1: V_{GS} = 3V, I_D = 2mA$$

$$M_2: V_{GS} = 5V, I_D = 8mA$$

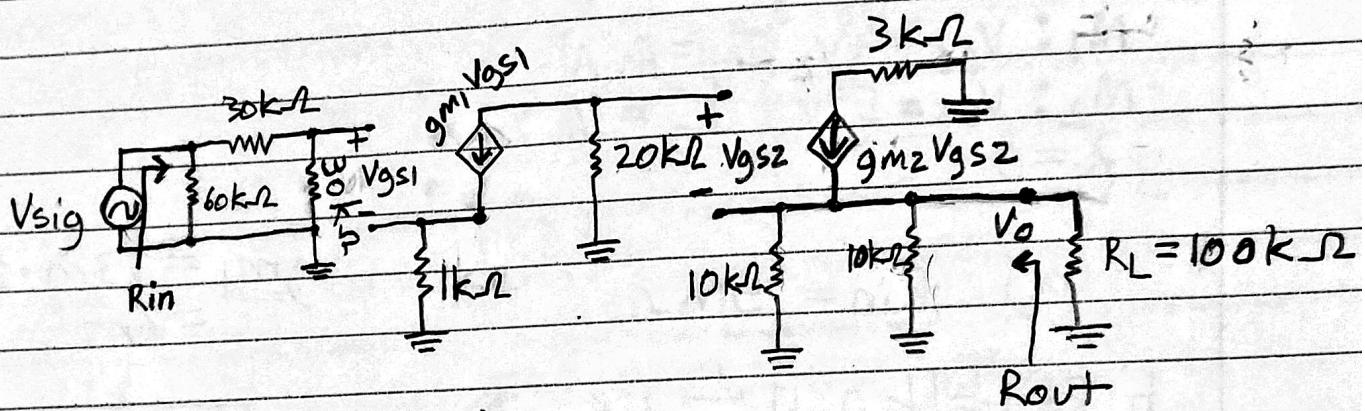

$$a) R_{in} = 60k \parallel 60k = 30k$$

$$b) R_{out} = 10k \parallel 10k \parallel \frac{1}{gm_2}$$

$$= 5k \parallel \frac{1}{gm_2}$$

$$= 238\Omega$$

$$gm_2 = 1mA(5V - 1V)$$

$$= 4mA$$

$$c) V_o = \frac{gm_2 V_{GS2}(5k)}{105k} (100k) = 19V_{GS2}$$

$$V_{GS2} = V_g - V_{S2}$$

$$V_{S2} = V_o \quad V_{S2} = \frac{gm_2 V_{GS2} (100k)}{105k} (5k) = 19V_{GS2}$$

$$V_g = -gm_1 V_{GS1} (20k)$$

$$= -V_{GS1} (40)$$

$$gm_1 = 1mA(3V - 1V)$$

$$= 2mA$$

$$V_{gs1} = V_{g1} - V_{s1}$$

$$V_{s1} = g_m V_{gs1} (1k) = 2 V_{gs1}$$

$$V_{g1} = \frac{V_{sig}(30k)}{60k} = \frac{V_{sig}}{2}$$

$$V_{gs1} = \frac{V_{sig}}{2} - 2 V_{gs1}$$

$$3 V_{gs1} = \frac{V_{sig}}{2}$$

$$V_{gs1} = \frac{V_{sig}}{2}$$

$$V_{gs2} = \left(-\frac{V_{sig}}{2}\right) 40 - 19 V_{gs2}$$

$$20 V_{gs2} = -20 V_{sig}$$

$$V_{gs2} = -V_{sig}$$

$$V_o = 19 (-V_{sig})$$


$$\frac{V_o}{V_{sig}} = -6.35V$$

5.

$$V_t = 1V, k_n \left( \frac{W}{L} \right) = 2mA/V^2, \lambda = 0$$

$$M_1: V_{GS} = 1.5V, I_D = 0.25mA$$

$$M_2: V_{GS} = 13.5V, I_D = 156.25mA$$

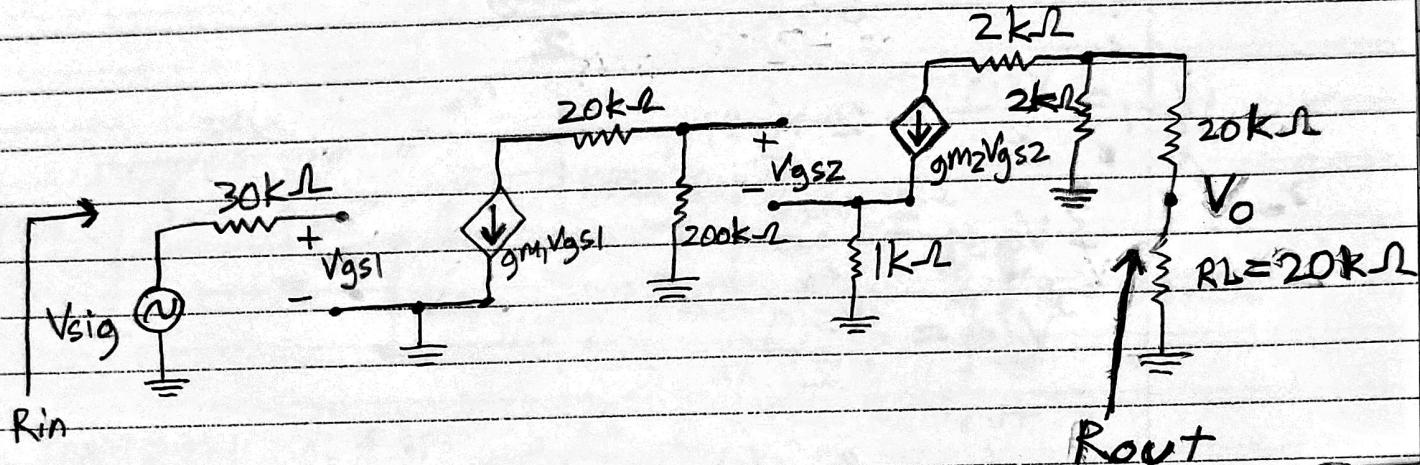

$$a) R_{in} = 0$$

$$b) R_{out} = 20k + 2k \\ = 22k\Omega$$

$$gm_2 = \sqrt{2mA(2)(156.25mA)} \\ = 25m$$

$$c) V_o = \frac{-gm_2 V_{GS2} (2k)}{40k} (20k) = -25V_{GS2}$$

$$V_{GS2} = V_g - V_{S2}$$

$$gm_1 = \sqrt{2mA(2)(0.25mA)} \\ = 1m$$

$$V_o = V_{S2} = gm_2 V_{GS2} (1k) = 25V_{GS2}$$

$$V_g = -gm_1 V_{GS1} (200k) \\ = -200V_{GS1}$$

$$V_{GS1} = V_g - V_{S1}$$

$$V_{S1} = 0$$

$$V_g = V_{sig}$$

$$V_{GS1} = V_{sig}$$

$$V_{g2} = -200 V_{sig}$$

$$V_{s2} = 25 V_{gs2}$$

$$V_{gs2} = -200 V_{sig} - 25 V_{gs2}$$


$$25 V_{gs2} = -200 V_{sig}$$

$$V_{gs2} = -7.7 V_{sig}$$

$$V_o = -25(-7.7 V_{sig})$$

$$V_o = 183 V$$

6.

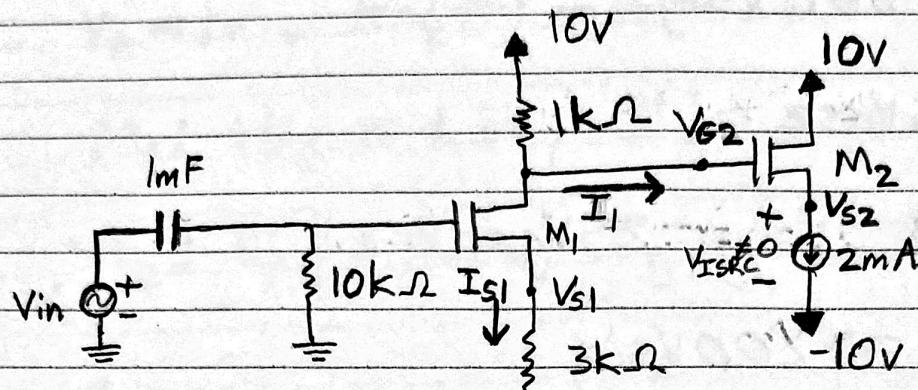

$$V_t = 1V$$

$$k_n \left( \frac{W}{L} \right) = 222 \mu A/V^2$$

$$\lambda = 0$$

$$V_{IN} = 3 + 0.002 \sin(2\omega t) - 10V$$

$$I_s1 = 0 \quad V_{G1} = 9V$$

$$2mA = \frac{1}{2} (222\mu) (9 - (-10 + V_s) - 1)^2$$

$$V_{S2} = 3.755$$

$$V_{G2} = 0$$

$$I_{s1} = \frac{1}{2} (222\mu) (0 - (-10 + 1kI_{s1} + 2 + 3kI_{s1}) - 1)^2$$

$$9009I_{s1} = (7 - 4kI_{s1})^2$$

$$9009I_{s1} = 49 - 28kI_{s1} - 28kI_{s1} + 16M I_{s1}^2$$

$$0 = 16M I_{s1}^2 - 65009 I_{s1} + 49$$

$$\frac{33017.71}{33017.71} I_{s1}$$

$$I_{s1} = \frac{65009 \pm \sqrt{-65009^2 - 4(16M)(49)}}{2(16M)} = 3mA$$

For 3mA:

$$V_{D1} = 10 - 1k(3mA) = 7V$$

$$V_{S1} = -10 + (1k)3mA + 2 + (3k)3mA = 4V$$

$$\frac{V_{DS1}}{7-4} > \frac{V_{GS1}}{(0-4)} - 1$$

$$3 > -5 \quad \checkmark$$

$$\frac{V_{GS1}}{-4} > \frac{V_t}{-1} \quad \times$$

For 1mA:

$$V_{D1} = 10 - 1k(1mA) = 9V$$

$$V_{S1} = -10 + 1k(1mA) + 2 + 3k(1mA) = \boxed{-4V}$$

$$V_{DS1} \geq V_{GS1} - V_t$$

$$9+4 > 4 - 1 \quad \checkmark$$

$$\frac{V_{GS1}}{4} > \frac{V_t}{1} \quad \checkmark$$

$$V_{S2\text{ Max}} = 4(2mA) + 3.755 = 3.763$$

$$V_{S2\text{ Min}} = 3.755 - 4(2mA) = 3.747$$

$$V_{DS2} \geq V_{GS2} - V_t$$

$$10 - 14.755 > (10 - 14.755) - 1 \quad \checkmark$$


$$V_{GS2} \geq V_t$$

$$-5.245 > 1 \quad \checkmark$$

$$V_{S2\text{ total}} = 3.75 - 8m \sin(\omega t)$$

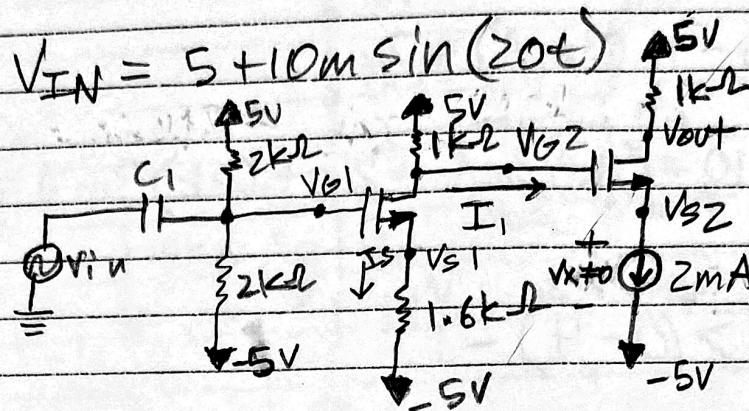7.

$$V_t = 1V \quad k'n(\%) = 1mA/V^2 \quad Z = 0$$



$$V_{G1} = 0$$

$$+5V/V$$

$$I_s = \frac{1}{2} (1mA) (0 - (-5 + 1.6k(I_s)) - 1)^2$$

$$2kI_s = 5 - 1.6k(I_s) - 1$$

$$2kI_s = (4 - 1.6k(I_s))^2$$

$$2kI_s = 16 - 6400(I_s) - 6400(I_s) + 2.56M I_s^2$$

$$0 = 16 - 14800I_s + 2.56M I_s^2$$

$$I_s = \frac{14800 \pm \sqrt{-14800^2 - 4(2.56M)(16)}}{2(2.56M)}$$

7429.7

$$= 4.3mA, \boxed{1.4mA}$$

For 4.3mA:

$$V_{D1} = 5V - 1k(4.3mA) = 700mV$$

$$V_{S1} = -5V + 1.6k(4.3mA) = 1.88V$$

$$1.18 > -1.88 \quad \checkmark$$

$$-1.88 > 1 \quad \times$$

For 1.4mA:

$$V_{D1} = 5 - 1k(1.4mA) = 3.6V$$


$$V_{S2_{\min}} = -5(2mA) + 0.6V = 0.59V$$

$$V_{S1} = -5 + 1.6k(1.4mA) = -2.76$$

$$V_{S2_{\max}} = 0.6V + 5(2mA) = 0.61V$$

$$3.6 + 2.76 > 2.76 - 1 \quad \checkmark$$

$$2.76 > 1 \quad \checkmark$$

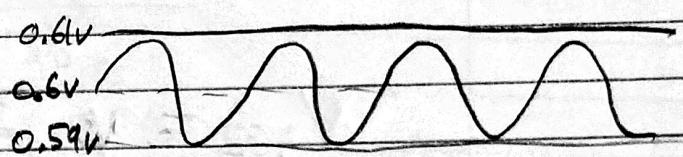


$$V_{G2} = 5 - 1k(1.4mA) = 3.6V$$

$$2mA = \frac{1}{2}(1mA)(3.6 - V_{S2} - 1)^2$$

$$V_{S2} = 0.6V$$

8.

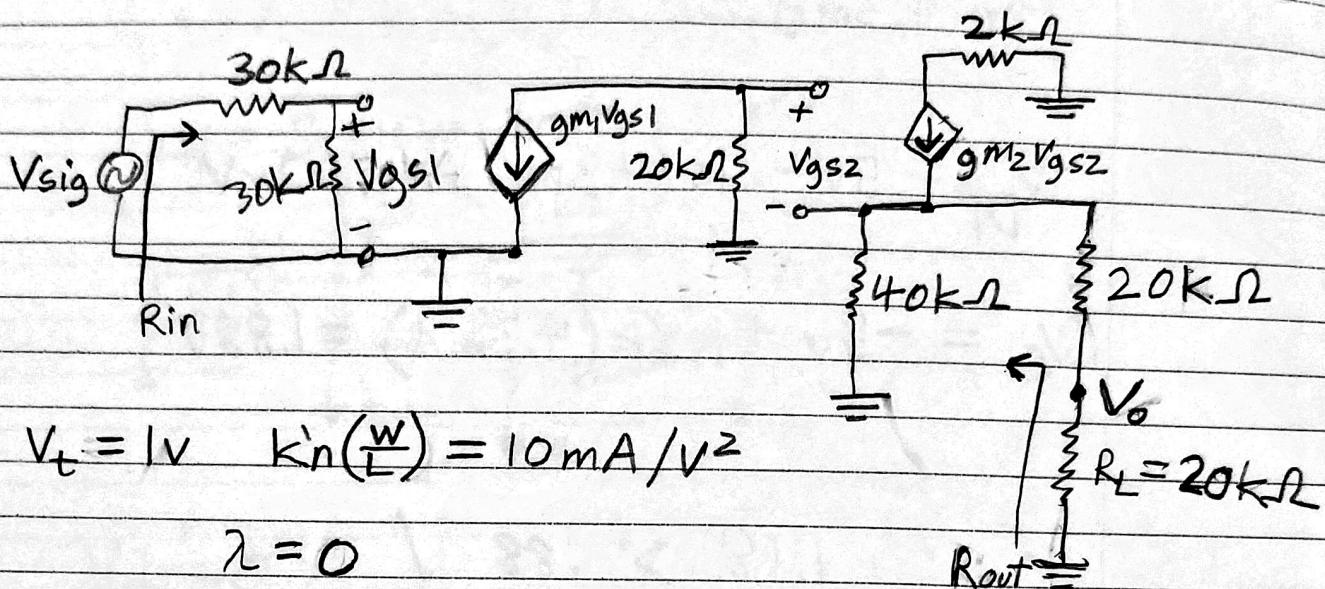

$$V_t = 1\text{V} \quad k'n\left(\frac{w}{L}\right) = 10\text{mA/V}^2$$

$$\lambda = 0$$

$$R_{out}$$

$$M_1: V_{GS} = 9\text{V}, I_D = 3.2\text{A}$$

$$M_2: V_{GS} = 1.18\text{V}, I_D = 162\mu\text{A}$$

$$R_{in} = 60\text{k}\Omega$$

$$R_{out} = 20\text{k}\Omega + 40\text{k} \parallel \frac{1}{gm_2} \\ = 20,548\Omega$$

$$gm_2 = \sqrt{10\text{mA} \cdot 2(162\text{mA})} \\ = 1.8\text{m}$$

$$gm_1 = \sqrt{10\text{mA} \cdot 2(3.2\text{A})} \\ = 253\text{m}$$

$$V_o = \frac{gm_2 V_{GS2} (40\text{k})}{80\text{k}\Omega} (20\text{k}) = 18 V_{GS2}$$

$$V_{GS2} = V_{g2} - V_{s2}$$

$$V_{g2} = -gm_1 V_{GS1} (20\text{k}) = -5060 V_{GS1}$$

$$V_{s2} = \frac{gm_2 V_{GS2} (40\text{k})}{80\text{k}\Omega} (40\text{k}) = 36 V_{GS2}$$

$$V_{gs1} = V_{g1} - V_{s1}$$

$$V_{g1} = \frac{V_{sig}(30k)}{60k}$$

$$V_{s1} = 0$$

$$V_{gs1} = \frac{V_{sig}}{2}$$

$$V_{g2} = \frac{-5060 V_{sig}}{2} = -2530 V_{sig}$$

$$V_{gs2} = -2530 V_{sig} - 36 V_{gs2}$$

$$-5059 V_{gs2} = -36 V_{sig}$$

$$V_{gs2} = 7.1mV_{sig}$$

$$\frac{V_o}{V_{sig}} = +1231$$

9.

$$V_t = 2V, \lambda = 0, k_n\left(\frac{w}{L}\right) = 1mA/\sqrt{2}$$

$$V_{IN} = 5 + 1m \sin(\omega t)$$

$$10mA = \frac{1}{2} (1mA)(0 - (V_s - 2))^2$$

$$V_s = -6.47V$$

$$V_D = 5V$$

$$V_{s\max} = 2(10mA) - 6.47 = -6.45$$

$$V_{s\min} = -2(10mA) - 6.47 = -6.49$$


$$V_{DS} \quad V_{GS} - V_t \\ 5 + 6.47 > 0 - (-6.47) - 2 \quad \checkmark$$

$$V_{GS}^{+7} \quad V_t \\ 0 + 6.47 > 2 \quad \checkmark$$

Because the current source  
is 10mA and not 1mA.

Also the capacitor could cause  
the difference, also outside  
of operating region

10.

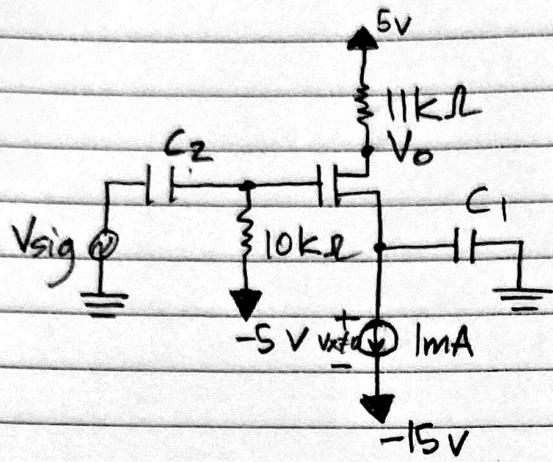

$$V_t = 2V, \lambda = 0$$

$$k_n(\mu) = 2mA/V^2$$

$$V_{IN} = 5 + 50m \sin(\omega t)$$

$$V_G = -5V$$

$I_T$  is outside of  
the operating region

$$ImA = \frac{1}{2}(2mA)(-5 - V_S - 2)^2$$


$$V_S = -8V$$

$$V_D = 5 - 11k(ImA) = -6V$$

$$V_{DS} \quad V_{GS} = V_t$$

$$14 \geq 3 - 2 \quad \checkmark$$

$$V_{GS} > V_t \quad \checkmark$$

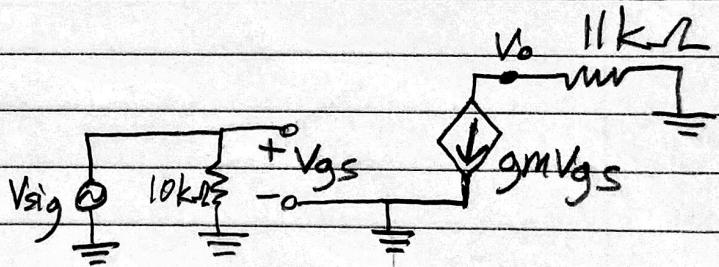

$$V_0 = -gmV_{GS}(11k\Omega)$$

$$R_{in} = 10k\Omega$$

$$R_{out} = 11k\Omega$$

$$V_{GS} = V_{sig} - 0$$

$$gm = 2mA(3 - 2) = 2mA$$

$$\frac{V_0}{V_{sig}} = -22$$