

| | Simulation | | Hand Analysis | |
|-------|------------|---------|---------------|---------|
| | Stage 1 | Stage 2 | Stage 1 | Stage 2 |
| I_C | 93.34mA | 47.21mA | 94mA | 47mA |
| I_B | 888.6nA | 500nA | 900nA | 500nA |
| I_E | 94.23mA | 47.7mA | 95mA | 48mA |
| V_C | 12.67V | 12.64V | 12.7V | 12.6V |
| V_B | 2.485V | 2.492V | 2.5V | 2.5V |
| V_E | 1.885V | 1.909V | 2V | 2V |
| Gain | 10mV/V | 14mV/V | 10mV/V | 14mV/V |

Full circuit Gain = 85

R_{in} :

$$I_{in} = \frac{2.485197250 - 2.48430902}{1k}$$

$$= 888.23\text{nA}$$



$$R_{in} = \frac{2.48430902}{888.23\text{nA}}$$

$$= 2.796\text{M}\Omega$$

Stage 1

$$\underline{R_{out}}: = \frac{12.6396 - 87.4\text{mV}}{87.4\text{mV}} \cdot 50\text{k} = 7.23\text{k}\Omega$$

Stage 2

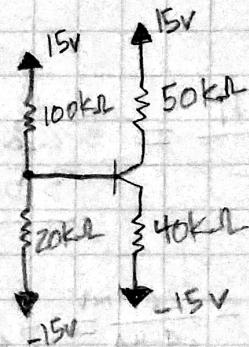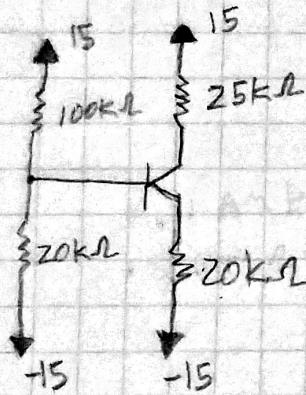

$$V_{Th} = \frac{(15)(20\text{k}\Omega) - (15)(100\text{k}\Omega)}{100\text{k} + 20\text{k}} = -10\text{V}$$


$$V_{Th} = \frac{15(20\text{k}) - 15(100\text{k}\Omega)}{100\text{k} + 20\text{k}\Omega}$$

$$= -10\text{V}$$

$$R_{Th} = 16.6\text{k}\Omega$$

$$-10 - I_B(16.6\text{k}) - 0.7 - I_E(40\text{k}) \stackrel{H(s)}{=} 0$$
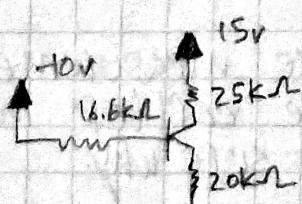
$$R_{Th} = \frac{100\text{k} \cdot 20\text{k}}{100\text{k} + 20\text{k}} = 16.6\text{k}\Omega$$



$$V_{B_1} = -10 - (16.6\text{k}\Omega I_E) = -15\text{V}$$

$$V_{E_1} = 2\text{V}$$

$$V_{C_1} = 15 - I_C(25\text{k}\Omega) = 12.7\text{V}$$

$$V_T = -15\text{V}$$

$$V_{E_2} = 2\text{V} \quad I_{E_2} = 148\text{mA}$$

$$V_{B_2} = -2.5\text{V} \quad I_{B_2} = 500\text{nA}$$

$$V_{C_2} = 12.6\text{V} \quad I_{C_2} = 47\text{mA}$$


$$-10 - I_B(16.6\text{k}\Omega) + 15 = .7 - I_E(20\text{k}\Omega) = 0$$

$$I_{E_1} \left(\frac{-16.6\text{k}\Omega}{10\text{k}} - 20\text{k}\Omega \right) = -4.3 = 295\text{mA}$$

$$I_{B_1} = \frac{I_E}{10\text{k}} = 900\text{nA}$$

$$I_C = 44\text{mA}$$

Full circuit

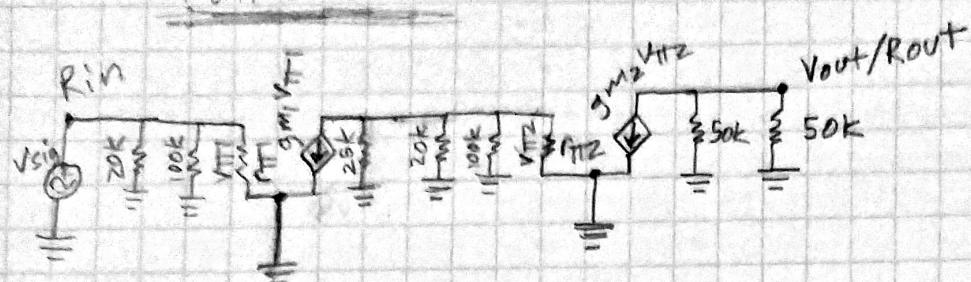

$$V_{out} = \frac{(gm_2 V_{\pi 2})(50k)}{50k + 50k} (50k)$$


* Don't know how to find exact values without any given variables.

$$R_{out} = 50k \parallel 50k = 25k \text{ } \Omega$$

$$R_{in} = (20k \parallel 100k) \parallel r_{\pi 1} = \frac{16.6k(r_{\pi 1})}{16.6k + r_{\pi 1}}$$

$$V_{\pi 2} = \frac{(gm_1 V_{\pi 1})(100k \parallel r_{\pi 2})}{25k \parallel 20k + 100k \parallel r_{\pi 2}}$$
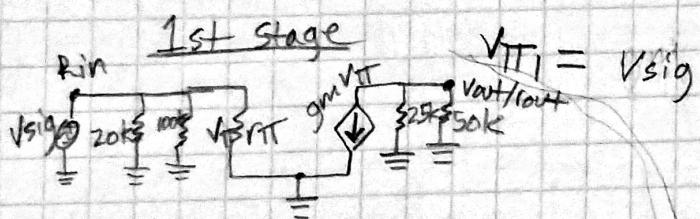
$$r_{\pi 2} = \frac{(gm_1 V_{\pi 1}) \frac{(100k)(r_{\pi 2})}{100k + r_{\pi 2}}}{11.11k + \frac{(100k)(r_{\pi 2})}{100k + r_{\pi 2}}}$$




$$V_{out} = \frac{(gm V_{\pi})(25k)}{75k} (50k)$$

$$V_{\pi} = V_{sig}$$

$$\frac{V_{out}}{V_{sig}} = \frac{(gm)(25k)}{75k} (50k)$$

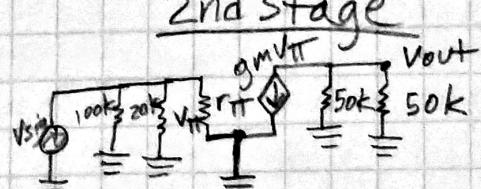
$$V_{out} = (gm_2) \frac{\frac{(100k)(r_{\pi 2})}{100k + r_{\pi 2}}}{11.11k + \frac{(100k)(r_{\pi 2})}{100k + r_{\pi 2}}} V_{sig}$$



$$V_{out} = \frac{(gm V_{\pi}) 50k}{50k}$$


$$\frac{V_{out}}{V_{sig}} = \frac{(gm) 50k}{100k} \frac{100k}{50k}$$

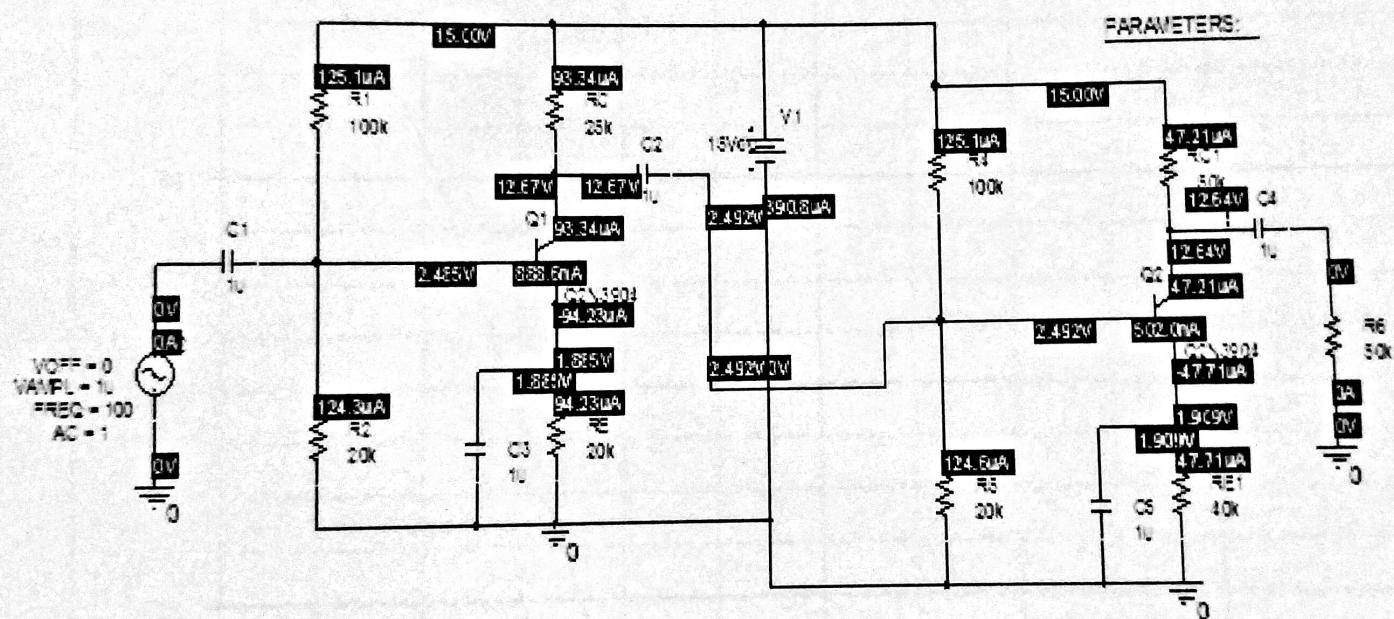Verification of DC voltages and currents for active mode.




(A) Lab3 Experiment 2 Sim. (active)


Impedance Vs. Frequency

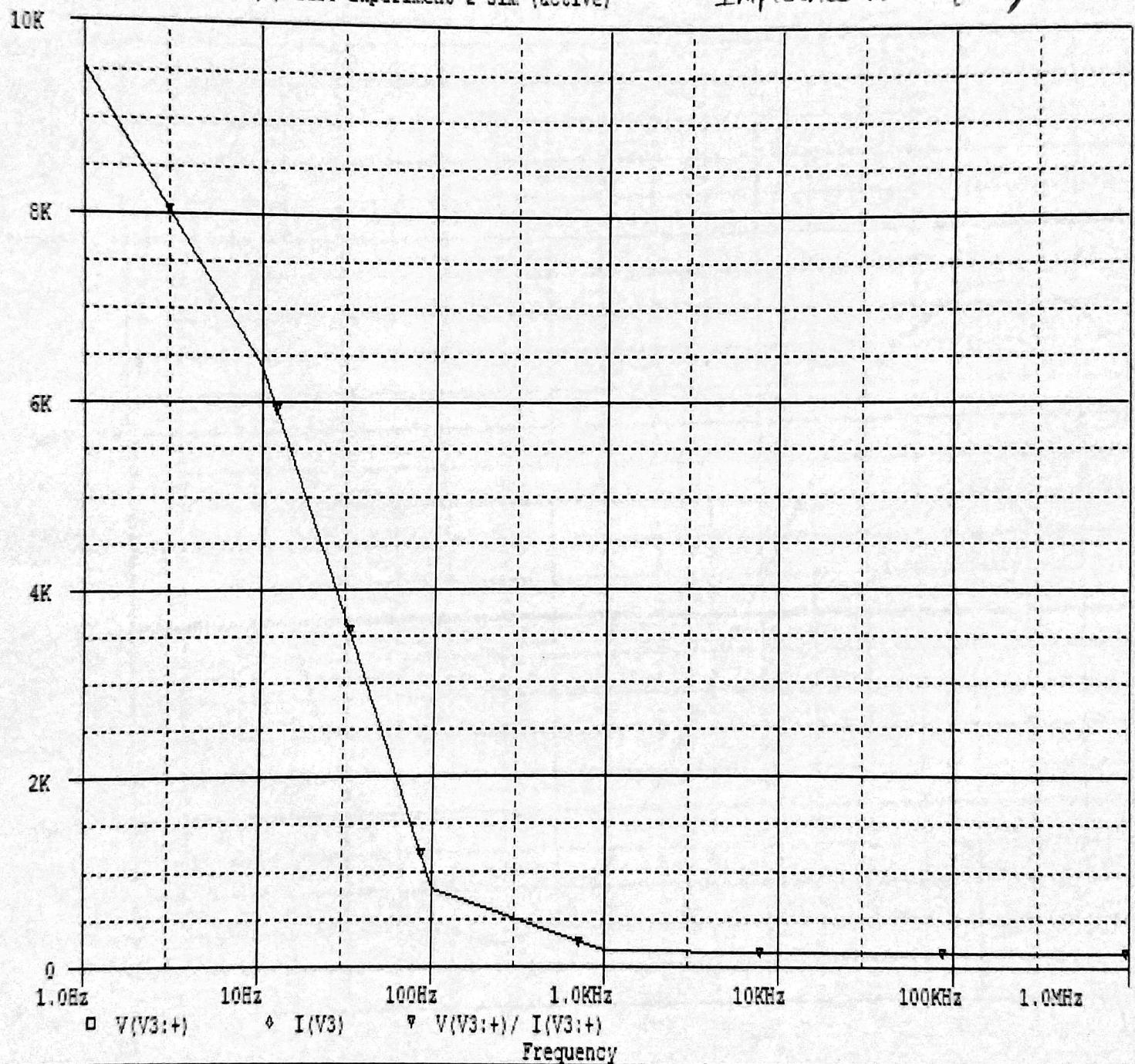


(a) Lab3 Experiment 2 Sim (active)

Gain at 100Hz

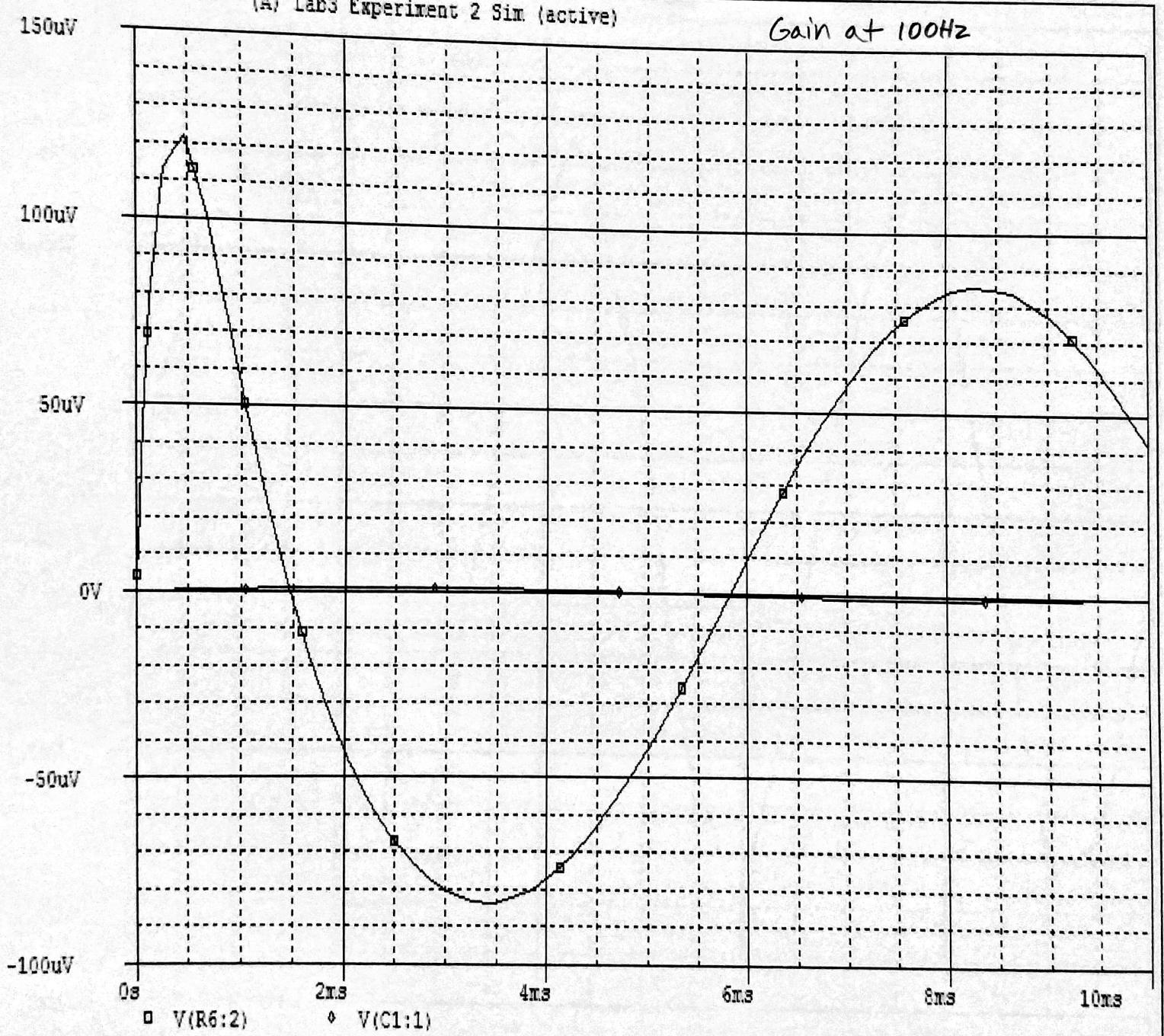

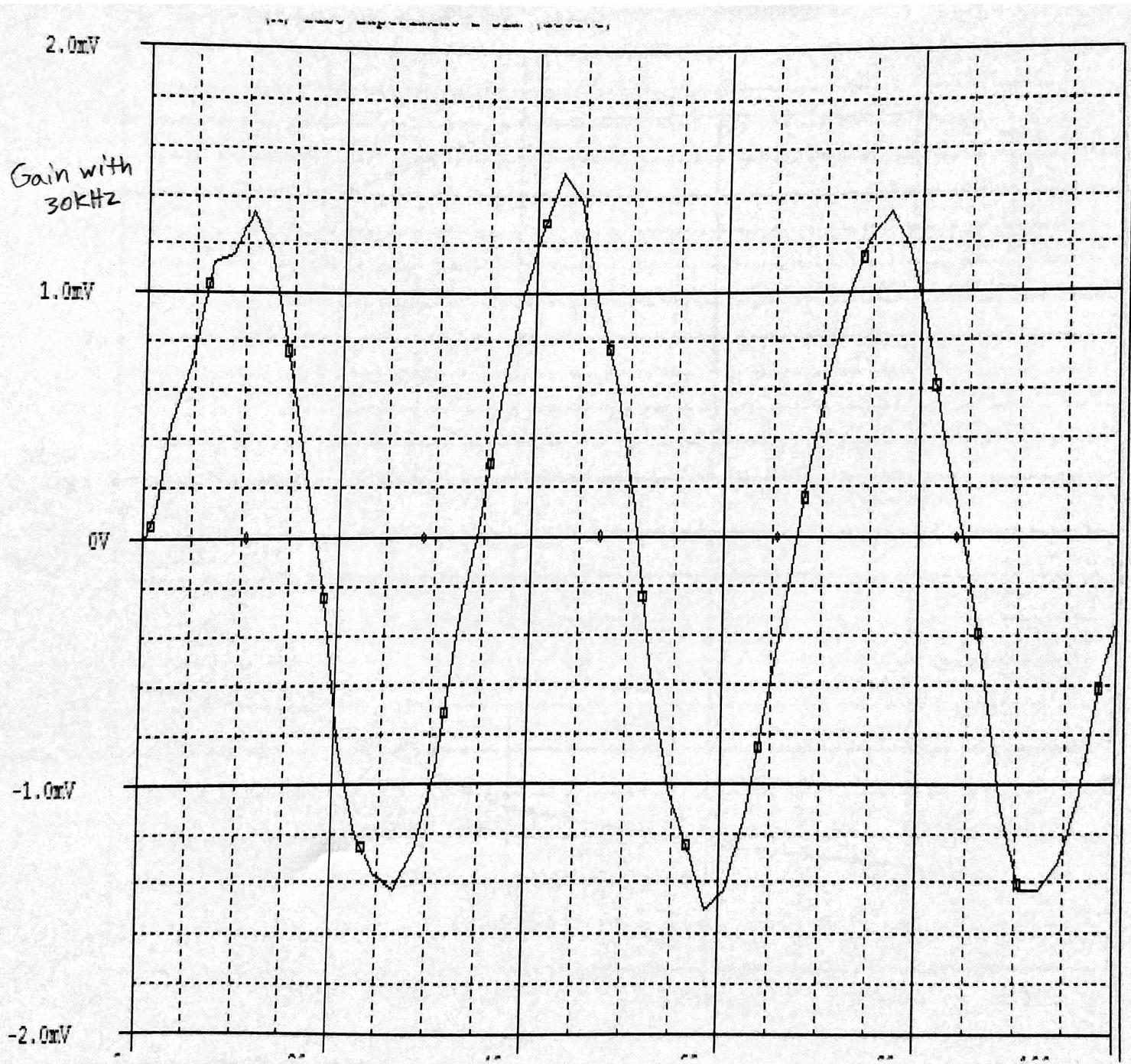

(A) Lab3 Experiment 2 Sim (active)

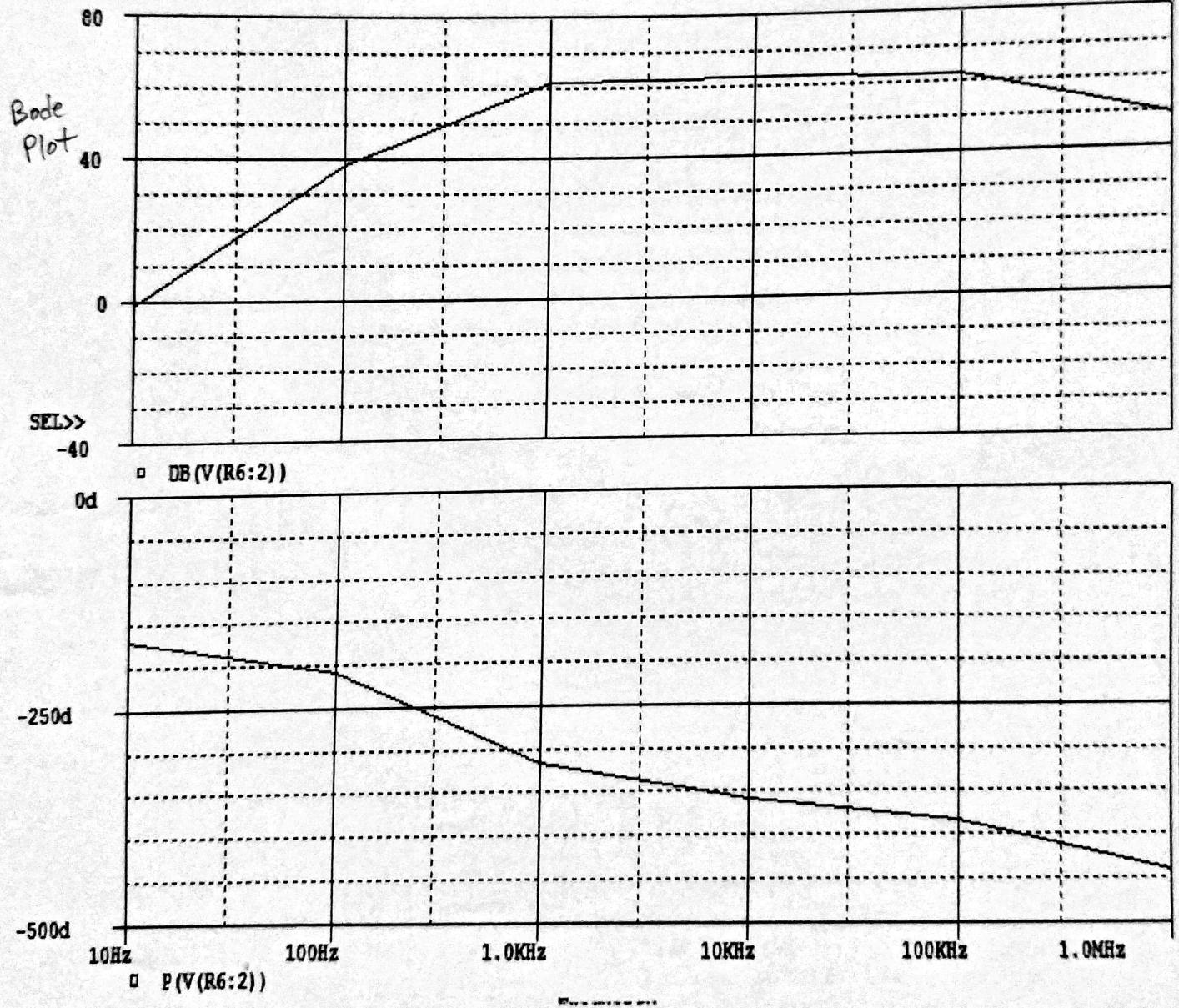

Parts needed:

3x $20k\Omega$
 $0.1\mu F$
 $1\mu F$
 $25k\Omega$
 $100k\Omega$

2x $50k\Omega$
 $40k\Omega$

| MEASUREMENTS | | | |
|--------------|----------------|----------------|------------------|
| | RJT1 | RJT2 | |
| Voltage | E1B1C | E1B1C | 100mV |
| Current | 1mA | 1mA | 1mA |

Measurements:

| | Stage 1 | Stage 2 |
|-------|---------------|---------|
| I_c | 100mA | 50mA |
| I_B | 1mA | .5mA |
| I_E | 100mA | 50mA |
| V_C | 1.82V | 11V |
| V_B | 12.83V | 14.55V |
| V_E | 13.46V | 15V |
| Gain | 30 | 20 |

For better sound, I increased capacitor values from $1\mu F$ to $100\mu F$ for all capacitors.

I'm not entirely sure if I did measurements correct but between 100-30K frequency I was getting an audible sound.

I added an op-amp at the end before output to speaker.

speaker It increased the amplification.

